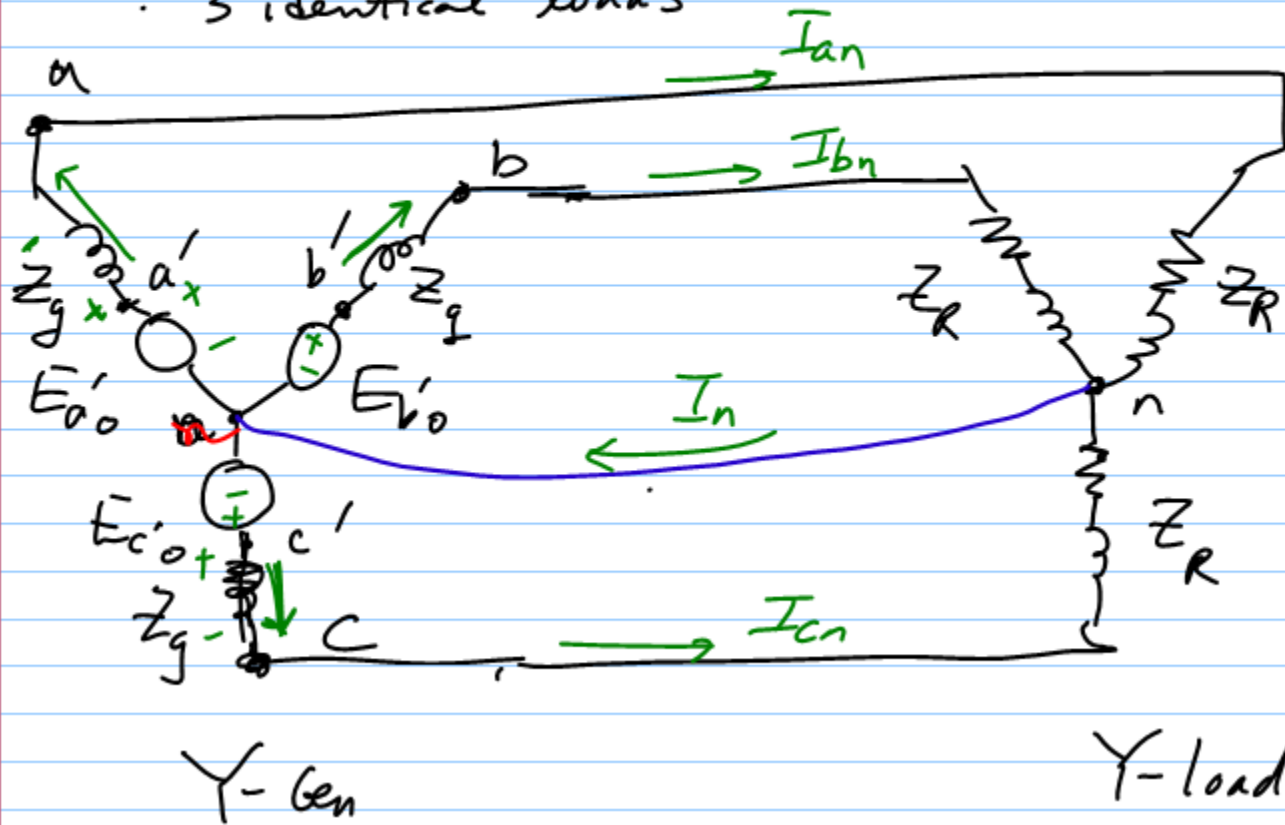


3-Phase Circuits




"Balanced 3- ϕ system"
: 3 ϕ generator
: 3 identical loads



Balanced 3-Phase System

$$E_{a'0} = E \angle 0^\circ \quad E_{b'0} = E \angle -120^\circ \quad E_{c'0} = E \angle 120^\circ$$

$$E_{b'0} (= E \angle 240^\circ)$$

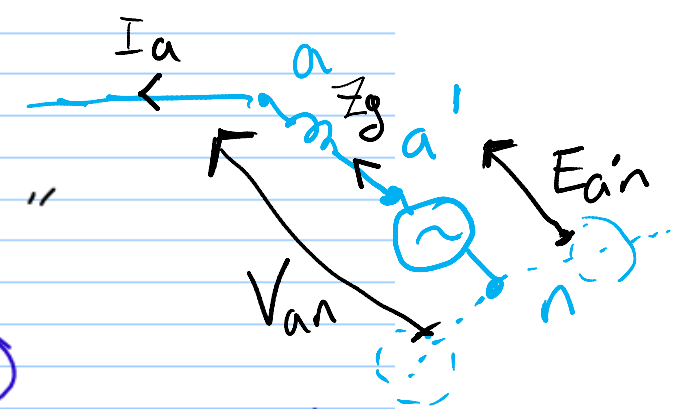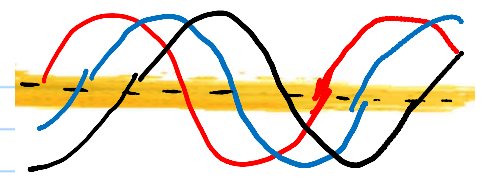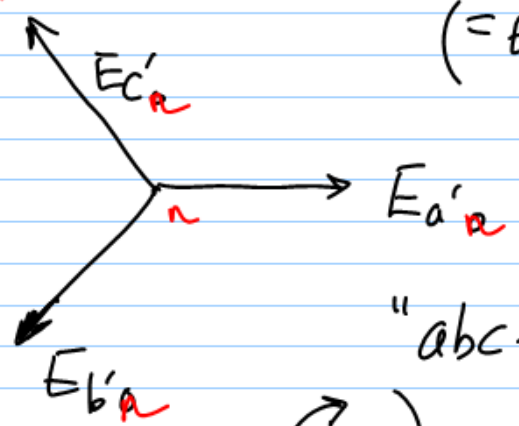

$$V_{an} = E_{a'0} - I_a Z_g$$


$$V_{bn} = E_{b'0} - I_b Z_g$$

$$V_{cn} = E_{c'0} - I_c Z_g$$

$$V_{an} = I_a Z_R \rightarrow I_a = \frac{V_{an}}{Z_R}$$

$$V_{bn} = I_b Z_R \rightarrow I_b = \frac{V_{bn}}{Z_R}$$
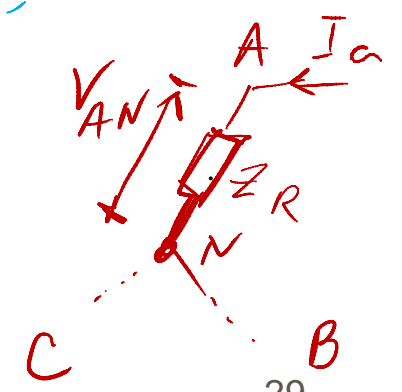
$$V_{cn} = I_c Z_R \rightarrow I_c = \frac{V_{cn}}{Z_R}$$




$$E_{a'a} = I_a (Z_g + Z_R) \rightarrow I_a = \frac{E_{a'a}}{Z_g + Z_R} = \frac{V_{an}}{Z_R}$$

$$E_{b'a} = I_b (Z_g + Z_R) \rightarrow I_b = \frac{E_{b'a}}{Z_g + Z_R} = \frac{V_{bn}}{Z_R}$$

$$E_{c'a} = I_c (Z_g + Z_R) \rightarrow I_c = \frac{E_{c'a}}{Z_g + Z_R} = \frac{V_{cn}}{Z_R}$$


Since $E_{a'a}$, $E_{b'a}$, and $E_{c'a}$ are balanced,

I_a , I_b , & I_c are also balanced.

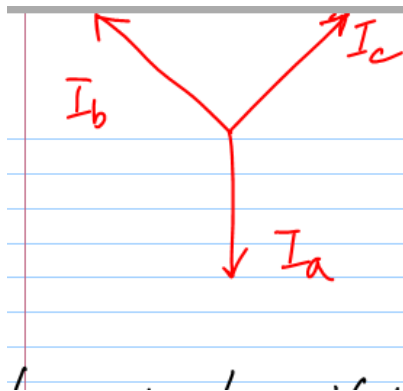

and $I_a + I_b + I_c = 0$

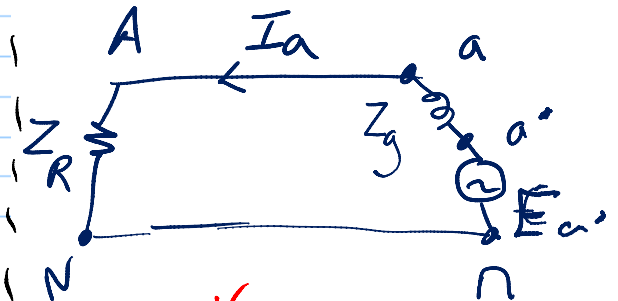$\rightarrow I_n = 0$ No current flow back to generator.




$$I_a = \frac{V_{an}}{Z_R} \text{ @ Load}$$

$$I_a = \frac{E_{a'a}}{Z_g + Z_R} \text{ @ Network}$$

Line-to-Line Voltage


Line-to-Line Voltage
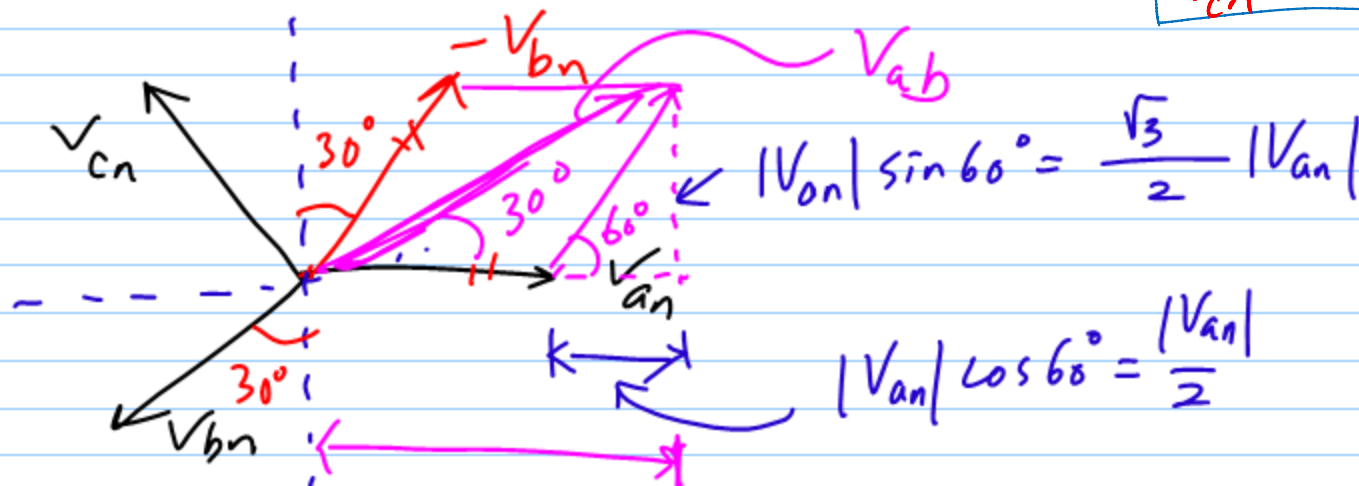
$$\vec{V}_{ab} = \vec{V}_{an} + \vec{V}_{nb} = \vec{V}_{an} - \vec{V}_{bn}$$



$$|V_{ab}| = \sqrt{\left(\frac{\sqrt{3}}{2} |V_{an}|\right)^2 + \left(\frac{3}{2} |V_{an}|\right)^2} = \sqrt{\frac{12}{4} |V_{an}|^2} = \sqrt{3} |V_{an}|$$

Phase Voltage

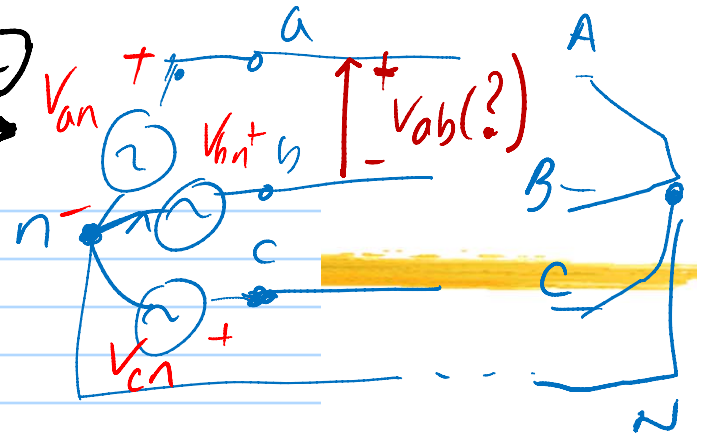


3

$$|V_{ab}| = \sqrt{\left(\frac{\sqrt{3}}{2}|V_{an}|\right)^2 + \left(\frac{3}{2}|V_{an}|\right)^2} = \sqrt{\frac{12}{4}|V_{an}|^2} = \sqrt{3}|V_{an}|$$

$$\Rightarrow \underline{V_{ab}} = \sqrt{3} \underline{V_{an}} \angle 30^\circ$$
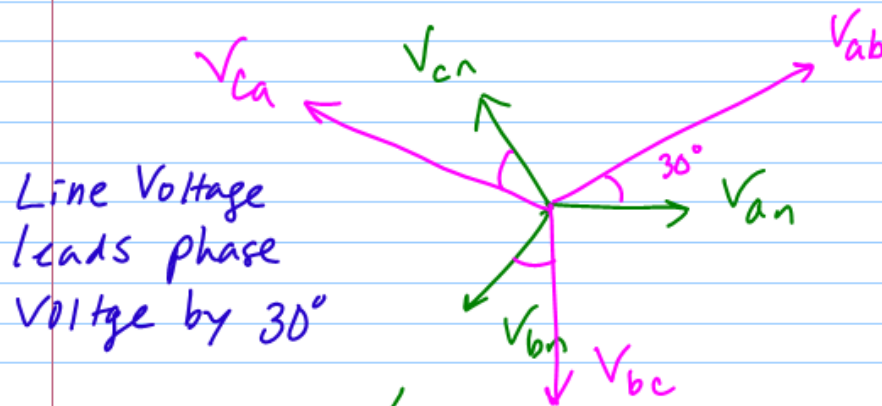
$$\Rightarrow \underline{V_{bc}} = \sqrt{3} \underline{V_{bn}} \angle 30^\circ \quad \Rightarrow \underline{V_{ca}} = \sqrt{3} \underline{V_{cn}} \angle 30^\circ$$



Line Voltage
leads phase
Voltage by 30°

Also,

$$\underline{V_{ab}} + \underline{V_{bc}} + \underline{V_{ca}} = 0$$

⌘ Algebraic Calculation

$$V = 100$$

$$V_{an} = V \cdot \exp(i \cdot 0) = 100$$

$$V_{bn} = V \cdot \exp\left[i \cdot (-120) \cdot \frac{\pi}{180}\right] = -50 - 86.6025404 \cdot i$$

$$V_{cn} = V \cdot \exp\left[i \cdot (120) \cdot \frac{\pi}{180}\right] = -50 + 86.6025404 \cdot i$$

$$V_{ab} = V_{an} - V_{bn} = 150 + 86.6025404 \cdot i$$

$$|V_{ab}| = 173.2050808$$

$$\theta_{ab} = \operatorname{atan}\left(\frac{\operatorname{Im}(V_{ab})}{\operatorname{Re}(V_{ab})}\right) \cdot \frac{180}{\pi} = 30$$

$$V_{ca} = V_{cn} - V_{an} = -150 + 86.6025404 \cdot i$$

$$|V_{ca}| = 173.2050808$$


$$\theta_{ca} = \operatorname{atan}\left(\frac{\operatorname{Im}(V_{ca})}{\operatorname{Re}(V_{ca})}\right) \cdot \frac{180}{\pi} = -30$$

$$\theta_{ca} = \theta_{ca} + 180 = 150$$

$$|V_{ab}| = \sqrt{\left(\frac{\sqrt{3}}{2}|V_{an}|\right)^2 + \left(\frac{3}{2}|V_{an}|\right)^2} = \sqrt{\frac{12}{4}|V_{an}|^2} = \sqrt{3}|V_{an}|$$

$$\Rightarrow \overline{V_{ab}} = \sqrt{3} \overline{V_{an}} \angle 30^\circ$$
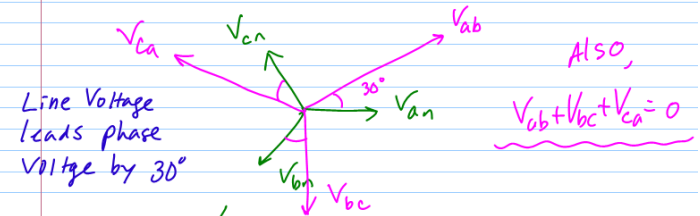
$$\Rightarrow \overline{V_{bc}} = \sqrt{3} \overline{V_{bn}} \angle 30^\circ \Rightarrow \overline{V_{ca}} = \sqrt{3} \overline{V_{cn}} \angle 30^\circ$$




$$V = 100$$

$$\theta_a = 0 \quad \theta_b = -120 \cdot \frac{\pi}{180} \quad \theta_c = 120 \cdot \frac{\pi}{180}$$


$$v_{an} = V \cdot (\cos(\theta_a) + i \cdot \sin(\theta_a)) = 100$$

$$v_{bn} = V \cdot (\cos(\theta_b) + i \cdot \sin(\theta_b)) = -50 - 86.6025404 \cdot i$$
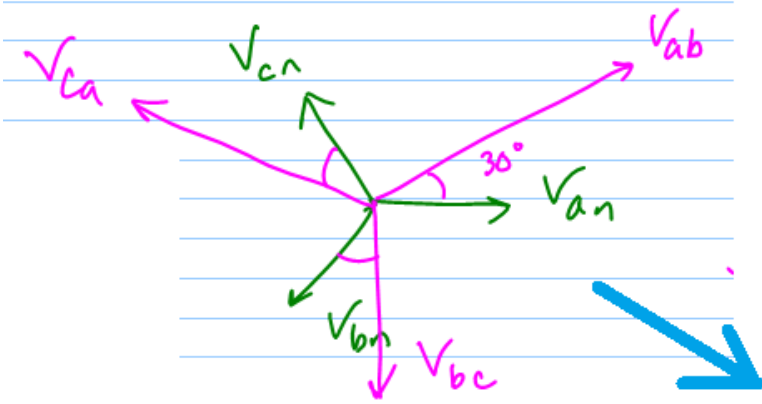
$$v_{cn} = V \cdot (\cos(\theta_c) + i \cdot \sin(\theta_c)) = -50 + 86.6025404 \cdot i$$



Line-To-Line Voltage (V_{ab}) vs. Phase Voltage (V_{an})

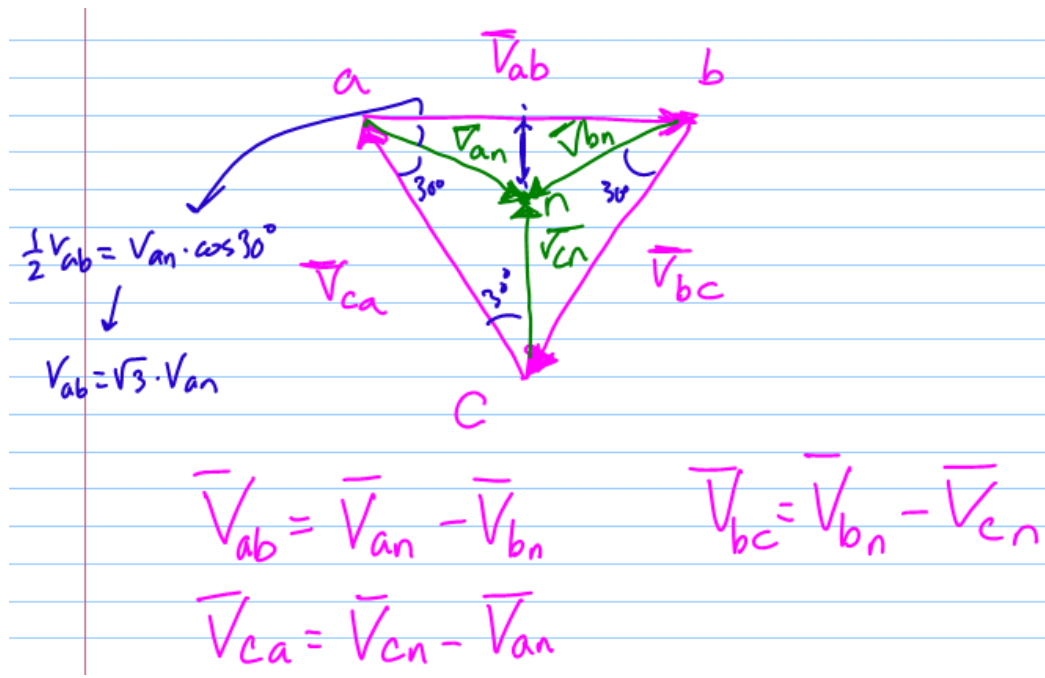

Example 2.2


In a balanced 3- ϕ circuit, $\overline{V}_{ab} = 173.2 \angle 0^\circ \text{ V}$.
Determine all the voltages and the currents in
a Y-connected load having $\underline{Z}_L = 10 \angle 20^\circ \Omega$.

⌘ Can you draw a circuit diagram for this example question?

Example 2.2

In a balanced 3- ϕ circuit, $\bar{V}_{ab} = 173.2 \angle 0^\circ$ V. Determine all the voltages and the currents in a Y-connected load having $Z_L = 10 \angle 20^\circ \Omega$.

Solution

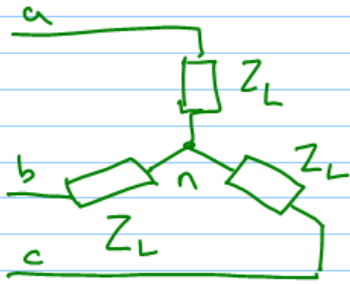

$$\bar{V}_{ab} = 173.2 \angle 0^\circ$$

$$\rightarrow \bar{V}_{bc} = 173.2 \angle -120^\circ$$

$$\bar{V}_{ca} = 173.2 \angle 120^\circ$$

$$\text{From } \bar{V}_{ab} = \sqrt{3} \bar{V}_{an} \angle 30^\circ$$


$$\bar{V}_{an} = \frac{1}{\sqrt{3}} \bar{V}_{ab} \angle -30^\circ = 100 \angle -30^\circ$$

$$\bar{V}_{bn} = 100 \angle -150^\circ$$

$$\bar{V}_{cn} = 100 \angle 90^\circ$$


$$\bar{I}_{a'} = \frac{V_{an}}{Z_L} = \frac{100 \angle -30^\circ}{10 \angle 20^\circ} = 10 \angle -50^\circ$$
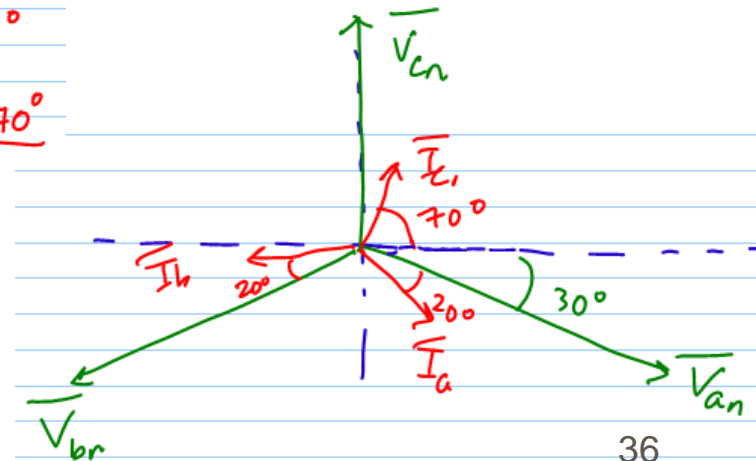
$$\bar{I}_b = 10 \angle -170^\circ, \quad \bar{I}_c = 10 \angle 70^\circ$$




Delta (Δ) Load

I_a ?

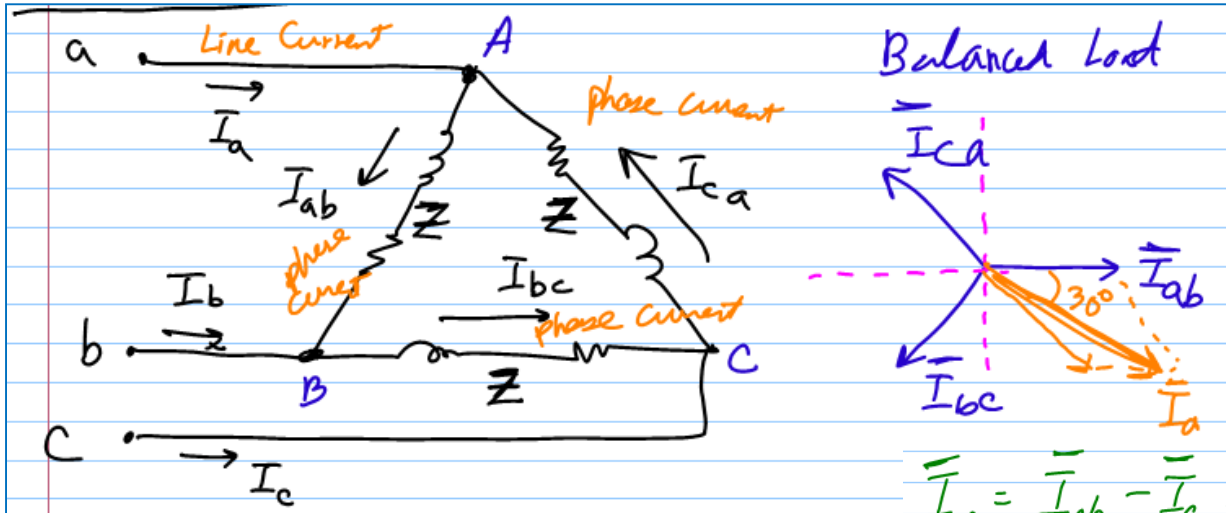

Balanced Load

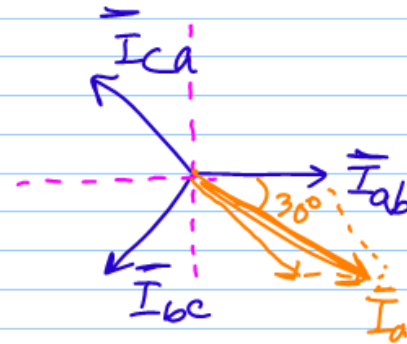

$$\vec{I}_a = \vec{I}_{ab} - \vec{I}_{ca} = \vec{I}_{ab} - \vec{I}_{ab} \angle 120^\circ$$

$$= \vec{I}_{ab} (1 - \angle 120^\circ)$$

$$= \vec{I}_{ab} \left(1 - \left(-\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) \right)$$

$$= \vec{I}_{ab} \left(\frac{3}{2} - j \frac{\sqrt{3}}{2} \right)$$


$$= \sqrt{3} \vec{I}_{ab} \angle -30^\circ$$

$$\vec{I}_b = \sqrt{3} \vec{I}_{bc} \angle -30^\circ$$

$$\vec{I}_c = \sqrt{3} \vec{I}_{ca} \angle -30^\circ$$




Phase current
leads line current
by 30°

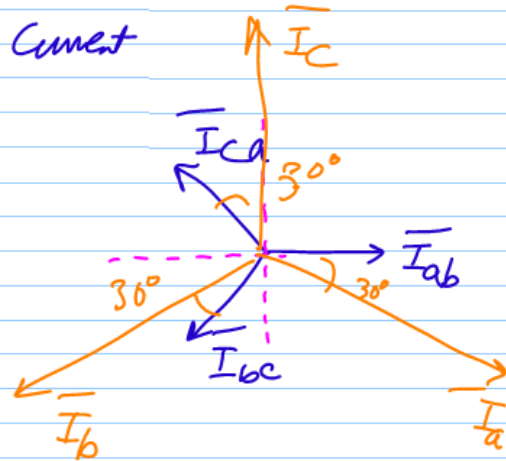


Per-phase analysis

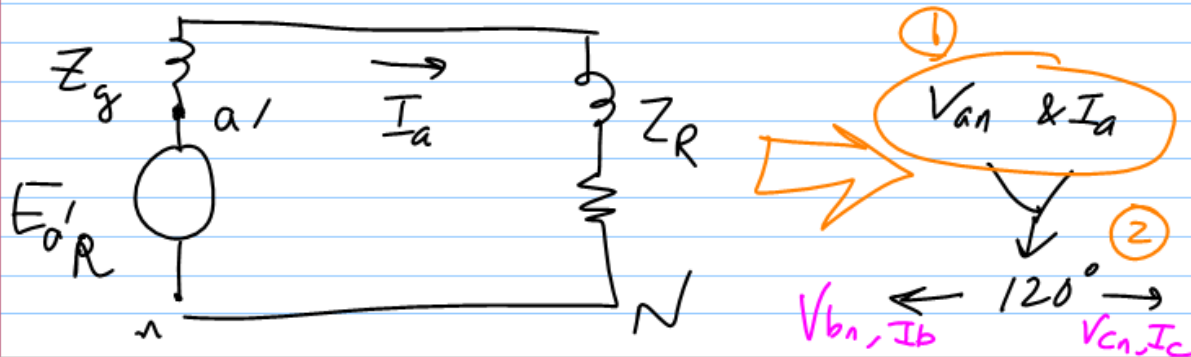Since, in Balanced System, voltage and currents in all 3 phases are the same in Magnitude, and the only difference is the phase angle, which we know (120° apart), we can do 3- ϕ circuit w/ single-phase equivalent circuit. \rightarrow "per-phase analysis"



Per-phase analysis with Delta (Δ) load \rightarrow Convert to Y-load

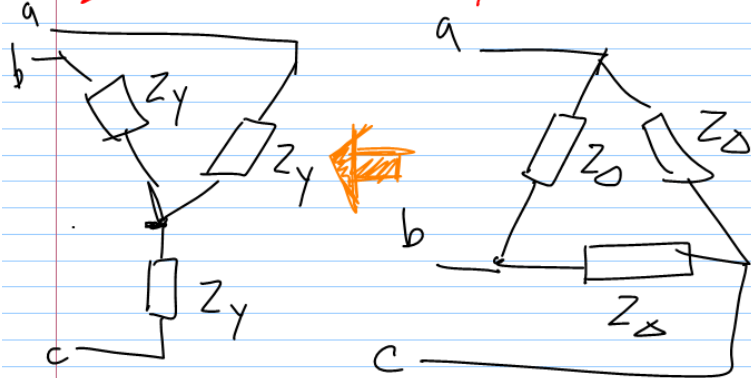CAVEAT: If the load is in Δ connection, it must be converted to Y-connected load.



① $Z_{ab} = Z_{\Delta} // 2Z_{\Delta}$
 $= \frac{2 \cdot Z_{\Delta}^2}{3Z_{\Delta}} = \frac{2 \cdot Z_{\Delta}}{3}$

② $Z_{ab} = Z_Y + Z_Y = 2Z_Y$

$\frac{2}{3} Z_{\Delta} = 2Z_Y$

Equivalent load in Y-load converted from Δ -load

$Z_Y = \frac{Z_{\Delta}}{3}$ Load in Δ -load

Example 2.3


Example 2.3 (p. 28). The terminal voltage of a Y-connected load consisting of 3 equal impedances of $20\angle 30^\circ \Omega$ is 4.4 kV line-to-line. The impedance of each of the 3 lines connecting the load to a bus at a substation is $Z_L = 1.4\angle 75^\circ \Omega$. Find the line-to-line voltage at the substation bus.

⌘ Draw a circuit diagram for this example question.


Example 2.3

Example 2.3 (p. 28). The terminal voltage of a Y-connected load consisting of 3 equal impedances of $20\angle 30^\circ \Omega$ is 4.4 kV line-to-line. The impedance of each of the 3 lines connecting the load to a bus at a substation is $Z_L = 1.4\angle 75^\circ \Omega$. Find the line-to-line voltage at the substation bus.

(Sol) 3 ϕ diagram

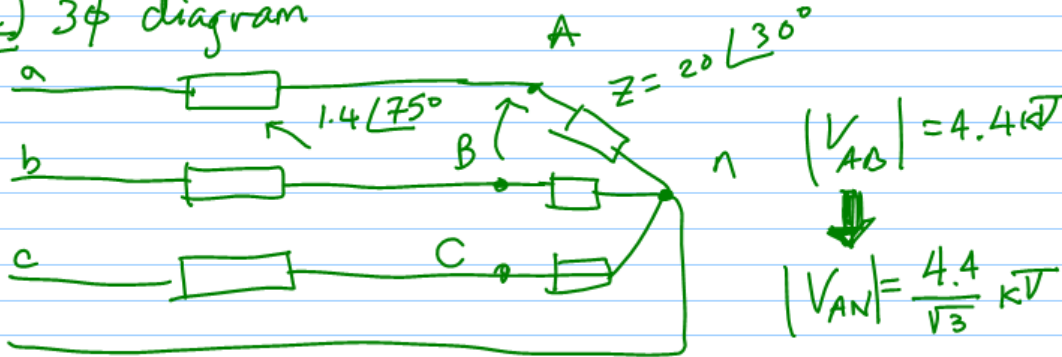

→ Single-phase equivalent circuit

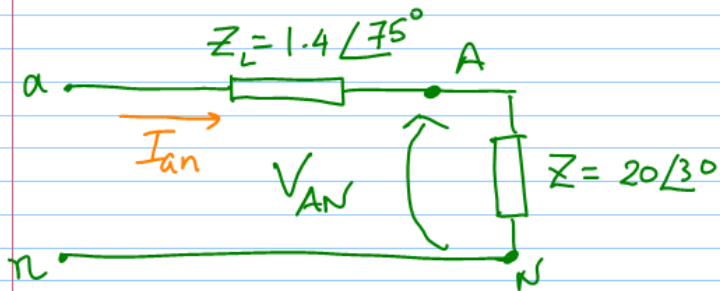


$$V_{AN} = \frac{4400}{\sqrt{3}} \angle 0^\circ \leftarrow \text{we choose phase a voltage as reference,}$$

$$= 2540 \angle 0^\circ$$

$$I_{an} = \frac{V_{AN}}{Z} = \frac{2540 \angle 0^\circ}{20 \angle 30^\circ} = 127 \angle -30^\circ$$

Example 2.3 - Continued

→ Single-phase equivalent circuit

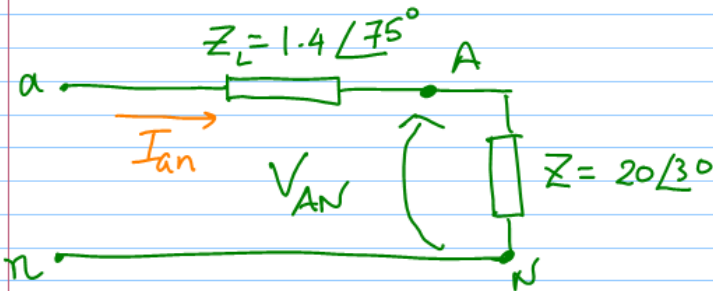

$$V_{AN} = \frac{4400}{\sqrt{3}} \angle 0^\circ \leftarrow \text{we choose phase a voltage as reference,}$$

$$= 2540 \angle 0^\circ$$

$$I_{an} = \frac{V_{AN}}{Z} = \frac{2540 \angle 0^\circ}{20 \angle 30^\circ} = 127 \angle -30^\circ$$

$$\rightarrow V_{an} = V_{AN} + I_{an} \cdot Z_L = 2540 \angle 0^\circ + (127 \angle -30^\circ)(1.4 \angle 75^\circ)$$

$$= 2666 + j125.7$$


$$= 2670 \angle 2.70^\circ$$

$$\rightarrow V_{ab} = \sqrt{3} V_{an} \angle 30^\circ = \sqrt{3} (2670) \angle 32.70^\circ$$


$$= 4620 \angle 32.70^\circ$$

$$\therefore |V_{ab}| = 4.62 \text{ kV}$$

Y-load and Δ -load in parallel

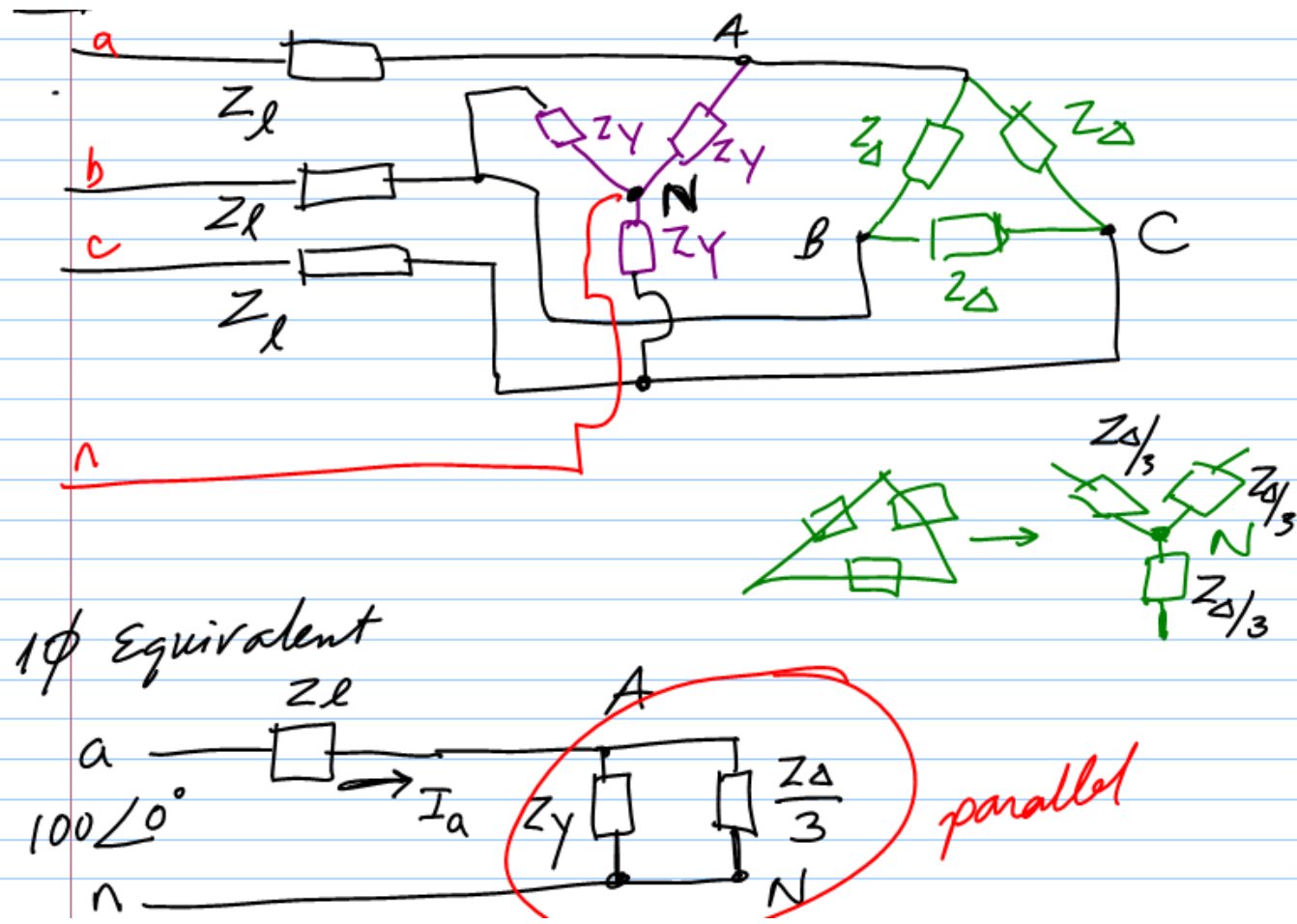

Y-load and Δ -load in parallel - Example

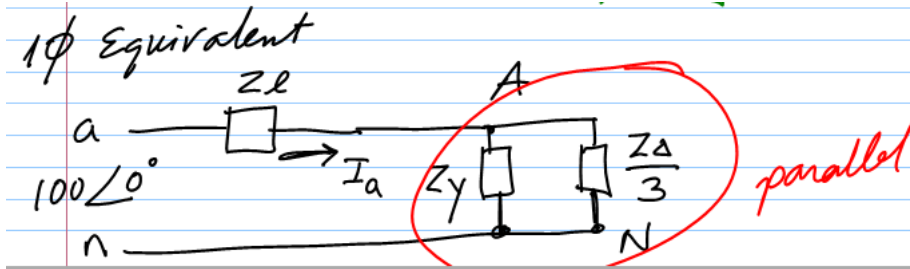

$$Z_L = j5, \quad Z_Y = 10 + j20, \quad Z_C = -j5$$

$$Z_Y \parallel Z_C \rightarrow \frac{(10 + j20)(-j5)}{(10 + j20) + (-j5)} = \frac{100 - j50}{10 + j15}$$

$$= \frac{20 - j10}{2 + j3} = \frac{(20 - j10)(2 - j3)}{(2 + j3)(2 - j3)}$$

$$= \frac{40 - j60 - j20 - 30}{13} = \frac{10 - j80}{13}$$

$$= 0.7692 - j6.1538$$

$Z_Y = 10 + j20$ $Z_C = -j5$
 $Z_P = \frac{Z_Y \cdot Z_C}{Z_Y + Z_C} = 0.7692 - 6.1538 \cdot j$

$$Z_P + Z_L = 0.7692 - j6.1538 + j5$$

$$= 0.7692 - j1.1538$$

$$= \sqrt{0.7692^2 + 1.1538^2} \angle \tan^{-1} \frac{-1.1538}{0.7692}$$

$$= 1.3868 \angle -56.31^\circ$$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{100 \angle 0^\circ}{1.3868 \angle -56.31^\circ}$$

$$= 72.11 \angle -56.31^\circ$$

$V = 100 + j0$
 $Z = Z_P + j5 = 0.7692 - 1.1538 \cdot j$
 $|Z| = 1.3868$
 $\arg(Z) = \frac{180}{\pi} \cdot -56.3099$
 $I = \frac{V}{Z} = 40 + 60 \cdot j$
 $|I| = 72.111$
 $\arg(I) = \frac{180}{\pi} \cdot -56.3099$

Power in balanced 3-phase circuits

$$P_{3\phi} = P_a + P_b + P_c$$

$$= 3 \cdot P_a \text{ (in Balanced system)}$$

V_p : phase voltage magnitude to neutral

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

I_p : phase current magnitude for Y-Load

$$I_p = |I_{an}| = |I_{bn}| = |I_{cn}|$$

$$\Rightarrow P_{3\phi} = 3 V_p I_p \cos \theta_p$$

θ_p : phase angle between \vec{V}_p & \vec{I}_p
: angle to the impedance $\rightarrow \theta_z$

Power in balanced 3-phase circuits

V_L : Line-to-Line Voltage magnitude or 1 ϕ eqn

$$V_p = \frac{V_L}{\sqrt{3}} \quad \text{and} \quad I_p = I_L \quad (\text{Y-load case})$$

$$I_L = I_p \sqrt{3} \quad \text{current over a line}$$

$$\Rightarrow P_{3\phi} = 3 V_p I_p \cos \theta_p$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta_p = \sqrt{3} V_L I_L \cos \theta_p$$

$$\& Q_{3\phi} = 3 V_p I_p \sin \theta_p = \sqrt{3} V_L I_L \sin \theta_p$$

Further,

$$S_{3\phi} = P_{3\phi} + j Q_{3\phi}$$

$$|S_{3\phi}| = \sqrt{P_{3\phi}^2 + Q_{3\phi}^2}$$

$$= \sqrt{3} V_L I_L$$

$$= 3 V_p I_p$$

3-phase instantaneous power $p_3(t)$

$$v_a = V_m \cos \omega t$$

$$i_a = I_m \cos(\omega t - \theta)$$

$$v_b = V_m \cos(\omega t - 120^\circ)$$

$$i_b = I_m \cos(\omega t - \theta - 120^\circ)$$

$$v_c = V_m \cos(\omega t + 120^\circ)$$

$$i_c = I_m \cos(\omega t - \theta + 120^\circ)$$

$$P_{3\phi} = P_a(t) + P_b(t) + P_c(t)$$

$$= V_m I_m \cos \omega t \cdot \cos(\omega t - \theta)$$

$$+ V_m I_m \cos(\omega t - 120^\circ) \cdot \cos(\omega t - 120^\circ - \theta)$$

$$+ V_m I_m \cos(\omega t + 120^\circ) \cdot \cos(\omega t + 120^\circ - \theta)$$

3-phase instantaneous power $p_3(t)$

From, 1ϕ instantaneous power $p(t)$

Phase a:

$$P_a(t) = \frac{V_m I_m}{2} \cos\theta + \frac{V_m I_m}{2} \cos\theta \cdot \cos 2\omega t + \frac{V_m I_m}{2} \sin\theta \cdot \sin 2\omega t$$

Phase b:

$$P_b(t) = \frac{V_m I_m}{2} \cos\theta + \frac{V_m I_m}{2} \cos\theta \cdot \cos(2\omega t - 240^\circ)$$

$$\frac{V_m I_m}{2} \sin\theta \cdot \sin(2\omega t - 240^\circ)$$

Phase c:

$$P_c(t) = \frac{V_m I_m}{2} \cos\theta + \frac{V_m I_m}{2} \cos\theta \cdot \cos(2\omega t + 240^\circ)$$

$$\frac{V_m I_m}{2} \sin\theta \cdot \sin(2\omega t + 240^\circ)$$

3-phase instantaneous power $p_3(t)$

$$P_3(t) = P_a(t) + P_b(t) + P_c(t)$$

$$= 3 \left(\frac{V_m I_m}{2} \cos \theta \right) + \frac{V_m I_m}{2} \cos \theta \left\{ \cos 2\omega t + \cos(2\omega t - 240^\circ) + \cos(2\omega t + 240^\circ) \right\}$$

$$+ \frac{V_m I_m}{2} \sin \theta \left\{ \sin 2\omega t + \sin(2\omega t - 240^\circ) + \sin(2\omega t + 240^\circ) \right\}$$

$$= 3 \frac{V_m I_m}{2} \cos \theta = 3 |V| |I| \cos \theta$$

Constant !!

$$\underline{\underline{P_3(t) = \text{Constant}}}$$

