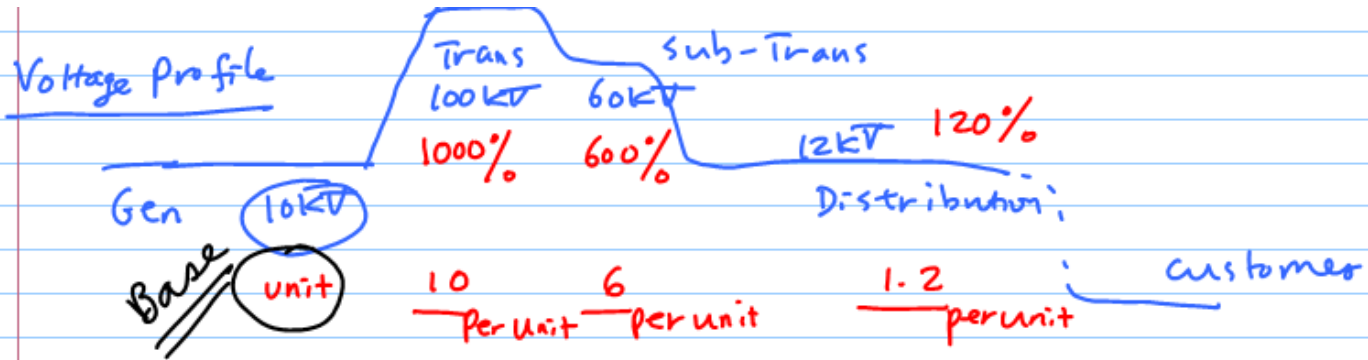


Per-unit (2.10 - 2.11)



(KV)

V, I,
VA, Z

Inter-related
Base Value

Knowing any 2 would
decide the other 2.

(KVA)

$$\left(\begin{array}{l} VA = V \cdot I \\ V = I \cdot Z \\ I = \frac{V}{Z} \end{array} \right)$$

• I_{base}

$$I = \frac{VA}{V}$$

$$[A] = \frac{S_{Base} \text{ KVA} \phi}{V_{Base} \text{ KV}_{LN}}$$


$$\bullet Z_{base} [\Omega] = \frac{V_{Base} V_{LN}}{I_{base, A}}$$

$$Z = \frac{V}{I}$$

$$VA = |S|$$

$$KVA = K|S|$$

Apparent
power

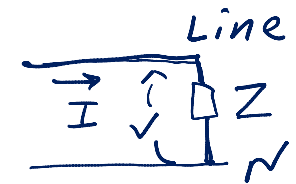

Per-unit system

$$\bullet Z_{base} [\Omega] = \frac{V_{Base}, V_{LN}}{I_{base}, A}$$
$$Z = \frac{V}{I}$$

$$\bullet Z_{base} = \frac{(V_{Base} \text{ kV}_{LN})^2 \times 10^3}{S_{base} \text{ kVA}_{1\phi}}$$

$$Z = \frac{V}{I} = \frac{V}{VA/V} = \frac{V^2}{VA}$$

$$Z_{base} = \frac{(V_{Base} \text{ kV}_{LN})^2}{S_{base} \text{ MVA}_{1\phi}}$$

$$P_{base} \text{ kW}_{1\phi} = S_{base} \text{ kVA}_{1\phi}$$

$$P_{base} \text{ MW}_{1\phi} = S_{base} \text{ MVA}_{1\phi}$$

$$Z_{pu} = \frac{Z_{actual} \Omega}{Z_{Base} \Omega}$$

• Usual Base Quantities in Power System Analysis

- ① $S_{base} \text{ MVA}$
- ② $V_{base} \text{ kV}_{LN}$

Per-unit system

3 ϕ case:

$$\text{If } S_{\text{Base}} \text{ kVA}_{3\phi} = 30,000 \text{ kVA}$$

$$\&V_{\text{Base}} \text{ kV}_{LL} = 120 \text{ kV},$$

Then \rightarrow

$$S_{\text{Base}} \text{ kVA}_{1\phi} = \frac{S_{\text{Base}} \text{ kVA}_{3\phi}}{3} = 10,000 \text{ kVA}$$

$$\&V_{\text{Base}} \text{ kV}_{LN} = \frac{120 \text{ kV}}{\sqrt{3}} = 69.2 \text{ kV}$$

If an Actual line-to-line voltage is
 $V_{LL} = 108 \text{ kV}$, $\rightarrow V_{LN} = \frac{108}{\sqrt{3}} = 62.3 \text{ kV}$


$$\rightarrow \text{per-unit Voltage} = \frac{62.3 \text{ kV}}{69.2 \text{ kV}} = 0.9$$

If total 3 ϕ power is 18,000 kW
(per phase power is 6000 kW)

$$\rightarrow \text{per unit Power} = \frac{18,000}{30,000} = \frac{6,000}{10,000} = 0.6$$

Per-unit system


$$\begin{aligned}
 I_{\text{base}} \text{ A} &= \frac{S_{\text{Base}} \text{ kVA}_{1\phi}}{V_{\text{Base}} \text{ Voltage } \text{kV}_{\text{LN}}} \\
 &= \frac{S_{\text{Base}} \text{ kVA}_{3\phi} / 3}{V_{\text{Base}} \text{ Voltage } \text{kV}_{\text{LL}} / \sqrt{3}} \\
 &= \frac{S_{\text{Base}} \text{ kVA}_{3\phi}}{\sqrt{3} \cdot V_{\text{Base}} \text{ Voltage } \text{kV}_{\text{LL}}}
 \end{aligned}$$

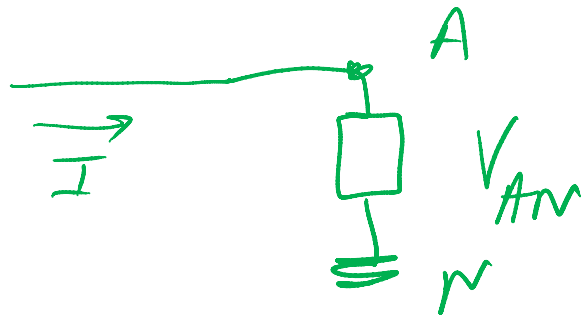

$$\begin{aligned}
 Z_{\text{base}} &= \frac{(V_{\text{base}} \text{ kV}_{\text{LN}})^2 \cdot 10^3}{S_{\text{Base}} \text{ kVA}_{1\phi}} \\
 &= \frac{(V_{\text{base}} \text{ kV}_{\text{LL}} / \sqrt{3})^2 \cdot 10^3}{S_{\text{Base}} \text{ kVA}_{3\phi} / 3} \\
 &= \frac{(V_{\text{base}} \text{ kV}_{\text{LL}})^2 \cdot 10^3}{S_{\text{Base}} \text{ kVA}_{3\phi}} \\
 &= \frac{(V_{\text{base}} \text{ kV}_{\text{LL}})^2 \cdot 10^3}{S_{\text{Base}} \text{ MVA}_{3\phi} / 10^3} \\
 &= \frac{(V_{\text{base}} \text{ kV}_{\text{LL}})^2}{S_{\text{Base}} \text{ MVA}_{3\phi}}
 \end{aligned}$$

$Z_{\text{base}} = \frac{V_{\text{base}}}{I_{\text{base}}}$
 $= \frac{V_{\text{base}}^2}{S_{\text{base}}}$

Per-unit system

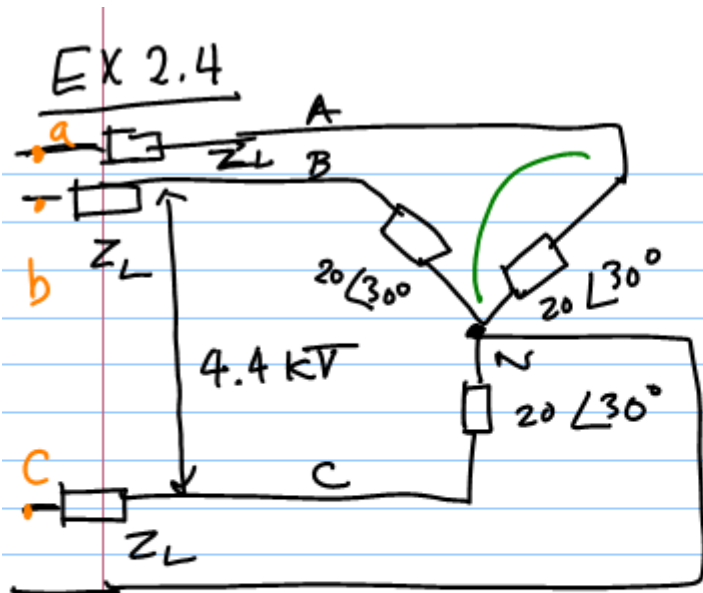

$Z_L = 1.4 \angle 75^\circ$
 Line Impedance
 Between the
 Substation and
 the Load

Q Find the
 Line-to-Line
 Voltage at the
 Substation by

using per-unit (pu) on a base of


4.4 kV and 127 A.

$V_{Base KVLL}$ $I_{Base A}$

$V_{base KVLL} \rightarrow V_{base KV_{LN}}$

Note
 V_{Base} given
 as line-to-
 line voltage.

Per-unit system

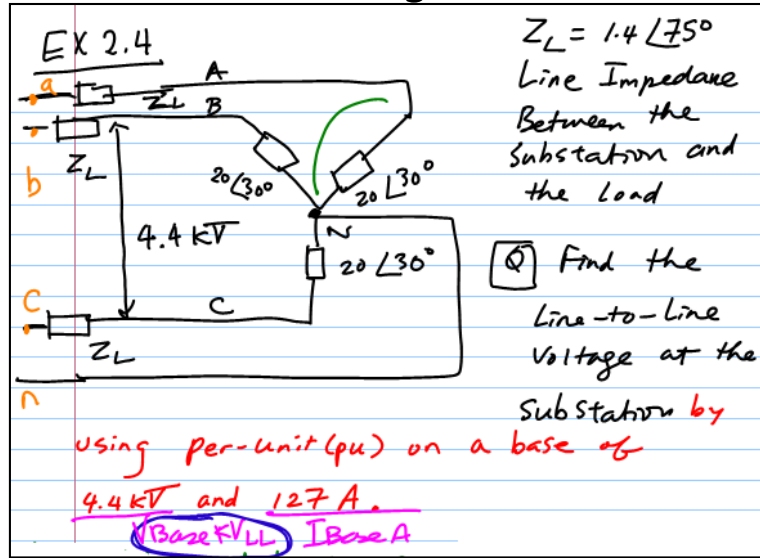

(Sol) We need to convert all into pu value.

$$Z_{Base} = \frac{V_{Base} V_{LN}}{I_{Base} A} = \frac{V_{Base} V_{LL} / \sqrt{3}}{I_{Base} A}$$

$$= \frac{4400 / \sqrt{3}}{127} = 20 \Omega$$

$$Z_{L \text{ pu}} = \frac{1.4 \angle 75^\circ}{20} = 0.07 \angle 75^\circ \text{ pu}$$

$$Z_{load \text{ pu}} = \frac{20 \angle 30^\circ}{20} = 1 \angle 30^\circ \text{ pu}$$

$$I_{\text{thru Load}} = \frac{V_{LN}}{Z_{Load}}, \rightarrow I_{\text{pu}} = \frac{V_{LN} \cdot \text{pu}}{Z_{\text{pu}}}$$

$$I_{Base} = \frac{V_{LN \text{ Base}}}{Z_{Base}} = \frac{4400 / \sqrt{3}}{20} = \frac{2540}{20} = 127$$

$$I_{\text{pu}} = \frac{1.0}{1 \angle 30^\circ} = 1 \angle 30^\circ \text{ pu}$$

$$V = 1.0 \text{ pu}$$

$$Z_{\text{pu}}$$


$$V_{AN \text{ pu}} = 1$$

$$V_{AN} = \frac{4.4 \text{ kV}}{\sqrt{3}}$$

$$V_{LN \text{ pu}} = \frac{4.4}{\sqrt{3}}$$

$$I_{\text{pu}} = \frac{V_{LN \text{ pu}}}{Z_{\text{pu}}} = \frac{1}{1 \angle 30^\circ}$$

Per-unit system

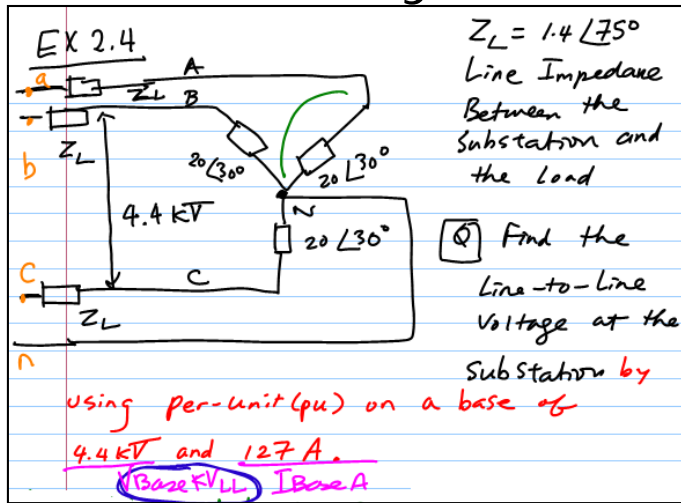

$$\vec{V}_{Substation} = \vec{I} \cdot Z_L + \vec{V}_{AN}$$

$$\begin{aligned}
 \vec{V}_{an\ pu} &= \vec{V}_{AN\ pu} + \vec{I}_{pu} \cdot Z_{L\ pu} \\
 &= 1.0 \angle 0^\circ + (1.0 \angle -30^\circ) (0.07 \angle 75^\circ) \\
 &= 1.0 \angle 0^\circ + 0.07 \angle 45^\circ \\
 &= 1.051 \angle 2.70^\circ \text{ pu}
 \end{aligned}$$

Actual Voltage?


$$\begin{aligned}
 V_{an} &= V_{an\ pu} \cdot V_{Base\ LN} \\
 &= 1.051 \cdot \left(\frac{4400}{\sqrt{3}} \right) = 2.67 \text{ kV}
 \end{aligned}$$

$$V_{LL} = V_{an\ pu} \cdot V_{Base\ LL}$$

$$= 1.051 \cdot (4400) = 4.62 \text{ kV}$$

$$\left(\frac{4400}{\sqrt{3}} \right) \sqrt{3} \xrightarrow{LN} LL$$

Example

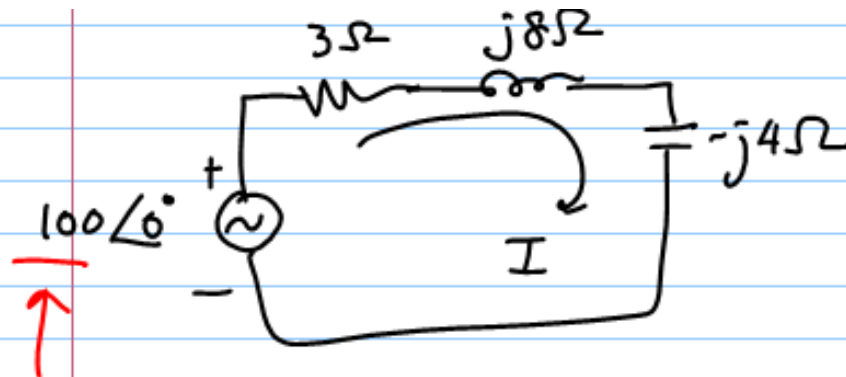

- ① Draw circuit Diagram in pu with $V_{base} = 100$ $S_{base} = 500$ VA
- ② Compute Series Impedance in pu
- ③ Compute the Current I in pu
- ④ Calculate the Complex Power (in pu) delivered to each of the 4 elements in the circuit

Example - Solution


Solution From $V_{base} = 100 \text{ V}$, $S_{base} = 500 \text{ VA}$

$$\rightarrow I_{base} = \frac{S_{base}}{V_{base}} = \frac{500}{100} = 5 \text{ A}$$

$$Z_{base} = \begin{cases} \frac{V_{base}}{I_{base}} = \frac{100}{5} = 20 \Omega \\ \frac{V_{base}^2}{S_{base}} = \frac{(100)^2}{500} = 20 \Omega \end{cases}$$

① ckt Diagram

<u>Actual</u>	<u>Base</u>	<u>pu</u>
$100 \angle 0^\circ$	100	$\frac{100 \angle 0^\circ}{100} \rightarrow 1 \angle 0^\circ \text{ pu}$
3Ω	20Ω	$\frac{3}{20} \rightarrow 0.15 \text{ pu}$
$j8 \Omega$	20Ω	$\frac{j8}{20} \rightarrow j0.4 \text{ pu}$
$-j4 \Omega$	20Ω	$\frac{-j4}{20} \rightarrow -j0.2 \text{ pu}$

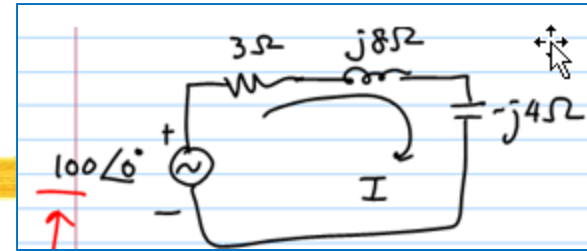

Example - Solution

Solution From $V_{base} = 100 \text{ V}$, $S_{base} = 500 \text{ VA}$



$$\rightarrow I_{base} = \frac{S_{base}}{V_{base}} = \frac{500}{100} = 5 \text{ A}$$

$$Z_{base} = \frac{V_{base}}{I_{base}} = \frac{100}{5} = 20 \Omega$$

$$\frac{V_{base}^2}{S_{base}} = \frac{(100)^2}{500} = 20 \Omega$$

① ckt Diagram

Actual	Base	pu
$100 \angle 0^\circ$	100	$\frac{100 \angle 0^\circ}{100} \rightarrow 1 \angle 0^\circ \text{ pu}$
3Ω	20Ω	$\frac{3}{20} \rightarrow 0.15 \text{ pu}$
$j8 \Omega$	20Ω	$\frac{j8}{20} \rightarrow j0.4 \text{ pu}$
$-j4 \Omega$	20Ω	$\frac{-j4}{20} \rightarrow -j0.2 \text{ pu}$

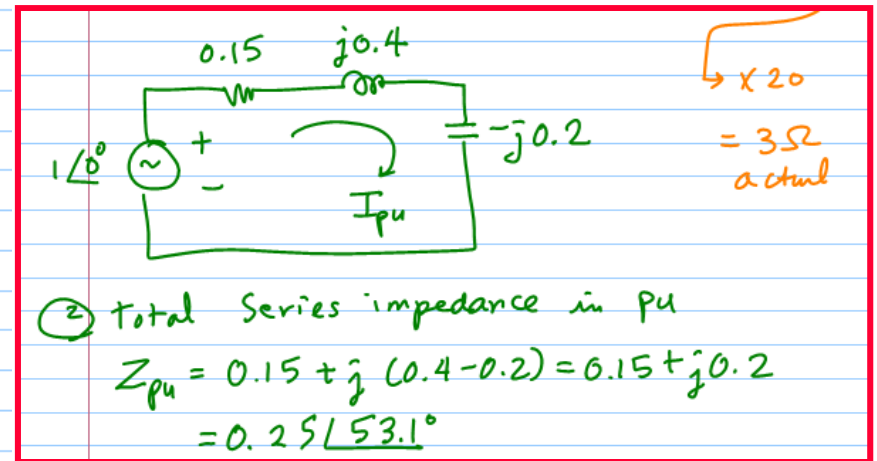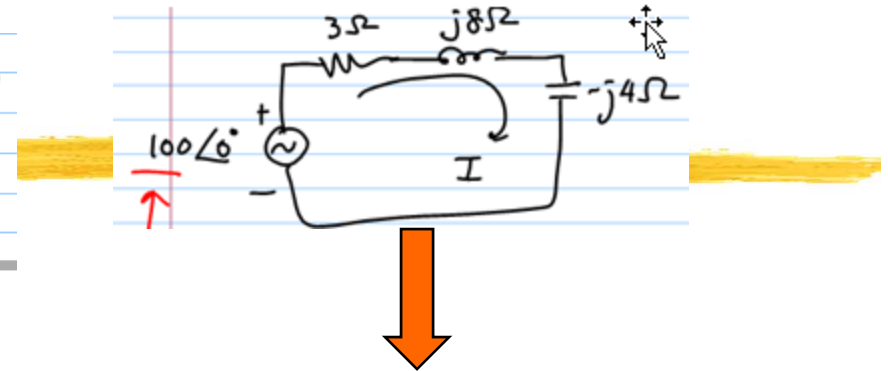

③ Current \bar{I}_{pu}

$$\bar{I}_{pu} = \frac{\bar{V}_{pu}}{Z_{pu}} = \frac{1.0 \angle 0^\circ}{0.25 \angle 53.1^\circ} = 4.0 \angle -53.1^\circ$$

↓ x 5
= 20 [A]
Actual

④ Complex Power in pu

$$\bar{S}_{R_{pu}} = \bar{I}_{pu}^2 R_{pu} = 4^2 \cdot (0.15) = 2.4 + j0$$

$$\bar{S}_{L_{pu}} = \bar{I}_{pu}^2 (jX_L) = 4^2 \cdot (j0.4) = 0 + j6.4$$

$$\bar{S}_{C_{pu}} = \bar{I}_{pu}^2 (-jX_C) = 4^2 \cdot (-j0.2) = 0 - j3.2$$


$$\bar{S}_{pu} = \bar{S}_{R_{pu}} + \bar{S}_{L_{pu}} + \bar{S}_{C_{pu}}$$

$$= 2.4 + j6.4 - j3.2$$

$$= 2.4 + j3.2$$

$$= 4.0 \angle 53.1^\circ \rightarrow \text{x 500} \rightarrow 2000 \text{ VA (actual)}$$

Example - Solution

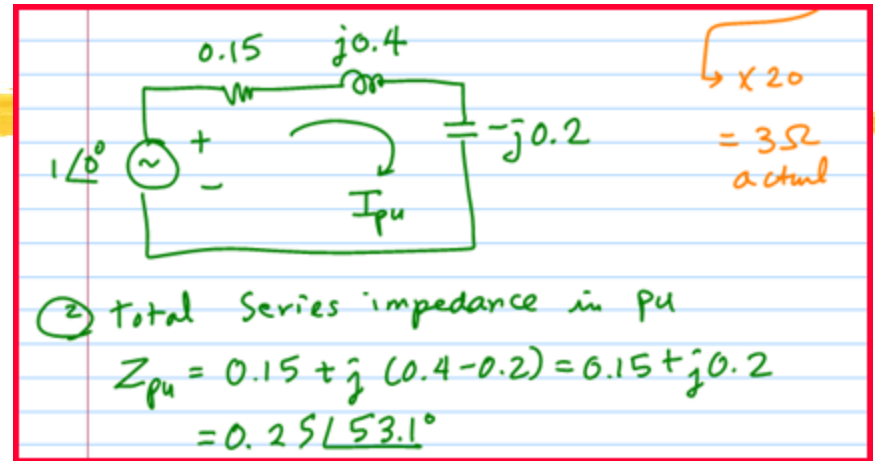

Example

A 2400-V 3 ϕ Source Supplies 2 parallel loads:

load 1 : 300 kVA pf = 0.8 lagging

load 2 : 240 kVA pf = 0.6 leading

If $V_{an} = 1386 \angle 0^\circ$ V, $S_{\text{base } 3\phi} = 300 \text{ kVA}$
and $V_{\text{base LL}} = 2.4 \text{ kV}$

① Draw a 1 ϕ equivalent circuit

② Determine all 3 source line currents

③ Find system bases for 1 ϕ equivalent circuit

④ Draw 1 ϕ equivalent circuit in pu

⑤ Determine source line current in pu

Sol


1 ϕ ; phase a

$$\textcircled{1} \bar{S}_{\text{load } 1 \text{ } 3\phi} = 300 \angle \cos^{-1} 0.8 \rightarrow S_{a_1} = \frac{1}{3} S_{\text{load } 1 \text{ } 3\phi}$$
$$\bar{S}_{\text{load } 2 \text{ } 3\phi} = 240 \angle \cos^{-1} 0.6 = 100 \angle \cos^{-1} 0.8 \text{ kVA}$$
$$\rightarrow S_{a_2} = 80 \angle \cos^{-1} 0.6 \text{ kVA}$$

$$\rightarrow \begin{cases} \bar{S}_{a_1} = 100 \angle 36.9^\circ \\ \bar{S}_{a_2} = 80 \angle -53.1^\circ \end{cases}$$

From $\bar{S} = \bar{V} \bar{I}^*$
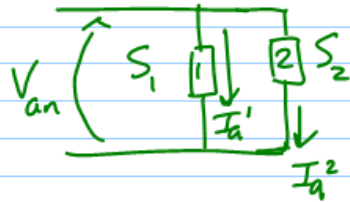
$$\bar{I}_{a_1} = \left[\frac{S_{a_1}}{V_{an}} \right]^*$$



Current through Load 1

$$= \left[\frac{100 \angle 36.9^\circ}{1.386 \angle 0^\circ} \right]^* = 72.2 \angle -36.9^\circ \text{ A}$$

$$\bar{I}_{a_2} = \left[\frac{S_{a_2}}{V_{an}} \right]^* = \left(\frac{80 \angle -53.1^\circ}{1.386 \angle 0^\circ} \right)^* = 57.7 \angle 53.1^\circ \text{ A}$$

load 1 : 300 kVA pf=0.8 lagging
load 2 : 240 kVA pf=0.6 leading

$$S_{\text{base } 3\phi} = 300 \text{ kVA}$$


$$V_{\text{base LL}} = 2.4 \text{ kV}$$


Load Impedance

$$Z_1 = \frac{\bar{V}_{an}}{\bar{I}_{a_1}} = \frac{1386 \angle 0^\circ}{72.2 \angle -36.9^\circ} = 19.2 \angle 36.9^\circ$$
$$= 15.36 + j11.52 \Omega$$

$$Z_2 = \frac{\bar{V}_{an}}{\bar{I}_{a_2}} = \frac{1386 \angle 0^\circ}{57.7 \angle 53.1^\circ} = 24 \angle -53.1^\circ$$
$$= 14.4 - j19.2 \Omega$$

Finally, we have 1 ϕ equivalent circuit.

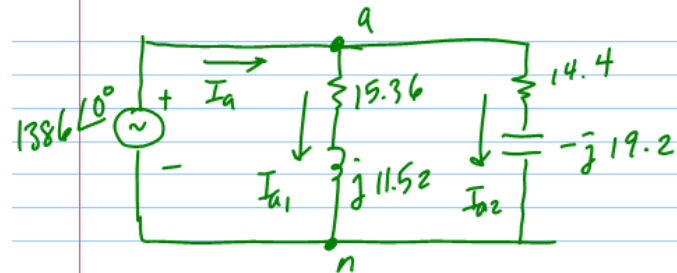

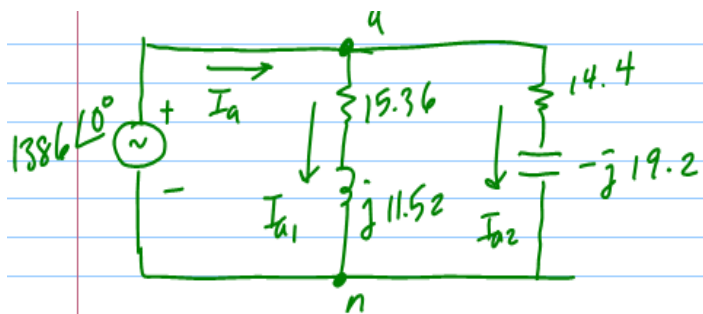

② Source Current \bar{I}_a

$$\begin{aligned}\bar{I}_a &= \bar{I}_{a1} + \bar{I}_{a2} = 72.2 \angle 36.9^\circ + 57.7 \angle 53.1^\circ \\ &= 57.7 - j43.3 + 34.6 + j46.2 \\ &= 92.3 + j2.9 \\ &= 92.4 \angle 1.8^\circ\end{aligned}$$

3 ϕ symmetry

$$\bar{I}_b = 92.4 \angle 1.8^\circ - 120^\circ = 92.4 \angle -118.2^\circ$$

$$\bar{I}_c = 92.4 \angle 1.8^\circ + 120^\circ = 92.4 \angle 121.8^\circ$$

③ System bases for 1 ϕ circuit

$$(S_{base\ 3\phi} = 300\text{ kVA} \ \& \ V_{base\ LL} = 2.4\text{ kV})$$

$$S_{base} = \frac{S_{base\ 3\phi}}{3} = 100\text{ kVA}$$

$$V_{base\ LN} = \frac{V_{base\ LL}}{\sqrt{3}} = \frac{2.4}{\sqrt{3}} = 1.386\text{ kV}$$

(default)

$$I_{base} = \frac{S_{base}}{V_{base}} = \frac{100}{1.386} = 72.2\text{ A}$$

$$Z_{base} = \frac{V_{base}}{I_{base}} = \frac{1386}{72.2} = 19.2\ \Omega$$


④ 1 ϕ equivalent circuit in pu.

$$Z_{a1\ pu} = \frac{19.2 \angle 36.9^\circ}{19.2} = 1 \angle 36.9^\circ = 0.8 + j0.6$$

$$Z_{a2\ pu} = \frac{24 \angle -53.1^\circ}{19.2} = 1.25 \angle -53.1^\circ = 0.75 - j1.0$$

$$V_{a\ pu} = \frac{1386 \angle 0^\circ}{1386} = 1 \angle 0^\circ$$

Example

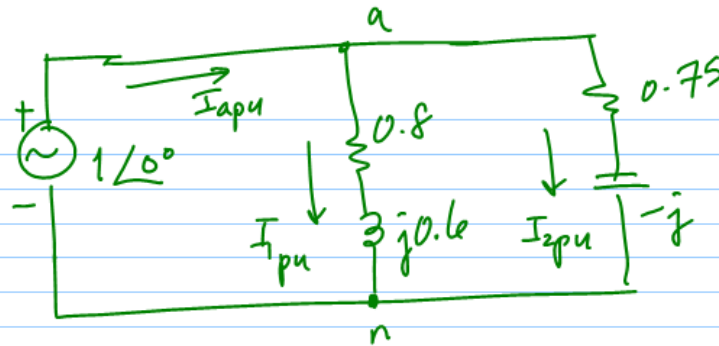

⑤ Source current $\bar{I}_{a pu}$

$$\begin{aligned}
 \bar{I}_{a pu} &= \bar{I}_{1 pu} + \bar{I}_{2 pu} \\
 &= \frac{1 \angle 0^\circ}{1 \angle 36.9^\circ} + \frac{1 \angle 0^\circ}{1.25 \angle -93.1^\circ} \\
 &= 1 \angle -36.9^\circ + 0.8 \angle 93.1^\circ \\
 &= 0.8 - j0.6 + 0.48 + j0.64 \\
 &= 1.28 + j0.04 \\
 &= \underline{1.28 \angle 1.8^\circ}
 \end{aligned}$$

cf. Actual Value? $\bar{I}_a = \bar{I}_{a pu} \cdot I_{base}$
 $= (1.28 \angle 1.8^\circ) (72.2) = 92.4 \angle 1.8^\circ$

Changing the Base of PU Quantities

* When making computations, all impedance in a system must be expressed on the same impedance base !!

→ Necessary to convert pu Z from one base to another.


Remember,

$$Z_{pu} = \frac{Z_{actual}}{Z_{base}} = \frac{Z_{actual}}{\left\{ \frac{(KV_{base})^2 \times 10^3}{KVA_{base}} \right\}}$$

$P = \frac{V^2}{R} \rightarrow R = \frac{V^2}{P}$

$$= \frac{(Z_{actual})(KVA_{base})}{(KV_{base})^2 (10^3)}$$

Alternatively

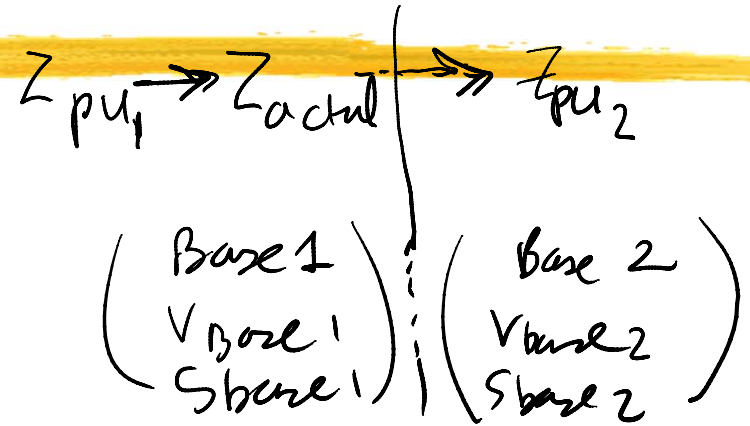

$$Z_{pu} \propto KVA_{base}$$

$$Z_{pu} \propto \frac{1}{(KV_{base})^2}$$


$$\rightarrow Z_{pu_{new}} = Z_{pu_{old}} \left(\frac{KV_{old}}{KV_{new}} \right)^2 \left(\frac{KVA_{new}}{KVA_{old}} \right)$$

EXAMPLE - Changing the Base of PU Quantities

The reactance a generator (X'')

$X''_{pu} = 0.25$ on generator's nameplate rating of 18 kV, 500 MVA.

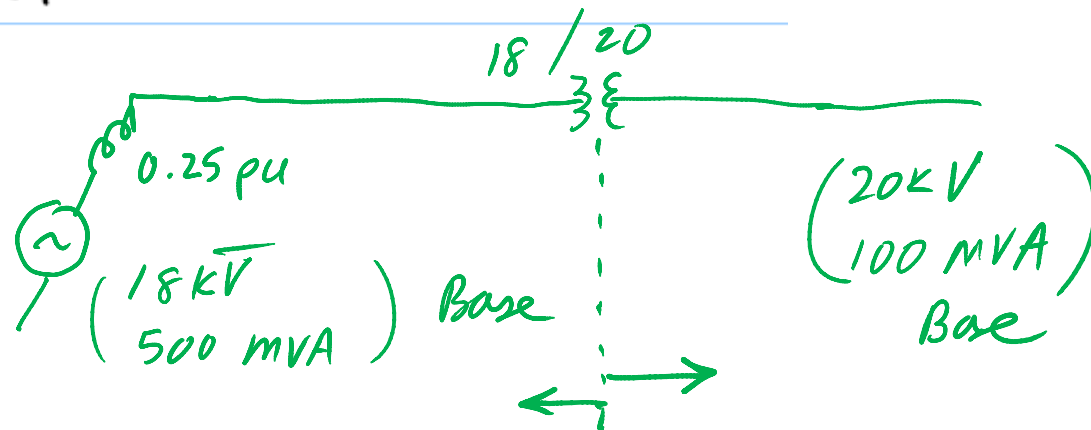Now, the base for circuit calculations is 20 kV, 100 MVA. Find X'' on the new base.



EXAMPLE - Changing the Base of PU Quantities

The reactance of a generator (X'')

$X''_{pu} = 0.25$ on generator's nameplate rating of 18 kV, 500 MVA.

Now, the base for circuit calculations is 20 kV, 100 MVA. Find X'' on the new base.

Alternatively,

① Find X'' in Ω from the old base.

$$\begin{aligned} X''_{\text{actual}} &= X''_{pu} \cdot \left(\frac{18^2}{500} \right) = (0.25) \left(\frac{18^2}{500} \right) \\ &= 0.162 (\Omega) \end{aligned}$$

← old Base

② Convert the Ω value into pu in the new base

$$\begin{aligned} X''_{pu} &= \frac{(0.162) \text{ actual}}{\left(\frac{20^2}{100} \right)} = \frac{(0.162)(100)}{20^2} \\ &= 0.0405 \text{ pu} \end{aligned}$$

new base

EXAMPLE - Changing the Base of PU Quantities


The reactance of a generator (X'')

$X''_{pu} = 0.25$ on generator's nameplate rating of 18 kV, 500 MVA.

Now, the base for circuit calculations is 20 kV, 100 MVA. Find X'' on the new base.

⌘ Using the formula
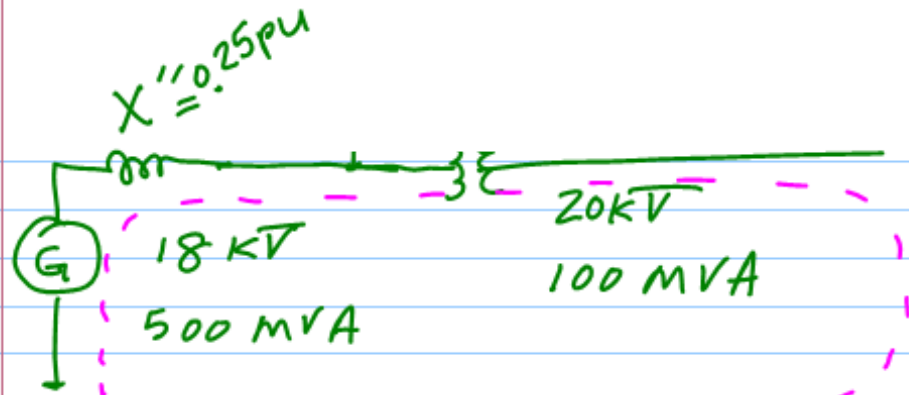
$$Z_{pu_{new}} = Z_{pu_{old}} \left(\frac{kV_{old}}{kV_{new}} \right)^2 \left(\frac{kVA_{new}}{kVA_{old}} \right)$$



$$X''_{pu_{new}} = (0.25) \left(\frac{18}{20} \right)^2 \left(\frac{100}{500} \right)$$
$$= 0.0405 pu$$