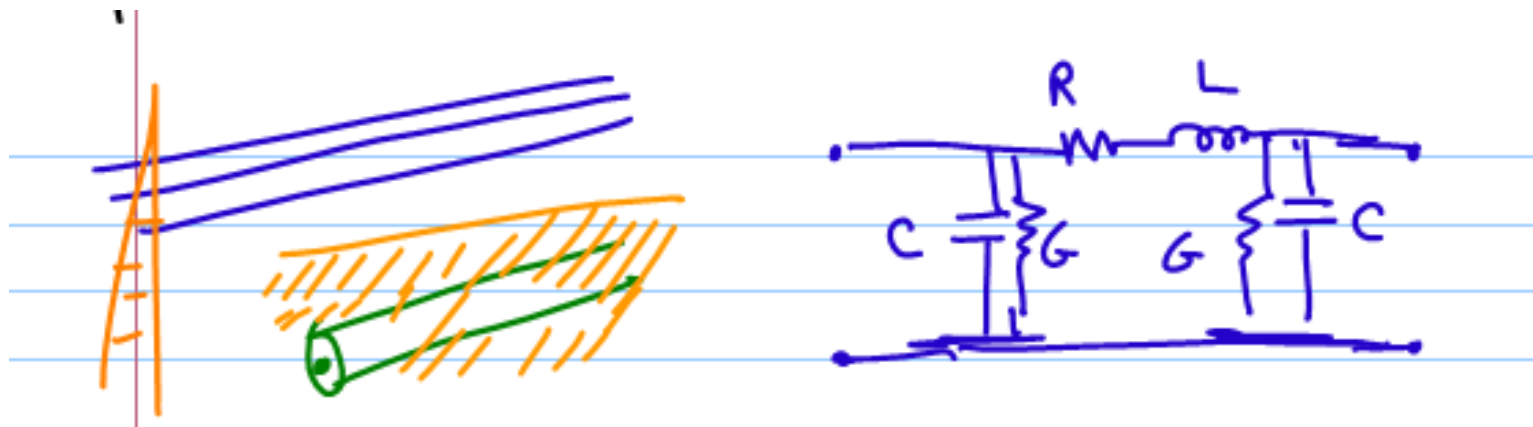


# EECE421 Power System Analysis

## ⌘ Chapter 5: Current and Voltage Relations on a Transmission Line



## Focus

- ⌘ Maintain voltage at various points within specified limits in the transmission system
- ⌘ Determination of  $V$ ,  $I$ , and  $S$  (P & Q) at any point on a transmission line with assumption that we know these ( $V$ ,  $I$ , and  $S$ ) at one point (usually at one end of the line)
- ⌘ Understand the effects of the parameters of the line on  $V$  and  $S$  flow
- ⌘ Understand transmission transient (due to surges caused by lightning and switching)

## 5.1 Representation of Lines

⌘ 3 classes by the length of the line

⊞ Short Line ( $L < 50$  miles):

⊞ lumped parameters with  $C$  ignored

⊞ Medium-length Line ( $50 < L < 150$  miles):


⊞ Lumped Parameters with  $C$  placed at both ends with amount of  $C/2$  each

⊞ Long Line ( $L > 150$  miles)

⊞ Distributed parameter approach

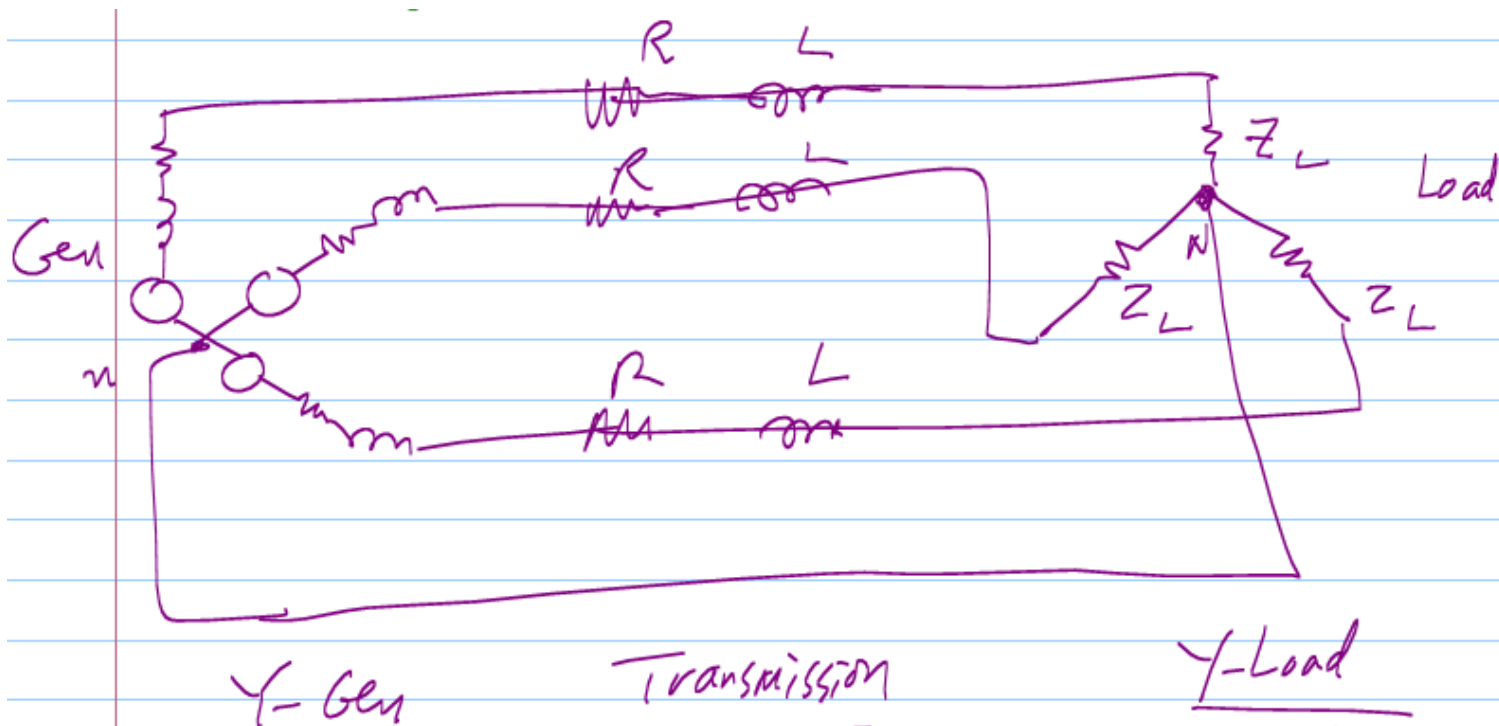
# Short Line - Lumped Parameter

- ⌘ R and L for the entire line ( of < 50 miles)
- ⌘ C ignored



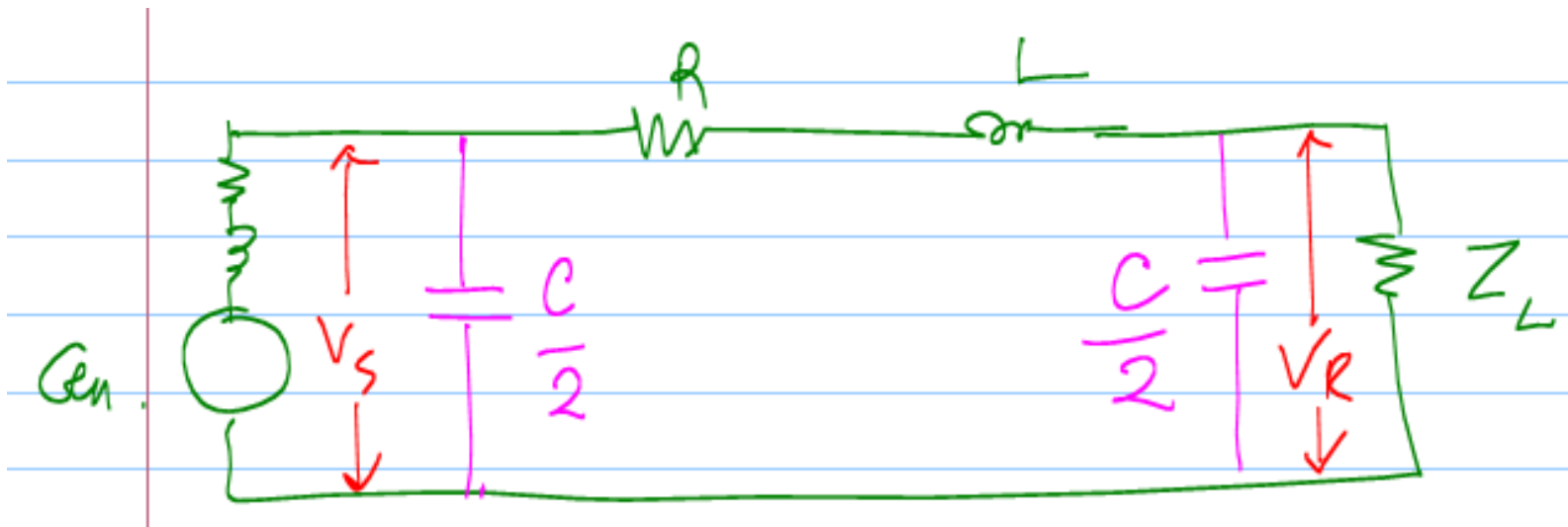
## Medium Line – Lumped Parameter

- ⌘ R and L for the entire line of [50, 150] miles
- ⌘  $C/2$  at both ends: C is the capacitance of the entire line




# Distributed Parameter – Long Line

(L > 150 miles)

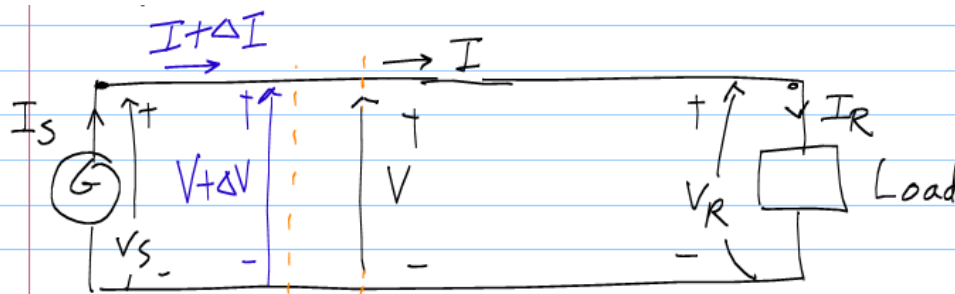

$x$   
distance from Receiving end.

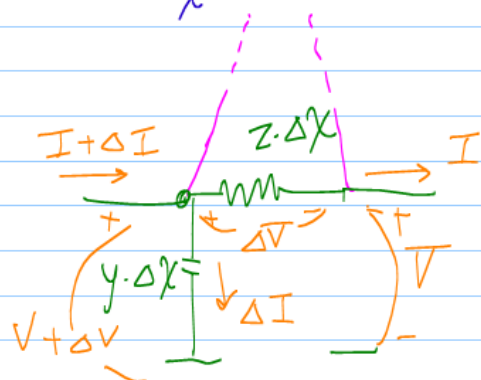

$z$ : series impedance per unit length =  $(r + j\omega L)$  per  $\Delta x$


$y$ : shunt admittance per unit length =

$l$ : length of line

$Z = z l$ : total series impedance per phase

$Y = y l$ : total shunt admittance per phase to neutral

# Short Transmission Line

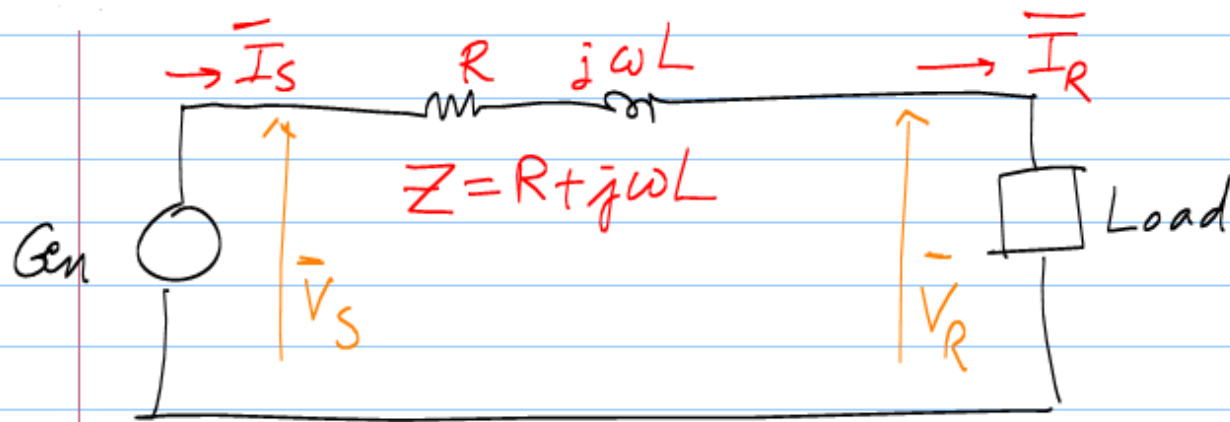


$$\vec{I}_R = \vec{I}_s$$

$$\vec{V}_s = \vec{V}_R + \vec{I}_R \vec{Z}$$

\* "Voltage Regulation"  
→ Rise in Voltage  
at the receiving end

→ Leading pf case!  
⇒ drop at R (losses)

# Voltage Regulation

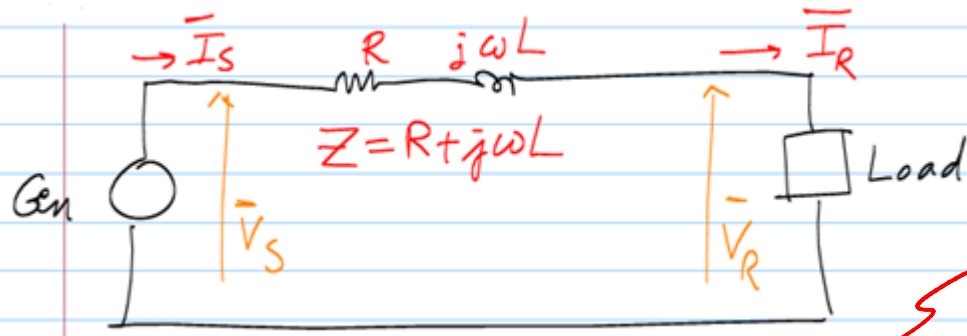

$$\% \text{ Voltage Regulation} = \frac{|V_R, \text{ No Load}| - |V_R, \text{ Full Load}|}{|V_R, \text{ Full Load}|} \times 100$$

Above circuit


(with  $|V_s|$  kept constant)

$|V_R| = |V_R, \text{ Full Load}|$  with Load Connected

$|V_s| = |V_R, \text{ No Load}|$  w/o Load Connected



# Voltage Regulation

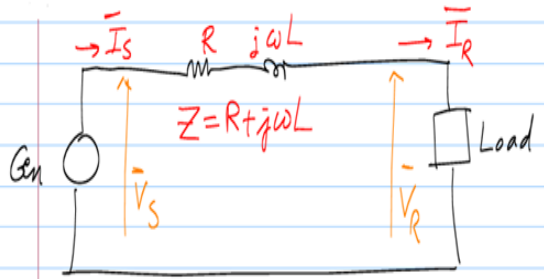


Let's draw a phasor diagram with the same  $|V_R|$  but different Load current (leading or lagging)


$$\vec{V}_s = \vec{V}_R + \vec{I} \cdot \vec{Z} = \vec{V}_R + \vec{I}_R (R + jX_L)$$

$$= \vec{V}_R + \vec{I}_R R + jX_L \vec{I}_R$$
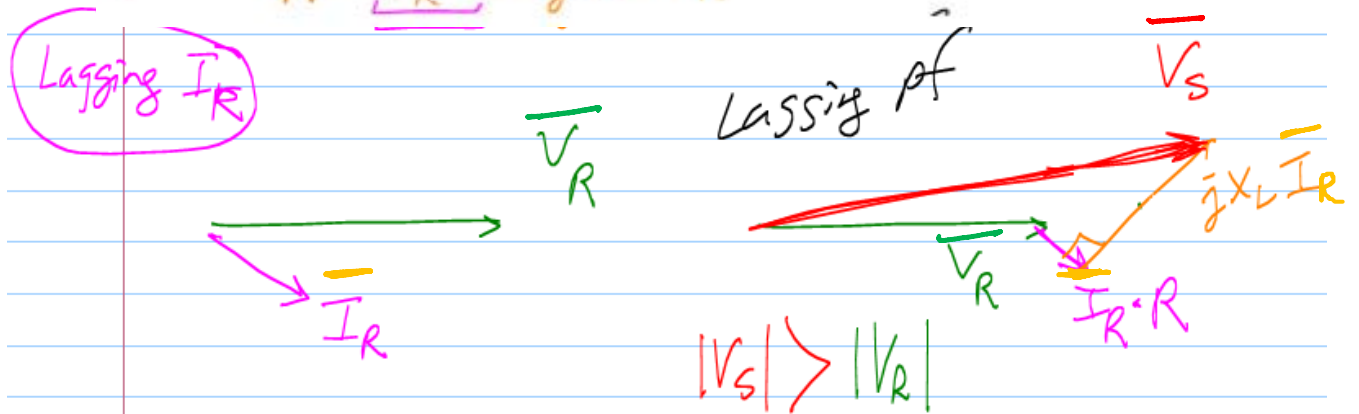
$$\vec{I}_R = \frac{\vec{V}_R}{Z_{Load}}$$




# Voltage Regulation

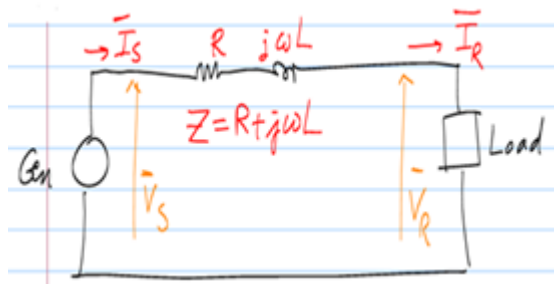

$$\vec{V}_s = \vec{V}_R + \vec{I} \cdot \vec{Z} = \vec{V}_R + \vec{I}_R (R + jX_L)$$

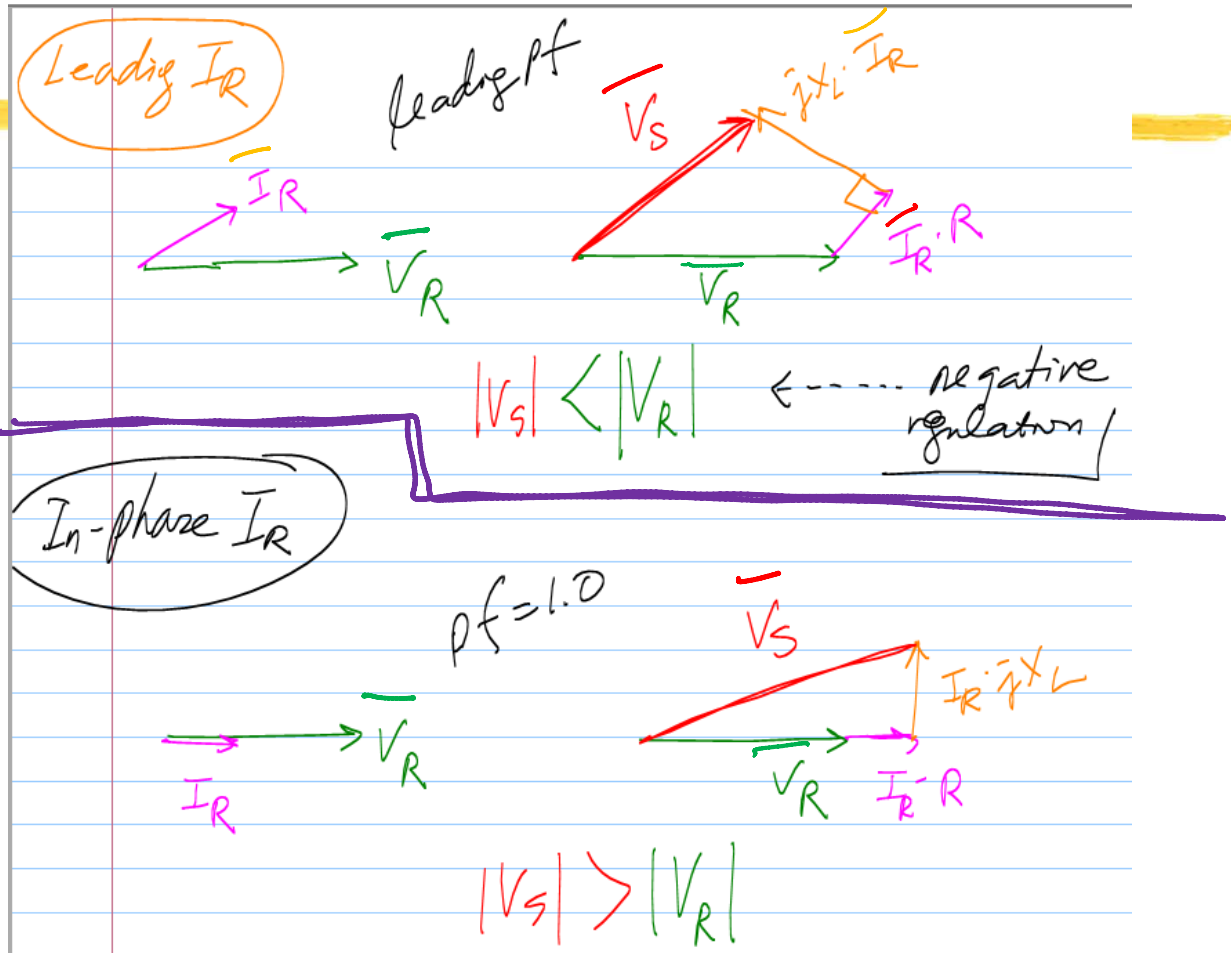
$$= \vec{V}_R + \vec{I}_R R + jX_L \vec{I}_R$$



## Class Activity

- ⌘ For a 12 mile long 60Hz single circuit 3-phase line is made of an unknown conductor. The line delivers 2500kW at 11,000 V to a 3-phase balanced load. We assume the receiving side voltage is kept the same. If the load is maintained a unity power factor, the sending-end line voltage is 12,081 V; however, when the load is of 0.8 lagging power factor, the sending end line voltage is changed to 13,268 V. Find the impedance of the conductor per mile.
- ⌘ Hint: Per-phase analysis and Line-to-neutral voltage


# Transmission Line Equation

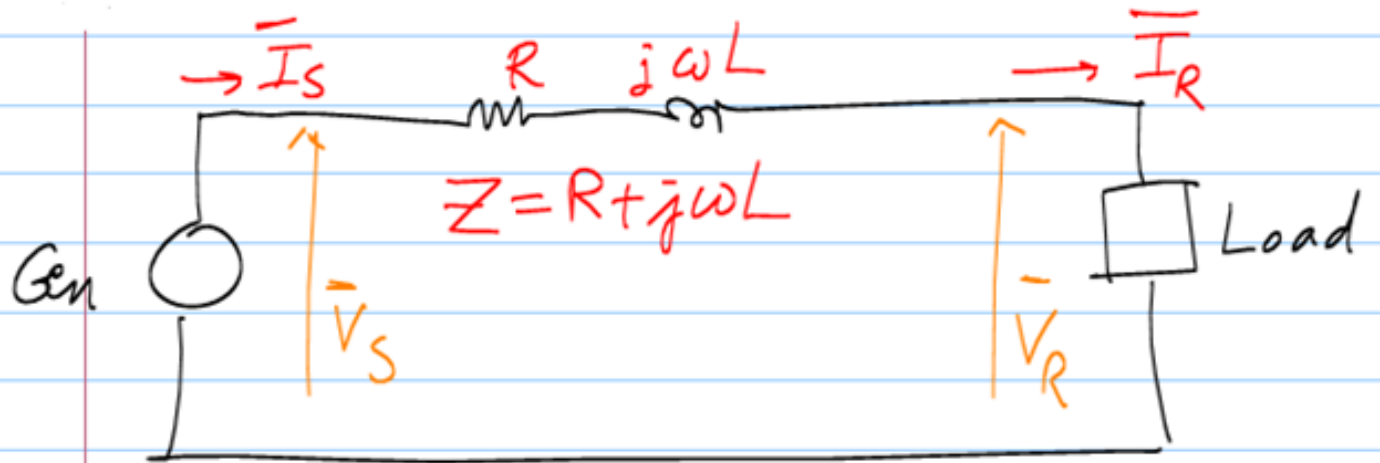

$$\vec{I}_R = \vec{I}_s$$

$$\vec{V}_s = \vec{V}_R + \vec{I}_R \vec{Z}$$

# Transmission Line Equation

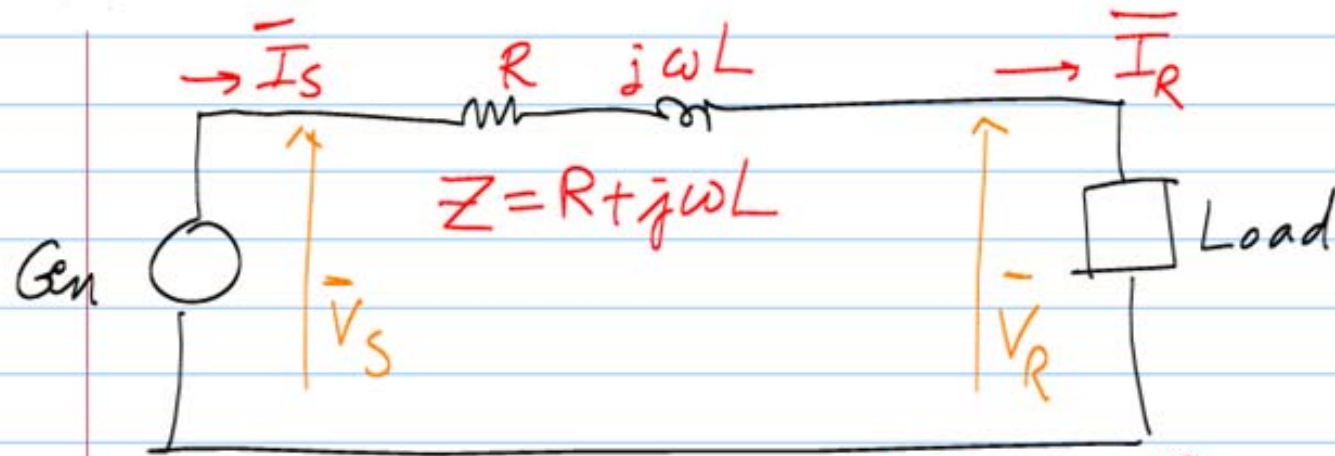


$$\vec{I}_R = \vec{I}_s$$

$$\vec{V}_s = \vec{V}_R + \vec{I}_R \vec{Z}$$

$$\vec{V}_s = \underbrace{1}_{(A)} \cdot \underbrace{\vec{V}_R}_{(C)} + \underbrace{\vec{Z}}_{(B)} \cdot \underbrace{\vec{I}_R}_{(D)}$$
$$\vec{I}_s = \underbrace{0}_{(C)} \cdot \underbrace{\vec{V}_R}_{(D)} + \underbrace{1}_{(D)} \cdot \underbrace{\vec{I}_R}_{(R)}$$

$$A = D = 1, \quad B = \vec{Z}, \quad C = 0$$

# Medium-Length Line ( $\pi$ -circuit)

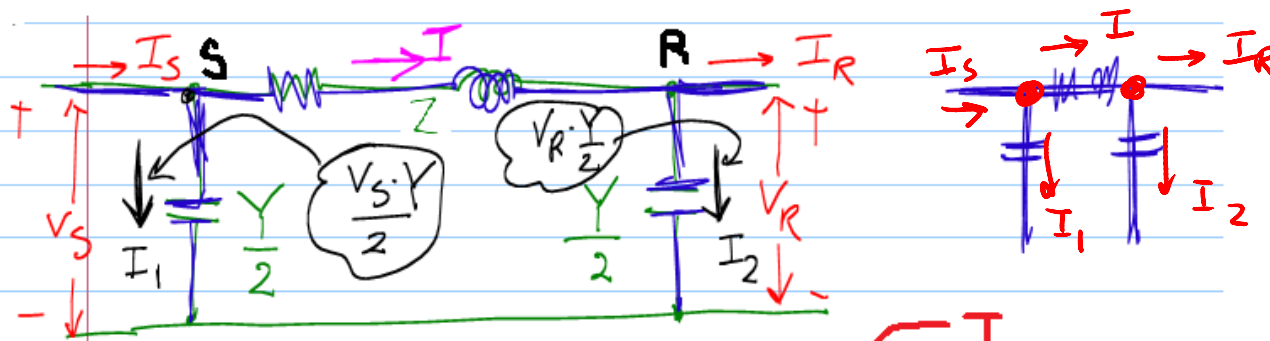

@ S:  $V_S = I \cdot Z + V_R = (I_R + \underbrace{V_R \cdot \frac{Y}{2}}_{I_2}) Z + \underline{V_R}$

@ R:  $\underline{I} = I_R + \underline{I_2} = I_R + \underline{V_R \cdot \frac{Y}{2}}$

$$\underline{V_S} = \left( \frac{ZY}{2} + 1 \right) \underline{V_R} + Z \cdot \underline{I_R}$$

# Medium-Length Line ( $\pi$ -circuit)

$$I_S = I + V_S \cdot \frac{Y}{2}$$

$$I = I_R + V_R \cdot \frac{Y}{2}$$

$$I_S = I_R + V_R \cdot \frac{Y}{2} + V_S \cdot \frac{Y}{2}$$


$$= V_S \cdot \frac{Y}{2} + V_R \cdot \frac{Y}{2} + I_R$$

$$V_S = \left( \frac{ZY}{2} + 1 \right) V_R + Z \cdot I_R$$


$$= \left[ \left( \frac{ZY}{2} + 1 \right) V_R + Z \cdot I_R \right] \cdot \frac{Y}{2} + \frac{Y}{2} V_R + I_R$$

$$= \left[ \frac{ZY^2}{4} + \frac{Y}{2} + \frac{Y}{2} \right] V_R + \left( \frac{ZY}{2} + 1 \right) I_R$$
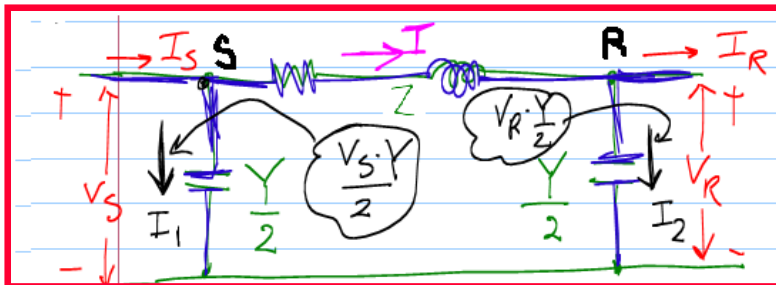
$$= Y \left( \frac{ZY}{4} + 1 \right) V_R + \left( \frac{ZY}{2} + 1 \right) I_R$$



# Medium-Length Line ( $\pi$ -circuit)

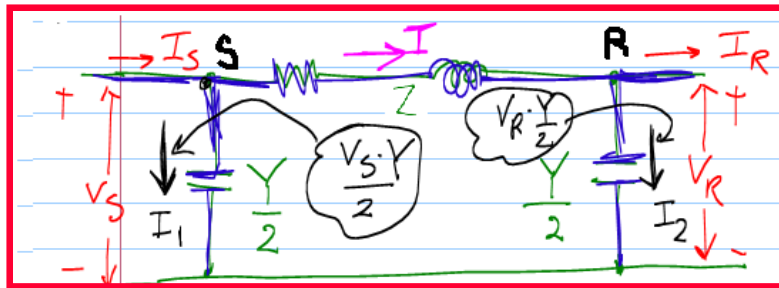

$$V_S = \underbrace{\left(\frac{ZY}{2} + 1\right)}_A V_R + \underbrace{Z}_{B} \cdot I_R$$

$$I_S = \underbrace{Y\left(\frac{ZY}{4} + 1\right)}_C V_R + \underbrace{\left(\frac{ZY}{2} + 1\right)}_D \cdot I_R$$

$$\rightarrow \begin{cases} V_S = A \cdot V_R + B \cdot I_R \\ I_S = C \cdot V_R + D \cdot I_R \end{cases} \begin{cases} A = D = \frac{ZY}{2} + 1 \quad [V/V] \\ B = Z \quad [\Omega] \\ C = Y\left(1 + \frac{ZY}{4}\right) \quad [S] \end{cases}$$

ABCD Constants: "generalized  
Circuit Constants"

①  $I_R = 0$   
: Open circuit (no load)

$$A = \frac{V_S}{V_R} \quad (\text{with } I_R = 0)$$

②  $V_R = 0$   
: Short circuit

$$B = \frac{I_S}{I_R} \quad (\text{with } V_R = 0)$$



# Medium-Length Line ( $\pi$ -circuit)

①  $I_R = 0$   
: Open circuit (no load)  
 $A = \frac{V_S}{V_R}$  (with  $I_R = 0$ )

②  $V_R = 0$   
: Short circuit  
 $B = \frac{I_S}{I_R}$  (with  $V_R = 0$ )


$$\frac{|V_S|}{|A|}$$

$$\% \text{ Voltage Regulation} = \frac{|V_{R, \text{No Load}}| - |V_{R, \text{Full Load}}|}{|V_{R, \text{Full Load}}|} \times 100$$


$$= \frac{\frac{|V_S|}{|A|} - |V_R|}{|V_R|} \times 100$$
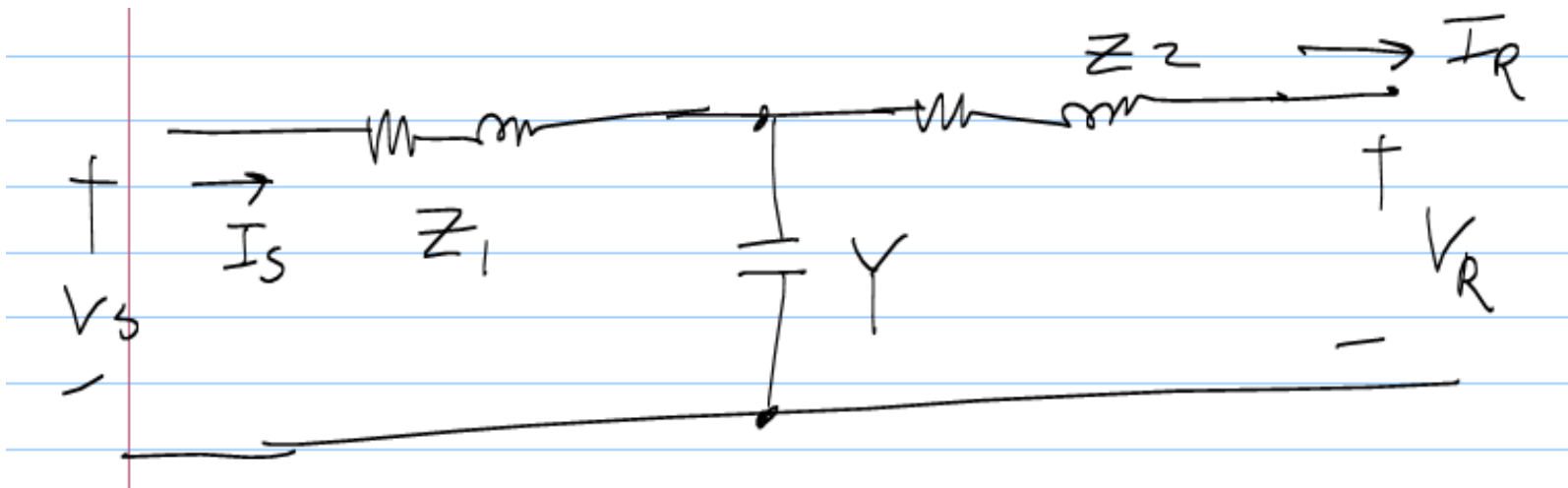
# Class Activity: ABCD-1

⌘ Find the ABCD constants for the following circuit




# ABCD constants for various circuits

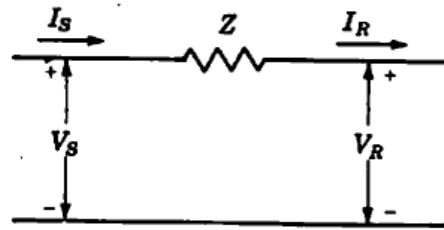


Series impedance
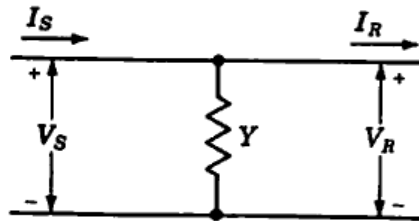
$$\begin{aligned} A &= 1 \\ B &= Z \\ C &= 0 \\ D &= 1 \end{aligned}$$



Shunt admittance

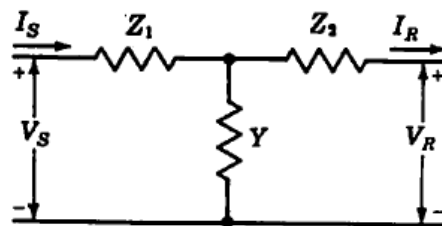
$$\begin{aligned} A &= 1 \\ B &= 0 \\ C &= Y \\ D &= 1 \end{aligned}$$




Unsymmetrical T

$$\begin{aligned} A &= 1 + YZ_1 \\ B &= Z_1 + Z_2 + YZ_1Z_2 \\ C &= Y \\ D &= 1 + YZ_2 \end{aligned}$$


# ABCD constants for various circuits

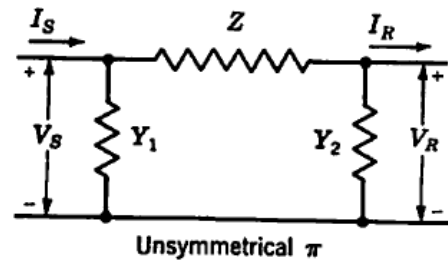
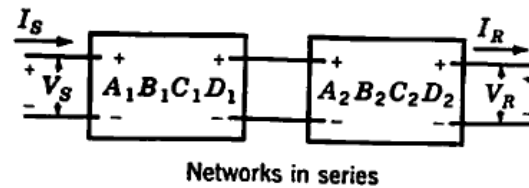
$$\begin{aligned} A &= 1 + Y_2 Z \\ B &= Z \\ C &= Y_1 + Y_2 + Z Y_1 Y_2 \\ D &= 1 + Y_1 Z \end{aligned}$$


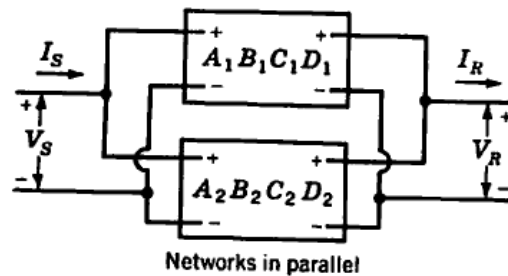
$$\begin{aligned} A &= A_1 A_2 + B_1 C_2 \\ B &= A_1 B_2 + B_1 D_2 \\ C &= A_2 C_1 + C_2 D_1 \\ D &= B_2 C_1 + D_1 D_2 \end{aligned}$$



$$\begin{aligned} A &= (A_1 B_2 + A_2 B_1) / (B_1 + B_2) \\ B &= B_1 B_2 / (B_1 + B_2) \\ C &= C_1 + C_2 + (A_1 - A_2)(D_2 - D_1) / (B_1 + B_2) \\ D &= (B_2 D_1 + B_1 D_2) / (B_1 + B_2) \end{aligned}$$


# HW #4

A 100-mile, single-circuit, 3-phase transmission line delivers 55MVA at 0.8 power factor lagging to the load at 132 kV (Line-to-line). The line is composed of Drake conductors (with Resistance per mile = 0.1284, and  $D_s=0.0373$  ft) with flat horizontal spacing of 11.9 ft between adjacent conductors.



Determine

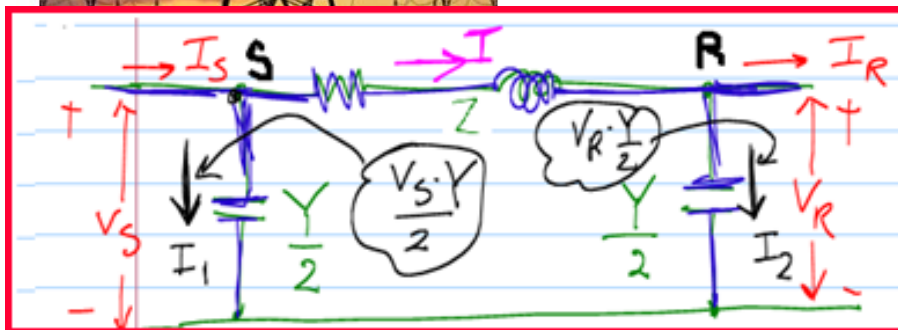- the series impedance ( $Z=R+jXL$ ) and the shunt admittance ( $Y=1/jXC$ ) of the line.
- the ABCD constants of the line.
- the sending-end voltage, current, real and reactive power, and the power factor.
- the percent regulation of the line.




$$V_S = \left( \frac{ZY}{2} + 1 \right) V_R + \frac{B}{Z} \cdot I_R$$

$$I_S = Y \left( \frac{ZY}{4} + 1 \right) V_R + \left( \frac{ZY}{2} + 1 \right) \cdot I_R$$


C D

# HW#4 - hint

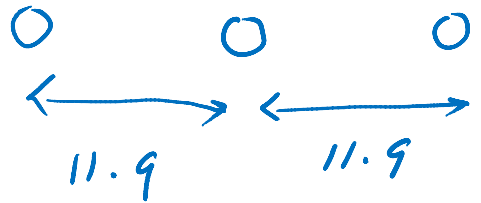

$$D_s = r' = 0.0373 \text{ (GMR)}$$

$$r = \frac{D_s}{0.7788}$$

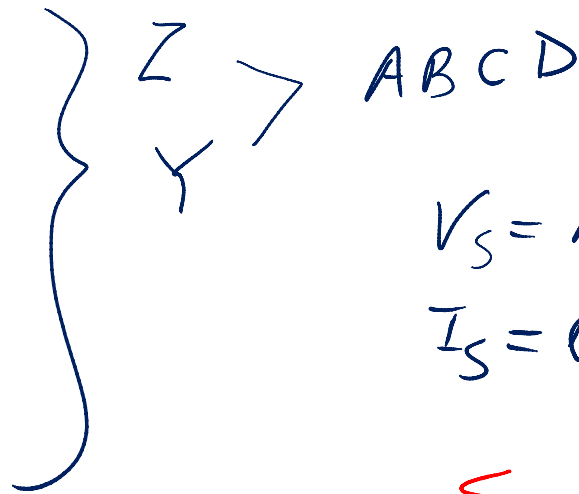

ABCD

$$V_S = A \cdot V_R + B \cdot I_R$$


$$I_S = C \cdot V_R + D \cdot \underline{I_R}$$

$$S_{3\phi} \rightarrow S_{1\phi} \quad V_R = |V_R| \angle 0^\circ$$


$$S_R = \overline{V_R} \overline{I_R}^* \quad P_R = |V_R| |I_R| \underbrace{\cos \theta}_{\text{pf}}$$
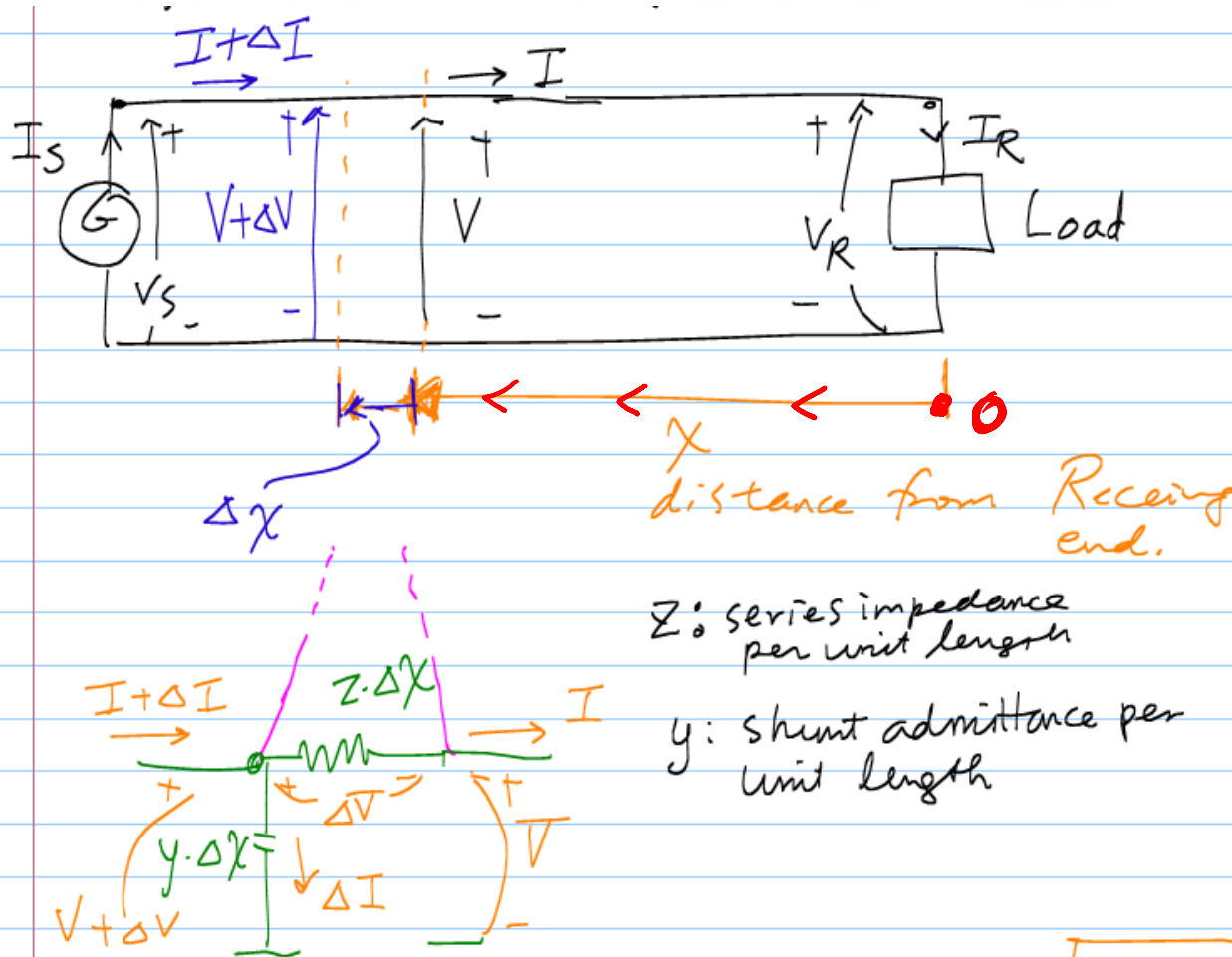
# Long Transmission Line (> 150 miles)

- ⌘ The parameters are not lumped but are distributed uniformly throughout the length of the line



# Long Transmission Line (> 150 miles)

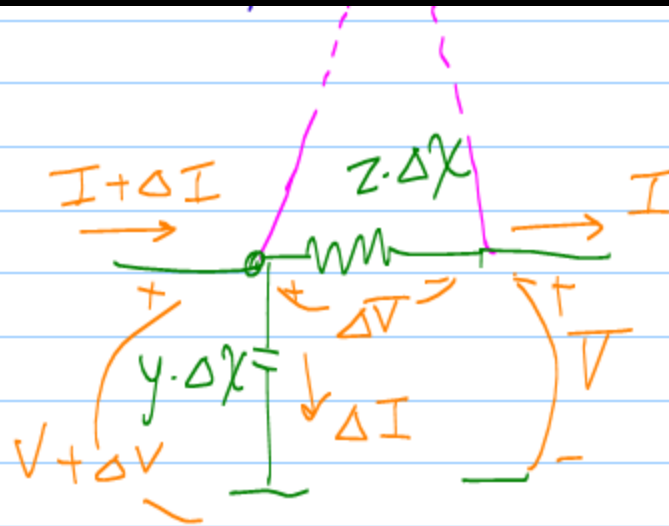

$Z$ : series impedance per unit length

$y$ : shunt admittance per unit length

$$\textcircled{1} \quad \Delta V = I \cdot z \cdot \Delta x \quad \longrightarrow \quad \frac{\Delta V}{\Delta x} = I \cdot z \quad \xrightarrow{\Delta x \rightarrow 0} \quad \boxed{\frac{dV}{dx} = I \cdot z}$$

$$\textcircled{2} \quad \Delta I = (V + \Delta V) (y \cdot \Delta x) \quad \longrightarrow \quad \frac{\Delta I}{\Delta x} = y (V + \Delta V) \quad \xrightarrow[\Delta V \rightarrow 0]{\Delta x \rightarrow 0} \quad \boxed{\frac{dI}{dx} = yV}$$



# Long Transmission Line (> 150 miles)

$$\frac{dV}{dx} = Iz \quad \& \quad \frac{dI}{dx} = yV$$

$\downarrow \left(\frac{d}{dx}\right)$

$$\frac{d^2V}{dx^2} = z \frac{dI}{dx}$$
$$\frac{d^2I}{dx^2} = y \frac{dV}{dx}$$

$\frac{d^2V}{dx^2} = zyV$

function of  $(V, x)$

$\frac{d^2I}{dx^2} = yzI$

function of  $(I, x)$

$$\frac{d^2V}{dx^2} = yzV \rightarrow \text{Solution Form?} : (\text{double derivative} \approx \text{itself})? \\ \text{exp function.}$$

$$\downarrow V = A_1 e^{\sqrt{yz} \cdot x} + A_2 e^{-\sqrt{yz} \cdot x} \quad (\text{A form of solution})$$

$$\downarrow \text{Take the second derivative:} \\ \left( \frac{d^2V}{dx^2} = yzV \right)$$

$$\frac{dV}{dx} = A_1 \sqrt{yz} e^{\sqrt{yz} \cdot x} - A_2 \sqrt{yz} e^{-\sqrt{yz} \cdot x}$$

$$\frac{d^2V}{dx^2} = A_1 yz e^{\sqrt{yz} \cdot x} + A_2 yz e^{-\sqrt{yz} \cdot x} \\ = yz (A_1 e^{\sqrt{yz} \cdot x} + A_2 e^{-\sqrt{yz} \cdot x})$$

✓ ← indeed, the solution for V.

# Long Transmission Line (> 150 miles)

From

$$\frac{dV}{dx} = IZ$$

$$(A_1 e^{\sqrt{yz} \cdot x} + A_2 e^{-\sqrt{yz} \cdot x})$$

$$IZ = A_1 \sqrt{yz} e^{\sqrt{yz} \cdot x} - A_2 \sqrt{yz} e^{-\sqrt{yz} \cdot x}$$

$$I = A_1 \sqrt{\frac{y}{z}} e^{\sqrt{yz} \cdot x} - A_2 \sqrt{\frac{y}{z}} e^{-\sqrt{yz} \cdot x}$$

$$= A_1 \frac{1}{\sqrt{z/y}} e^{\sqrt{yz} \cdot x} - A_2 \frac{1}{\sqrt{z/y}} e^{-\sqrt{yz} \cdot x}$$

$\swarrow$   $Z_c$

# Long Transmission Line (> 150 miles)

Q? How do find  $A_1$  and  $A_2$ ?

A Evaluation of  $V$  and  $I$  at the Receiving end (where  $x=0, V=V_R, I=I_R$ )

$$V = A_1 e^{\sqrt{yz} \cdot x} + A_2 e^{-\sqrt{yz} \cdot x}$$

$$I = A_1 \frac{1}{\sqrt{z/y}} e^{\sqrt{yz} \cdot x} - A_2 \frac{1}{\sqrt{z/y}} e^{-\sqrt{yz} \cdot x}$$

$$V(x=0) = V_R = A_1 + A_2$$

$$I(x=0) = I_R = \frac{1}{\sqrt{z/y}} (A_1 - A_2)$$

$$A_1 + A_2 = V_R$$

$$A_1 - A_2 = Z_c \cdot I_R$$

$$Z_c = \sqrt{\frac{z}{y}}$$

characteristic impedance,  
a complex number

# Long Transmission Line (> 150 miles)

$$2A_1 = V_R + I_R \cdot Z_C \longrightarrow A_1 = \frac{V_R + I_R \cdot Z_C}{2}$$

$$A_2 = V_R - A_1 = \frac{2V_R}{2} - \frac{V_R + I_R \cdot Z_C}{2} = \frac{V_R - I_R \cdot Z_C}{2}$$

Finally,  $\gamma = \sqrt{yz}$  ← "propagation constant" *complex number*

$$\left\{ \begin{aligned} V(x) &= \frac{V_R + I_R \cdot Z_C}{2} e^{\gamma x} + \frac{V_R - I_R \cdot Z_C}{2} e^{-\gamma x} \\ I(x) &= \frac{V_R / Z_C + I_R}{2} e^{\gamma x} - \frac{V_R / Z_C - I_R}{2} e^{-\gamma x} \end{aligned} \right\}$$

## Line (> 150 miles)

$$V(x) = \frac{V_R + I_R \cdot Z_c}{2} e^{\gamma x} + \frac{V_R - I_R Z_c}{2} e^{-\gamma x}$$

$$I(x) = \frac{V_R/Z_c + I_R}{2} e^{\gamma x} - \frac{V_R/Z_c - I_R}{2} e^{-\gamma x}$$

$\gamma$ : propagation constant ( $= \sqrt{yz}$ ), Complex

$Z_c$ : characteristic impedance ( $= \sqrt{z/y}$ ), Complex

$$e^{\alpha x}$$

$$e^{j\beta x} = \cos \beta x + j \sin \beta x = \angle \beta$$

$\gamma = \alpha + j\beta$  ← phase constant  
[radian per unit length]

↑  
attenuation constant [Neper per unit length]

$$V(x) = \frac{V_R + I_R \cdot Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

$$I(x) = \frac{V_R/Z_c + I_R}{2} e^{\alpha x} e^{j\beta x} - \frac{V_R/Z_c - I_R}{2} e^{-\alpha x} e^{-j\beta x}$$

## Long Transmission Line (> 150 miles)

$$V(x) = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

# Long Transmission Line (> 150 miles)

$$V(x) = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

$S \leftarrow$   $R$

<p>increases in mag. &amp;  <u>advances in phase</u>  as distance from  Receiver (i.e., <math>x</math>)  increases</p>	<p>diminishes in mag. &amp;  <u>retards in phase</u>  as the distance <math>x</math>  from receiver (<math>x</math>)  increases</p>
--	---




$$V(x) = \frac{V_R + I_R Z_0}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_0}{2} e^{-\alpha x} e^{-j\beta x}$$

$\leftarrow$  S  
 R  
 increases in mag. & advances in phase as distance from Receiver (i.e.,  $x$ ) increases

diminishes in mag. & retards in phase as the distance  $\leftarrow$  S from Receiver ( $x$ ) increases

diminished as it moves from the sending end toward receiving end.

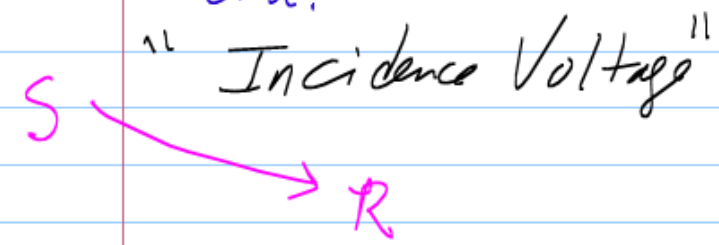diminishes as it moves toward the sending end from the Receiver end  
 "Reflected Voltage"



## Long Transmission Line (> 150 miles)

$$V(x) = \frac{V_R + I_R Z_0}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_0}{2} e^{-\alpha x} e^{-j\beta x}$$

$$V(x) = \text{Incidence Voltage}(x) + \text{Reflected Voltage}(x)$$

Similarly,

$$I(x) = \frac{V_R/Z_0 + I_R}{2} e^{\alpha x} e^{j\beta x} - \frac{V_R/Z_0 - I_R}{2} e^{-\alpha x} e^{-j\beta x}$$

$$I(x) = \text{Incident Current}(x) + \text{Reflected Current}(x)$$

# Long Transmission Line (> 150 miles)

## ⌘ Example

- ☒ 230 mile long line
- ☒  $z=0.1603+j0.8277$
- ☒  $y= j5.105 \times 10^{-6}$

$$\gamma := \sqrt{z \cdot y} = 1.981 \times 10^{-4} + 2.065i \times 10^{-3}$$

$$Z_c := \sqrt{\frac{z}{y}} = 404.526 - 38.812i$$

$$V_R := 124130$$

$$I_R := 335.7$$

$$|Z_c| = 406.384 \quad \arg(Z_c) = -0.096$$

$Z_{load} = \text{Resistance of } \frac{V_R}{I_R}$

$$\Delta L := \frac{L}{100} = 2.3$$



$$x := 0 .. 100$$

$$V_{inc_x} := \frac{V_R + I_R \cdot Z_c}{2} \cdot e^{\gamma x \cdot \Delta L}$$

$$V_{ref_x} := \frac{V_R - I_R \cdot Z_c}{2} \cdot e^{-\gamma x \cdot \Delta L}$$


$$V_x := V_{inc_x} + V_{ref_x}$$

# Long Transmission Line (> 150 miles)

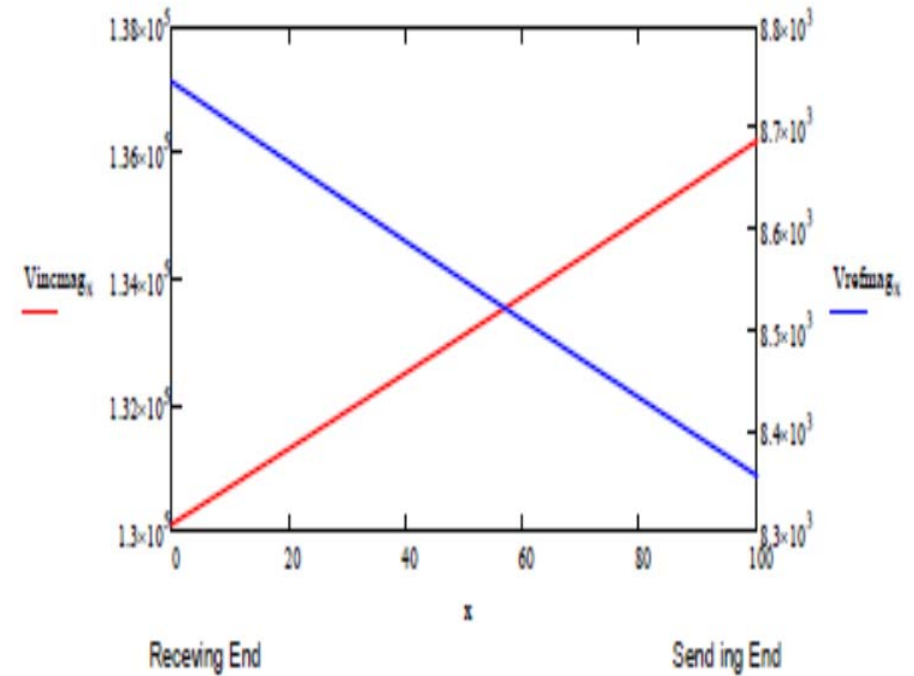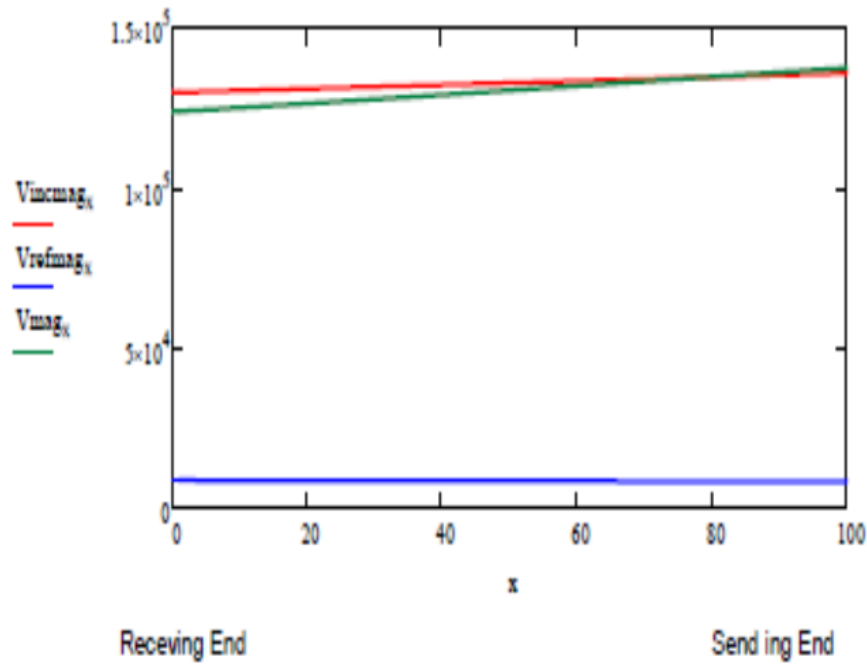
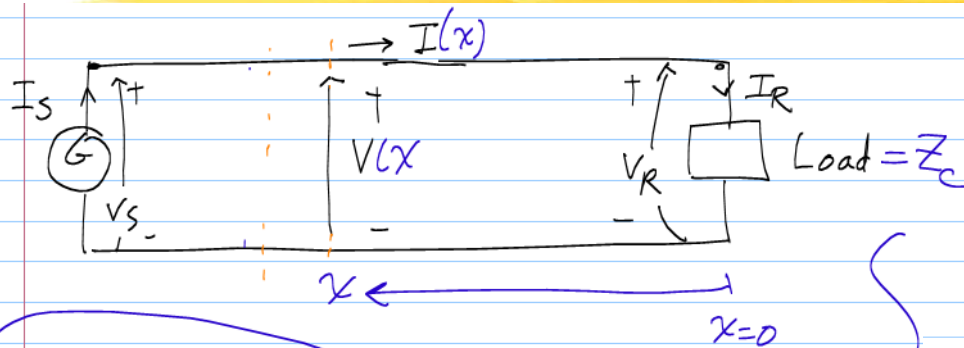
# Flat Line or "Infinite Line"

⌘ Load at the receiver side =  $Z_c$  (Characteristic Impedance) case



$$\rightarrow V_R = I_R \cdot Z_c$$

$$V(x) = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

No Reflected Voltage!!


$$I(x) = \frac{V_R/Z_c + I_R}{2} e^{\alpha x} - \frac{V_R/Z_c - I_R}{2} e^{-\alpha x}$$

No Reflected Current!!

(Load =  $Z_c$ )  
 → "Flat Line", "Infinite Line"
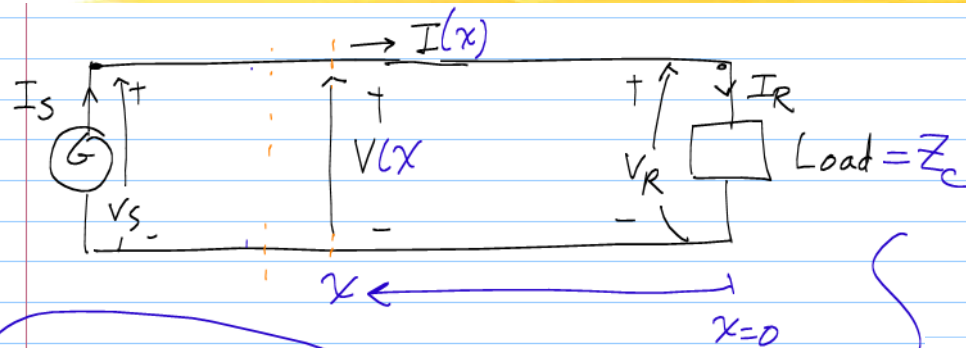
# Flat Line or "Infinite Line"

⌘ Load at the receiver side =  $Z_c$  (Characteristic Impedance) case



$$\rightarrow V_R = I_R \cdot Z_c$$

$$V(x) = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

No Reflected Voltage!!



$$I(x) = \frac{V_R/Z_c + I_R}{2} e^{\alpha x} - \frac{V_R/Z_c - I_R}{2} e^{-\alpha x}$$

No Reflected Current!!

(Load =  $Z_c$ )  
 → "Flat Line", "Infinite Line"

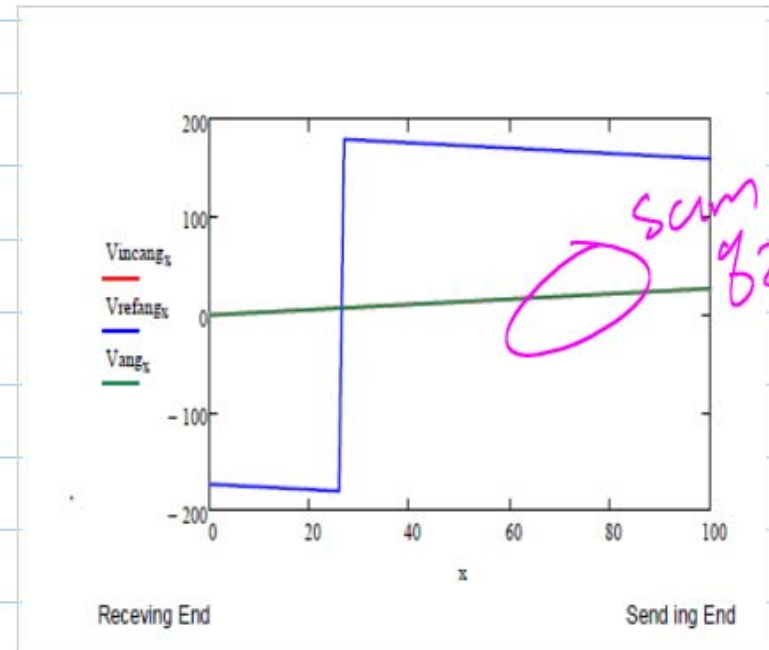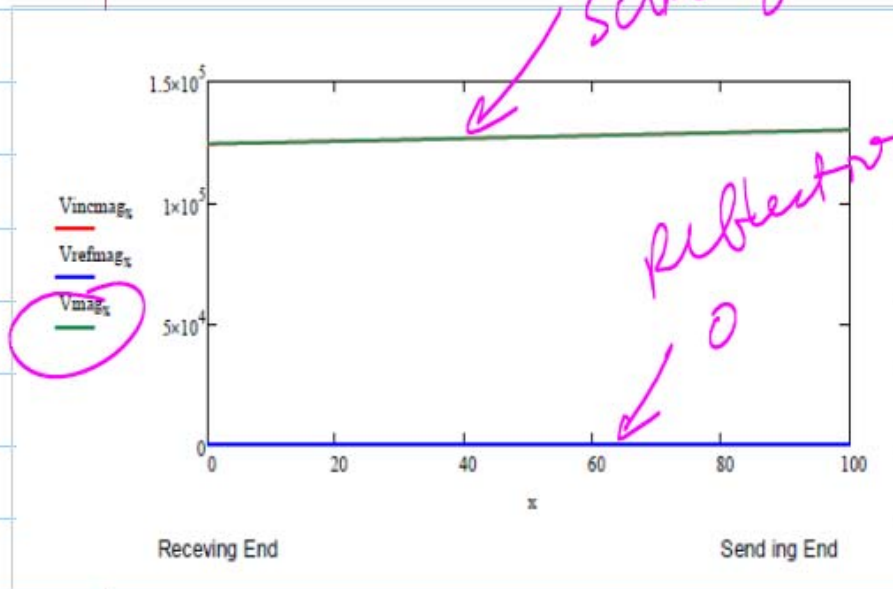
# Long Transmission Line (> 150 miles)

$$IR := \frac{VR}{Zc} = 304.054 + 29.172i$$


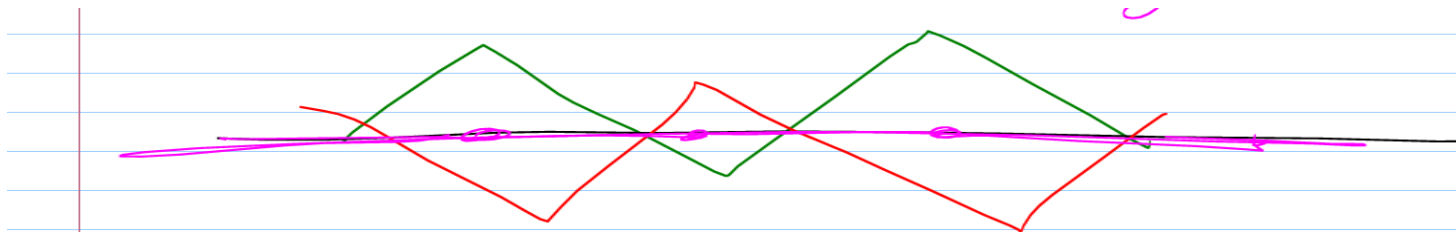
# Observation

- ⌘ Termination of a line with the characteristic impedance of the transmission line eliminates the reflection wave
- ⌘ Reflective wave can interfere with the incident wave and produces interference, and leads to standing waves which do not propagate along the line



- ⌘ Power lines are difficult to terminate with the characteristic impedance
- ⌘ Communication lines are frequently terminated with characteristic impedance to eliminate the reflected wave and thus any interference




# Zc and “Surge Impedance”

- ⌘ Characteristic impedance (Zc)

$$Z_c = \sqrt{\frac{Z}{y}}$$

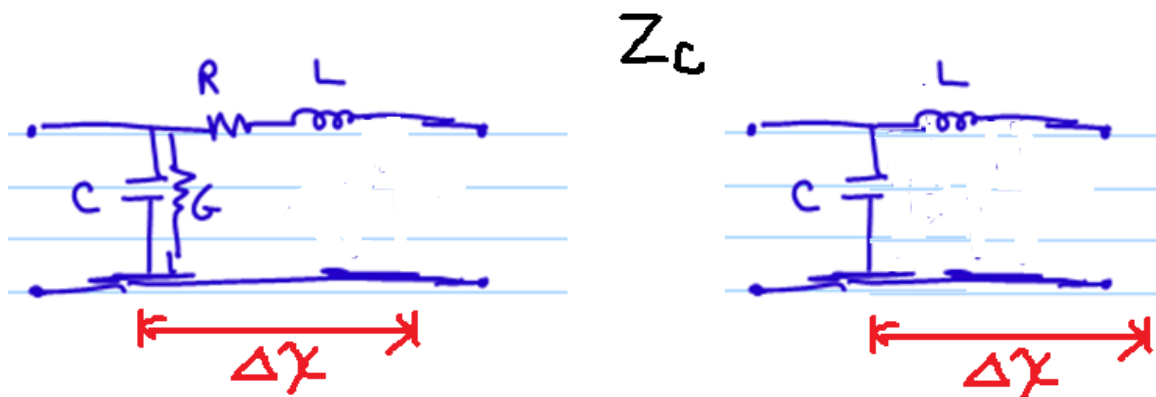- ⌘ Surge Impedance: Zc with the **condition** that r (series resistance) = 0 and G (shunt conductance) = 0 [this condition is called **Lossless Line**]



- ⌘ Surge Impedance

$$Z_c = \sqrt{\frac{L}{C}} \quad [\Omega]$$