

Surge Impedance and Loading Power

⌘ Remember: Surge Impedance

$$Z_c = \sqrt{\frac{L}{C}} \quad [\Omega]$$

⌘ Lossless Line is assumed

⌘ If a load is purely resistive equal to the surge impedance

$$Z_{load} = \sqrt{\frac{L}{C}}$$

⌘ The, Load Current is given by (where V_L is line-to-line voltage)

$$|I_L| = \frac{|V_L|}{\sqrt{3} \cdot \sqrt{\frac{L}{C}}}$$

Surge Impedance and Loading Power

- ⌘ If a load is purely resistive equal to the surge impedance

$$Z_{load} = \sqrt{\frac{L}{C}}$$

- ⌘ The, Power (3-phase) delivered to the load:

$$|I_L| = \frac{|V_L|}{\sqrt{3} \cdot \sqrt{\frac{L}{C}}}$$

3φ

$$P_L = \sqrt{3} |V_L| |I_L| \quad (\text{in a lossless line})$$
$$= \sqrt{3} |V_L| \frac{|V_L|}{\sqrt{3} \sqrt{\frac{L}{C}}} = \frac{|V_L|^2}{\sqrt{\frac{L}{C}}} \text{ [W]}$$
$$= SIL \text{ (Surge Impedance Loading) [W]}$$

No [Var]

Surge Impedance Loading

⌘

$$V(x) = \frac{V_R + I_R Z_c}{2} e^{\alpha x} e^{j\beta x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x} e^{-j\beta x}$$

No Reflected Voltage!!

$$e^{\gamma x} = e^{\alpha x} \cdot e^{j\beta x}$$

⌘

$$V_R = I_R Z_c$$


$$\frac{V_R + I_R Z_c}{2} = V_R$$



$$V(x) = V_R$$

Voltage at any location x is the same as the receiving end voltage
Flat Voltage Profile

⌘

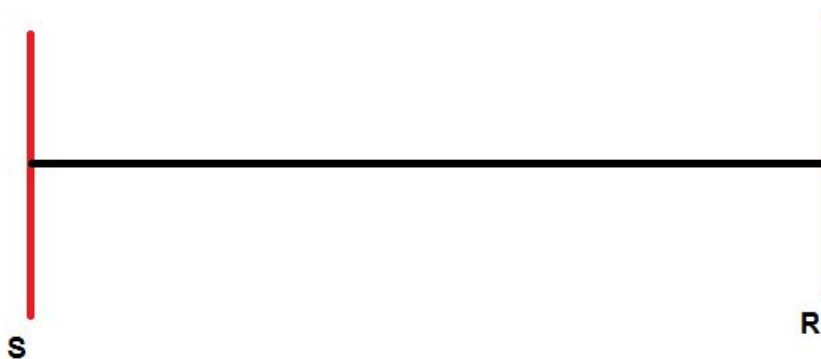

$$\gamma = \alpha + j\beta$$

$$\gamma = \sqrt{zy}$$

$$j\omega L \quad j\omega C$$

$$= j\omega \sqrt{LC}$$


$$= 0 + j\beta$$

$$\alpha = 0$$

No attenuation

Surge Impedance and Loading Power

⌘ Role of Transmission Line

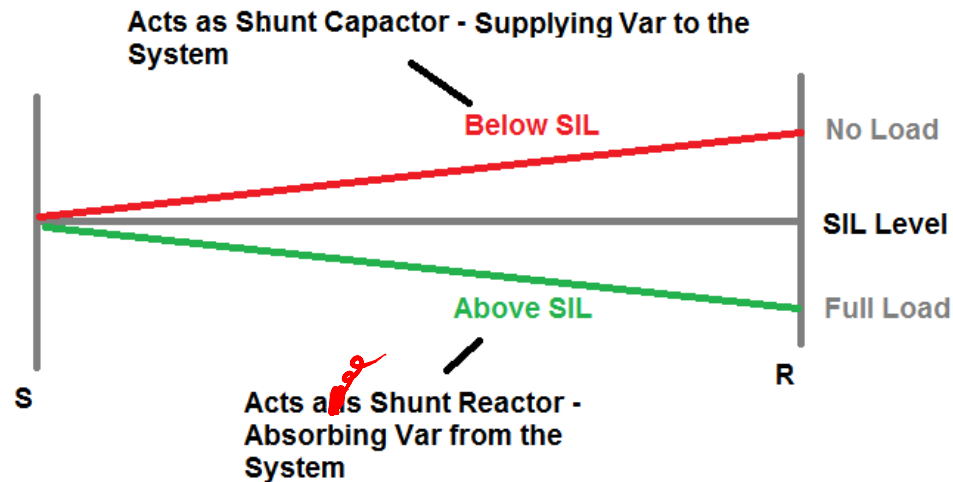

⌘ Practical use of SIL (Surge Impedance Loading)

- ⊞ A permissible loading of a transmission may be expressed by a fraction of its SIL
- ⊞ SIL may provide a comparison of load carrying capability of lines

Surge Impedance Loading

⌘ Role of Transmission Line

www.o-t-s.com/surge_impedance_loading.html

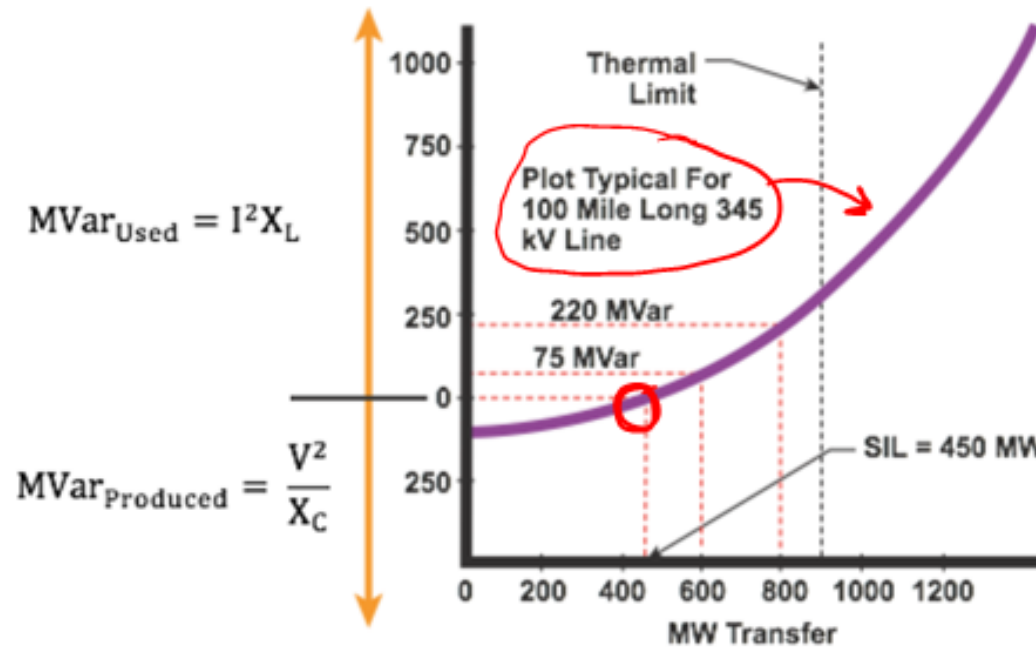


Figure 1

Surge Impedance Loading of a Transmission Line

Hyperbolic Form or the equations

⌘

$$V(x) = \frac{V_R + I_R \cdot Z_c}{2} e^{\nu x} + \frac{V_R - I_R Z_c}{2} e^{-\nu x}$$

$$I(x) = \frac{V_R/Z_c + I_R}{2} e^{\nu x} - \frac{V_R/Z_c - I_R}{2} e^{-\nu x}$$

more convenient form by hyperbolic functions:


$$\begin{cases} \sinh \theta = \frac{e^\theta - e^{-\theta}}{2} \\ \cosh \theta = \frac{e^\theta + e^{-\theta}}{2} \end{cases}$$

$$\rightarrow \begin{cases} e^\theta = \sinh \theta + \cosh \theta \\ e^{-\theta} = \cosh \theta - \sinh \theta \end{cases}$$

⌘

$$\sinh x = \frac{1}{2} [e^x - e^{-x}]$$

$$\cosh x = \frac{1}{2} [e^x + e^{-x}]$$

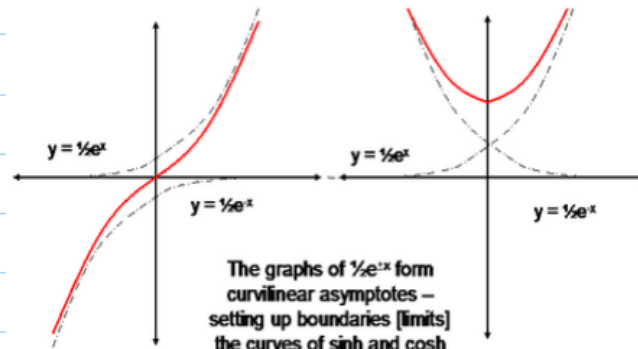

Hyperbolic Form or the equations

$$V(x) = \frac{V_R + I_R \cdot Z_c}{2} e^{\alpha x} + \frac{V_R - I_R Z_c}{2} e^{-\alpha x}$$

$$= \frac{V_R + I_R \cdot Z_c}{2} (\sinh \alpha x + \cosh \alpha x)$$

$$+ \frac{V_R - I_R \cdot Z_c}{2} (\cosh \alpha x - \sinh \alpha x)$$

$$= \left[\frac{V_R + I_R \cdot Z_c + V_R - I_R \cdot Z_c}{2} \cosh \alpha x \right]$$

$$+ \left[\frac{V_R + I_R \cdot Z_c - V_R + I_R \cdot Z_c}{2} \sinh \alpha x \right]$$



$$V(x) = V_R \cdot \cosh \alpha x + I_R \cdot Z_c \cdot \sinh \alpha x$$

Similarly,

$$I(x) = I_R \cdot \cosh \alpha x + \frac{V_R}{Z_c} \cdot \sinh \alpha x$$




Hyperbolic Form or the equations

ABCD constants? → Need to find $\underline{V_S}$.

⌘ $V_S = V(x) \Big|_{x=l} \leftarrow \begin{array}{c} S \xleftarrow{x=l} \xrightarrow{x=0} R \\ \text{length of the line} \end{array}$

$$\begin{cases} V_S = V_R \cdot \cosh \alpha l + I_R \cdot Z_c \cdot \sinh \alpha l \\ I_S = \frac{V_R}{Z_c} \cdot \sinh \alpha l + I_R \cdot \cosh \alpha l \end{cases}$$
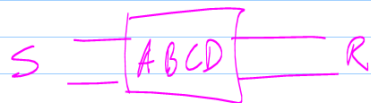
$$\begin{aligned} A &= \cosh \alpha l & B &= Z_c \cdot \sinh \alpha l \\ C &= \frac{\sinh \alpha l}{Z_c} & D &= \cosh \alpha l \end{aligned}$$



NOTE:

$\begin{cases} V_S, V_R : \text{Line-to-neutral Voltage (V}_\phi\text{)} \\ I_S, I_R : \text{Line current.} \end{cases}$

⌘
$$\begin{cases} V_R = V_S \cdot \cosh \alpha l - I_S \cdot Z_c \cdot \sinh \alpha l \\ I_R = I_S \cdot \cosh \alpha l - \frac{V_S}{Z_c} \cdot \sinh \alpha l \end{cases}$$

What if your calculator does not do Hyperbolic?

⌘

$$V(x) = \frac{V_R + I_R \cdot Z_C}{2} e^{\gamma x} + \frac{V_R - I_R \cdot Z_C}{2} e^{-\gamma x}$$

$$I(x) = \frac{V_R / Z_C + I_R}{2} e^{\gamma x} - \frac{V_R / Z_C - I_R}{2} e^{-\gamma x}$$



⌘

$$V_S = \frac{V_R + I_R \cdot Z_C}{2} e^{\gamma l} + \frac{V_R - I_R \cdot Z_C}{2} e^{-\gamma l}$$

$$I_S = \frac{V_R / Z_C + I_R}{2} e^{\gamma l} - \frac{V_R / Z_C - I_R}{2} e^{-\gamma l}$$

Hyperbolic Form or the equations

More on hyperbolic cos & sin

$$\begin{cases} \cosh(\alpha + j\beta l) = \cosh \alpha \cos \beta l + j \sinh \alpha \sin \beta l \\ \sinh(\alpha + j\beta l) = \sinh \alpha \cos \beta l + j \cosh \alpha \sin \beta l \end{cases}$$

Maclaurin's Series

$$\begin{cases} \cosh \theta = 1 + \frac{\theta^2}{2!} + \frac{\theta^4}{4!} + \frac{\theta^6}{6!} + \dots \\ \sinh \theta = \theta + \frac{\theta^3}{3!} + \frac{\theta^5}{5!} + \frac{\theta^7}{7!} + \dots \end{cases}$$

phasor


$$\begin{cases} \cosh(\alpha + j\beta) = \frac{e^{\alpha + j\beta} + e^{\alpha - j\beta}}{2} = \frac{1}{2}(e^{\alpha} \angle \beta + e^{\alpha} \angle -\beta) \\ \sinh(\alpha + j\beta) = \frac{e^{\alpha + j\beta} - e^{\alpha - j\beta}}{2} = \frac{1}{2}(e^{\alpha} \angle \beta - e^{\alpha} \angle -\beta) \end{cases}$$

Example 5.1

⌘ A single-circuit 60-Hz transmission line is 370 km (or 230 mi) long. The conductor's outside diameter is 0.977 in. And the flat horizontal spacing is 7.25 m (or 23.8 ft) between conductors. The resistance of the conductor is 0.1603 ohm/mile. The load on the line is 125 MW at 215 kV with 1 unity power factor. (a) Find the voltage, current, and power at the sending end. (b) Find the voltage regulation of the line. (c) Determine the wavelength and velocity of propagation of the line.

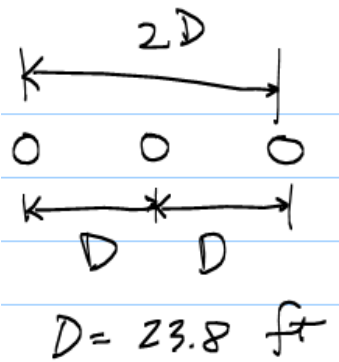Example 5.1

- ⌘ A single-circuit 60-Hz transmission line is 370 km (or 230 mi) long. The conductor's outside diameter is 0.977 in. And the flat horizontal spacing is 7.25 m (or 23.8 ft) between conductors. The resistance of the conductor is 0.1603 ohm/mile. The load on the line is 125 MW at 215kV with 1 unity power factor. (a) Find the voltage, current, and power at the sending end. (b) Find the voltage regulation of the line. (c) Determine the wavelength and velocity of propagation of the line.



$$d = 0.977 \text{ in}$$

$$R = 0.1603 / \text{mile}$$

$$D_{eq} := \sqrt[3]{D_{12} \cdot D_{23} \cdot D_{31}} = 29.9861 \text{ ft}$$

$$R_0 := 0.1603 \text{ } \Omega / \text{mile}$$

$$r' := r \cdot 0.7788$$

$$d = 0.977 \text{ in} \quad \text{len} = 230 \text{ mile}$$

$$r = \frac{d}{2.12} = 0.0407 \text{ ft}$$

$$L := 2 \cdot 10^{-7} \cdot \ln \left(\frac{D_{eq}}{r'} \right) = 1.3704 \cdot 10^{-6} \text{ H / m}$$


$$XL := 2 \cdot \pi \cdot 60 \cdot L \cdot 1609 = 0.8313 \text{ } \Omega / \text{mile}$$

$$z := R_0 + i \cdot XL = 0.1603 + 0.8313 \cdot i \text{ } \Omega / \text{mile}$$



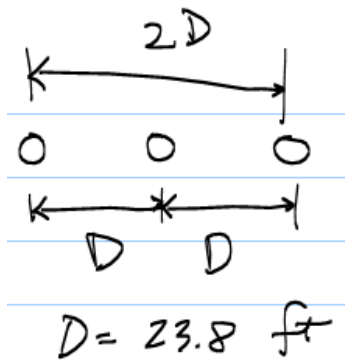Example 5.1

- ⌘ A single-circuit 60-Hz transmission line is 370 km (or 230 mi) long. The conductor's outside diameter is 0.977 in. And the flat horizontal spacing is 7.25 m (or 23.8 ft) between conductors. The resistance of the conductor is 0.1603 ohm/mile. The load on the line is 125 MW at 215kV with 1 unity power factor. (a) Find the voltage, current, and power at the sending end. (b) Find the voltage regulation of the line. (c) Determine the wavelength and velocity of propagation of the line.



$$d = 0.977 \text{ in}$$

$$R = 0.1603 / \text{mile}$$

$$k = 8.85 \cdot 10^{-12}$$

$$C_n = \frac{2 \cdot \pi \cdot k}{\ln\left(\frac{D_{eq}}{r}\right)} = 8.4226 \cdot 10^{-12} \text{ F / m}$$

$$X_c = \frac{1}{2 \cdot \pi \cdot 60 \cdot C_n \cdot 1609 \cdot i} = -1.9574 \cdot 10^5 \cdot i \text{ } \Omega \text{ mile}$$

$$y = \frac{1}{X_c} = 5.1089426 \cdot 10^{-6} \cdot i \text{ S / mile}$$

$$y_1 = \sqrt{y \cdot z} \cdot \text{len} = 0.0454922 + 0.4761608 \cdot i$$



Example 5.1

⌘ $V_S = V_R \cdot \cosh \gamma l + I_R \cdot Z_C \cdot \sinh \gamma l$ km (or 230 mi) long. The conductor's outside spacing is 7.25 m (or 23.8 ft) between
 $I_S = \frac{V_R}{Z_C} \cdot \sinh \gamma l + I_R \cdot \cosh \gamma l$ 0.1603 ohm/mile. The load on the line is 125
 (a) Determine the voltage, current, and power at the the line. (c) Determine the wavelength and

$$\gamma l := \sqrt{y \cdot z} \cdot \text{len} = 0.0454922 + 0.4761608 \cdot i$$

$$Z_C := \sqrt{\frac{z}{y}} = 405.2236295 - 38.7148641 \cdot i$$

$$P_R := 125 \cdot 10^6$$

$$V_R := \frac{215000}{\sqrt{3}} = 1.2413031 \cdot 10^5$$

$$I_R := \frac{P_R}{3 \cdot V_R} = 335.6687612$$

$$\cosh(\gamma l) = 0.8896811 + 0.0208595 \cdot i$$

$$\sinh(\gamma l) = 0.0404456 + 0.4588448 \cdot i$$

⌘

Example 5.1

$$V_S = V_R \cdot \cosh \gamma l + I_R \cdot Z_C \cdot \sinh \gamma l \quad \cosh(\gamma l) = 0.8896811 + 0.0208595 \cdot i$$

$$I_S = \frac{V_R}{Z_C} \cdot \sinh \gamma l + I_R \cdot \cosh \gamma l \quad \sinh(\gamma l) = 0.0404456 + 0.4588448 \cdot i$$

$$V_S := V_R \cdot \cosh(\gamma l) + I_R \cdot Z_C \cdot \sinh(\gamma l) = 1.2190069 \cdot 10^5 + 64476.1743055 \cdot i$$

$$|V_S| = 1.3790198 \cdot 10^5 \quad \arg(V_S) \cdot \frac{180}{\pi} = 27.8754275$$

$$I_S := \frac{V_R}{Z_C} \cdot \sinh(\gamma l) + I_R \cdot \cosh(\gamma l) = 297.6084302 + 147.4593272 \cdot i$$

$$|I_S| = 332.1371 \quad \arg(I_S) \cdot \frac{180}{\pi} = 26.3575$$

$$\text{pf} := \cos(\arg(V_S) - \arg(I_S)) = 0.9996491$$

$$PS := 3 \cdot |V_S| \cdot |I_S| = 1.3740708 \cdot 10^8$$

Example 5.1

- ⌘ A single-circuit 60-Hz transmission line is 370 km (or 230 mi) long. The conductor's outside diameter is 0.977in. And the flat horizontal spacing is 7.25 m (or 23.8 ft) between conductors. The resistance of the conductor is 0.1603 ohm/mile. The load on the line is 125 MW at 215kV with 1 unity power factor. (a) Find the voltage, current, and power at the sending end. (b) Find the voltage regulation of the line. (c) Determine the wavelength and velocity of propagation of the line.

No Load Voltage: VR at IR=0

$$VR_{nl} := \frac{VS}{\cosh(\gamma l)} = 1.3863912 \cdot 10^5 + 69220.5777301 \cdot i$$

$$V_{reg} := \frac{|VR_{nl}| - |VR|}{|VR|} \cdot 100 = 24.8357524 \text{ percent}$$



Example 5.1

- ⌘ A single-circuit 60-Hz transmission line is 370 km (or 230 mi) long. The conductor's outside diameter is 0.977in. And the flat horizontal spacing is 7.25 m (or 23.8 ft) between conductors. The resistance of the conductor is 0.1603 ohm/mile. The load on the line is 125 MW at 215kV with 1 unity power factor. (a) Find the voltage, current, and power at the sending end. (b) Find the voltage regulation of the line. (c) Determine the wavelength and velocity of propagation of the line.

phase shift per mile

$$\text{Since } \gamma l = \alpha l + j\beta l$$

$$\beta l = \text{Im}(\gamma l) = 0.4761608$$

$$\beta = \frac{\beta l}{\text{len}} = 0.0020703$$

wavelength

$$\lambda = \frac{2 \cdot \pi}{\beta} = 3034.9677489 \quad \text{mile}$$

Velocity

$$f = 60 \quad \text{Hz}$$

$$v = f \cdot \lambda = 1.8209806 \cdot 10^5 \quad \text{mile / sec}$$

Class Activity

⌘ Class Activity on Transmission Parameters

A 3-phase 60-Hz transmission line is 250 miles long. The voltage at the sending end is 220 kV. The parameters of the line are $R = 0.2 \Omega/\text{mile}$, $X = 0.8 \Omega/\text{mile}$, and $Y = 5.3 \mu\text{S}/\text{mile}$. Find the sending-end current when there is no load on the line.

$$V_S = V_R \cdot \cosh \gamma l + I_R \cdot Z_c \cdot \sinh \gamma l$$

$$I_S = \frac{V_R}{Z_c} \cdot \sinh \gamma l + I_R \cdot \cosh \gamma l$$

$$V_S = \frac{V_R + I_R \cdot Z_c}{2} e^{\gamma l} + \frac{V_R - I_R \cdot Z_c}{2} e^{-\gamma l}$$

$$I_S = \frac{V_R/Z_c + I_R}{2} e^{\gamma l} - \frac{V_R/Z_c - I_R}{2} e^{-\gamma l}$$

⌘

$$\gamma l := \sqrt{y \cdot z} \cdot \text{len}$$

$$Z_c := \sqrt{\frac{z}{y}}$$

$$V_S := \frac{220}{\sqrt{3}} \cdot 10^3$$

For $I_R = 0$:

$$V_R := \frac{V_S}{\cosh(\gamma l)}$$

$$I_S := \left(\frac{V_R}{Z_c} \right) \cdot \sinh(\gamma l)$$

What if your calculator does not do Hyperbolic?

⌘

$$V(x) = \frac{V_R + I_R \cdot Z_c}{2} e^{\nu x} + \frac{V_R - I_R \cdot Z_c}{2} e^{-\nu x}$$

$$I(x) = \frac{V_R / Z_c + I_R}{2} e^{\nu x} - \frac{V_R / Z_c - I_R}{2} e^{-\nu x}$$



⌘

$$V_S = \frac{V_R + I_R \cdot Z_c}{2} e^{\nu l} + \frac{V_R - I_R \cdot Z_c}{2} e^{-\nu l}$$


$$I_S = \frac{V_R / Z_c + I_R}{2} e^{\nu l} - \frac{V_R / Z_c - I_R}{2} e^{-\nu l}$$

$$\begin{aligned} \nu &= \alpha + j\beta \\ e^{\nu x} &= e^{\alpha x} \cdot e^{j\beta x} \\ &= e^{\alpha x} \cdot \left(\cos \beta x + j \sin \beta x \right) \end{aligned}$$

[rad]

Equivalent Circuit of a Long Line

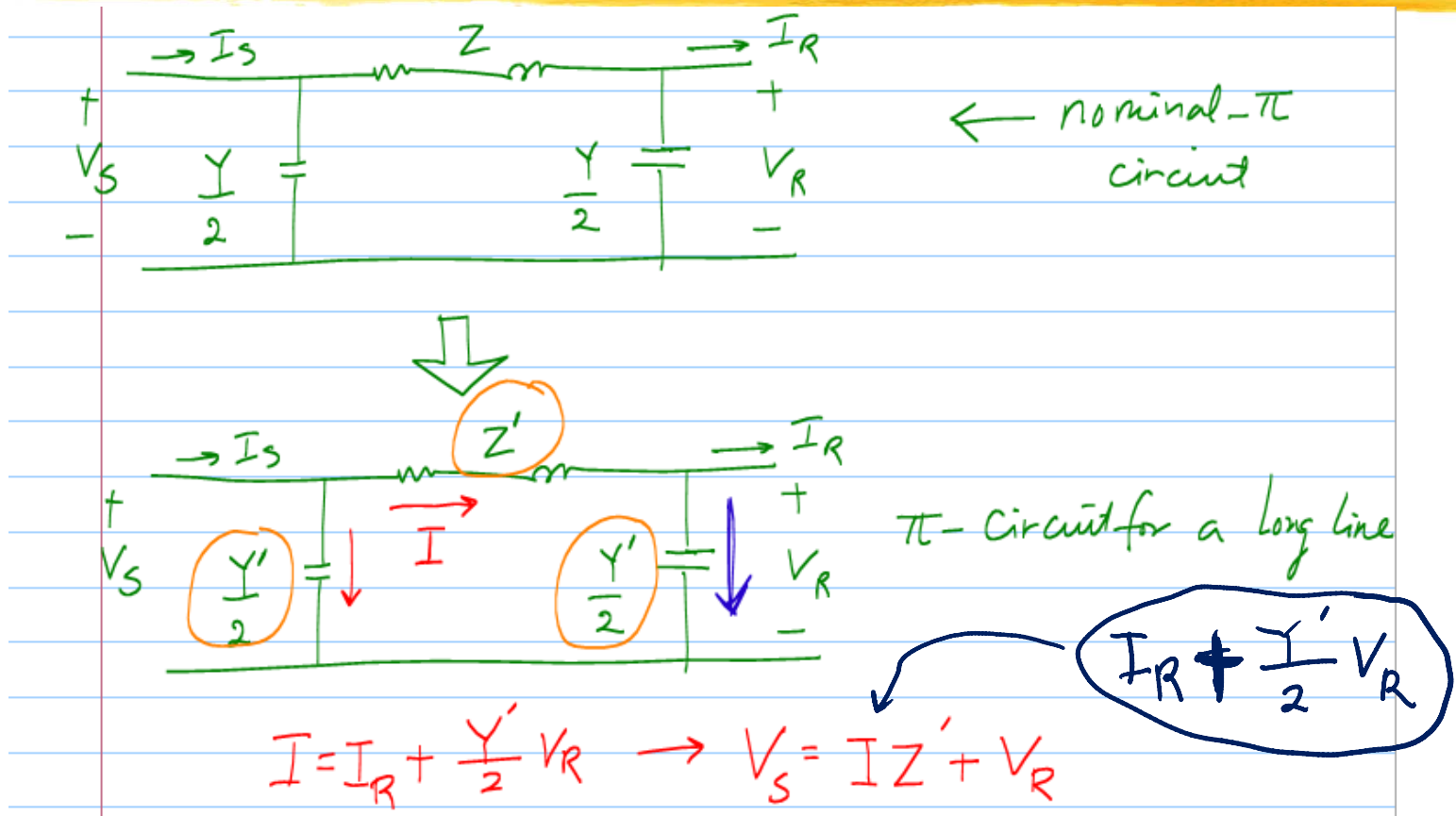⌘ Can we use Pi-circuit even for a long line?



Equi

⌘ Can we

$$V_S = \left(I_R + \frac{Y'}{2} V_R \right) Z' + V_R$$

$$V_S = \left(\frac{ZY'}{2} + 1 \right) V_R + Z' I_R$$

$$V_S = V_R \cosh \gamma l + I_R Z_c \sinh \gamma l$$

$$I_S = I_R \cosh \gamma l + \frac{V_R}{Z_c} \sinh \gamma l$$

$$Z_c = \sqrt{\frac{z}{y}} \quad \gamma = \sqrt{zy}$$

$$V_S = \left(\frac{ZY}{2} + 1 \right) V_R + Z \cdot I_R$$

$$I_S = Y \left(\frac{ZY}{4} + 1 \right) V_R + \left(\frac{ZY}{2} + 1 \right) I_R$$

Nominal
π-ckt

$$Z' = Z_c \cdot \sinh \gamma l$$

$$= \sqrt{\frac{z}{y}} \cdot \sinh \gamma l = \frac{\sqrt{z} \cdot \sqrt{z} \cdot l}{\sqrt{y} \cdot \sqrt{z} \cdot l} \cdot \sinh \gamma l = z l = Z_{\text{(total series impedance)}}$$

$$Z' = Z \frac{\sinh \gamma l}{\sqrt{zy} l} = Z \cdot \frac{\sinh \gamma l}{\gamma l}$$

multiplying factor to convert nominal-π ckt to long-line equivalent-π ckt

If γl is small, $\frac{\sinh \gamma l}{\gamma l} \sim 1$

medium / short transmission line

E

For Y'

ne

⌘ Can

$$V_S = \left(\frac{Z'Y'}{2} + 1 \right) V_R + Z' \cdot I_R$$

Equate

$$V_S = V_R \cosh \nu l + I_R Z_c \sinh \nu l$$

$$\begin{aligned} (Z = z l) \\ \nu l = \sqrt{yz} \cdot l \end{aligned}$$

$$\frac{Z'Y'}{2} + 1 = \cosh \nu l$$

From above

$$Z' = Z \cdot \frac{\sinh \nu l}{\nu l}$$

$$= Z_c \sinh \nu l$$

$$\frac{Y' (Z_c \sinh \nu l)}{2} + 1 = \cosh \nu l$$

$$\frac{Y'}{2} = \frac{\cosh \nu l - 1}{Z_c \sinh \nu l} = \frac{1}{Z_c} \cdot \frac{\cosh \nu l - 1}{\sinh \nu l}$$

E

ne

⌘ Can

$$\tanh\left(\frac{rl}{2}\right) = \frac{\cosh rl - 1}{\sinh rl}$$

$$\frac{Y'}{2} = \left(\frac{1}{Z_c}\right) \cdot \tanh\left(\frac{rl}{2}\right)$$

$$\begin{cases} Z_c = \sqrt{\frac{z}{y}} & r = \sqrt{yz} \\ Y = yl \end{cases}$$

$$\begin{aligned} \frac{1}{Z_c} &= \sqrt{\frac{y}{z}} = \sqrt{\frac{y \cdot y}{zy}} = \frac{y}{\sqrt{zy}} = \frac{yl}{\sqrt{zy}l} = \frac{Y/2}{rl/2} \\ &= \frac{Y}{2} \cdot \frac{1}{rl/2} \end{aligned}$$

$$\tanh x = \frac{e^{2x} - 1}{e^{2x} + 1}$$

$$\rightarrow \frac{Y'}{2} = \frac{Y}{2} \cdot \frac{\tanh\left(\frac{rl}{2}\right)}{\left(\frac{rl}{2}\right)}$$

Correction factor from nominal- π ckt to long line equivalent- π circuit.

Nominal π to long-line π

⌘ From Nominal Pi-ckt equation ($50 < l < 150$)

$$V_S = \left(\frac{ZY}{2} + 1 \right) V_R + Z \cdot I_R$$

$$I_S = Y \left(\frac{ZY}{4} + 1 \right) V_R + \left(\frac{ZY}{2} + 1 \right) \cdot I_R$$

⌘ Lon-line equivalent pi-ckt equation ($l > 150$ miles)

$$\textcircled{Z} \leftarrow Z \cdot \frac{\sinh \nu l}{\nu l} \quad (Z')$$

$$\textcircled{Y} \leftarrow Y \cdot \frac{\tanh\left(\frac{\nu l}{2}\right)}{\tanh\left(\frac{\nu l}{2}\right)} \quad (Y')$$

Example 5.3

- ⌘ Find the equivalent pi-circuit for the line described in Example 5.1 and compare it with the nominal pi.

$$z = R_0 + i \cdot XL = 0.1603 + 0.8313 \cdot i \quad \Omega / \text{mile}$$

$$|z| = 0.8465775^{\Omega}$$

$$Z = z \cdot \text{len} = 36.869 + 191.1903779 \cdot i$$

$$\arg(z) \cdot \frac{180}{\pi} = 79.0851086$$

$$|z| = 194.7128238 \quad \arg(z) \cdot \frac{180}{\pi} = 79.0851086$$

deg

$$k = 8.85 \cdot 10^{-12}$$

$$C_n = \frac{2 \cdot \pi \cdot k}{\ln\left(\frac{D_{eq}}{r}\right)} = 8.4226 \cdot 10^{-12} \quad \text{F / m}$$

$$X_c = \frac{1}{2 \cdot \pi \cdot 60 \cdot C_n \cdot 1609 \cdot i} = -1.9574 \cdot 10^{-5} \cdot i \quad \Omega \text{ mile}$$

$$y = \frac{1}{X_c} = 5.1089426 \cdot 10^{-6} \cdot i \quad \text{S / mile}$$

$$|y| = 5.1089426 \cdot 10^{-6} \quad \arg(y) \cdot \frac{180}{\pi} = 90$$

deg

$$Y = y \cdot \text{len} = 0.0011751 \cdot i$$

$$Y_2 = \frac{Y}{2} = 0.0005875 \cdot i$$

$$|Y_2| = 0.0005875 \quad \arg(Y_2) \cdot \frac{180}{\pi} = 90$$

$$y_1 = \sqrt{y \cdot z} \cdot \text{len} = 0.0454922 + 0.4761608 \cdot i$$

$$z_c = \sqrt{\frac{Z}{Y}} = 405.2236295 - 38.7148641 \cdot i$$

Example 5.3

- ⌘ Find the equivalent pi-circuit for the line described in Example 5.1 and compare it with the nominal pi.

$$Z' = Z_0 \cdot \sinh(\gamma l) = 34.1536353 + 184.3689102 \cdot i$$

$$|Z'| = 187.5056422 \quad \arg(Z') \cdot \frac{180}{\pi} = 79.5051445$$

$$|Z| = 194.7128238$$

$$\frac{|Z'| - |Z|}{|Z|} \cdot 100 = -3.7014417 \quad \text{percent}$$

$$Y_2' = Y_2 \cdot \frac{\tanh\left(\frac{\gamma l}{2}\right)}{\frac{\gamma l}{2}} = 2.2197466 \cdot 10^{-6} + 0.0005988 \cdot i$$

$$|Y_2'| = 0.0005988 \quad |Y_2| = 0.0005875$$

$$\frac{|Y_2'| - |Y_2|}{|Y_2|} \cdot 100 = 1.9142259 \quad \text{percent}$$

$\left\{ \begin{array}{l} Z' : 3.7\% \text{ lower} \\ Y' : 2\% \text{ higher} \end{array} \right\} \rightarrow \underline{\text{Ignorable}}$

Nominal- π
 Circuit
 can represent
 Even long
 lines!!

Power Flow

⌘ Power Flow (P & Q)

- ⌘ Expressed by V, I, and pf
- ⌘ Expressed by ABCD circuit constants
 - ⌘ Focus: How V_R and I_R affects V_S
 - ⌘ ABCD Constants: All Complex Numbers

$$\begin{cases} \bar{V}_S = \bar{A} \cdot \bar{V}_R + \bar{B} \cdot \bar{I}_R & \textcircled{1} \\ \bar{I}_S = \bar{C} \cdot \bar{V}_R + \bar{D} \cdot \bar{I}_R & \textcircled{2} \end{cases}$$

$$\text{Let } \begin{cases} \bar{A} = A \angle \alpha \\ \bar{B} = B \angle \beta \\ \bar{V}_R = V_R \angle 0^\circ \\ \bar{V}_S = V_S \angle \delta \end{cases}$$

Power Flow

$$\bar{V}_S = \bar{A} \cdot \bar{V}_R + \bar{B} \cdot \bar{I}_R \quad \textcircled{1}$$

$$\textcircled{1} \rightarrow : \bar{I}_R = \frac{\bar{V}_S - \bar{A} \cdot \bar{V}_R}{\bar{B}} = \frac{\bar{V}_S}{\bar{B}} - \frac{\bar{A}}{\bar{B}} \bar{V}_R$$

$$\text{Let } \begin{cases} \bar{A} = A \angle \alpha \\ \bar{B} = B \angle \beta \\ \bar{V}_R = V_R \angle 0^\circ \\ \bar{V}_S = V_S \angle \delta \end{cases}$$

$$= \frac{V_S}{B} \angle \delta - \beta - \frac{A \cdot V_R}{B} \angle \alpha - \beta$$

$$\text{From } \bar{S}_R = \bar{V}_R \cdot \bar{I}_R^* = \frac{V_S \cdot V_R}{B} \angle \beta - \delta - \frac{A \cdot V_R^2}{B} \angle \beta - \alpha$$


Power Flow

$$\vec{S}_R = \vec{V}_R \cdot \vec{I}_R^* = \frac{V_S \cdot V_R}{B} \angle \beta - \delta - \frac{A \cdot V_R^2}{B} \angle \beta - \alpha$$

⑧ angle of V_S

④ angle of A

③ angle of B

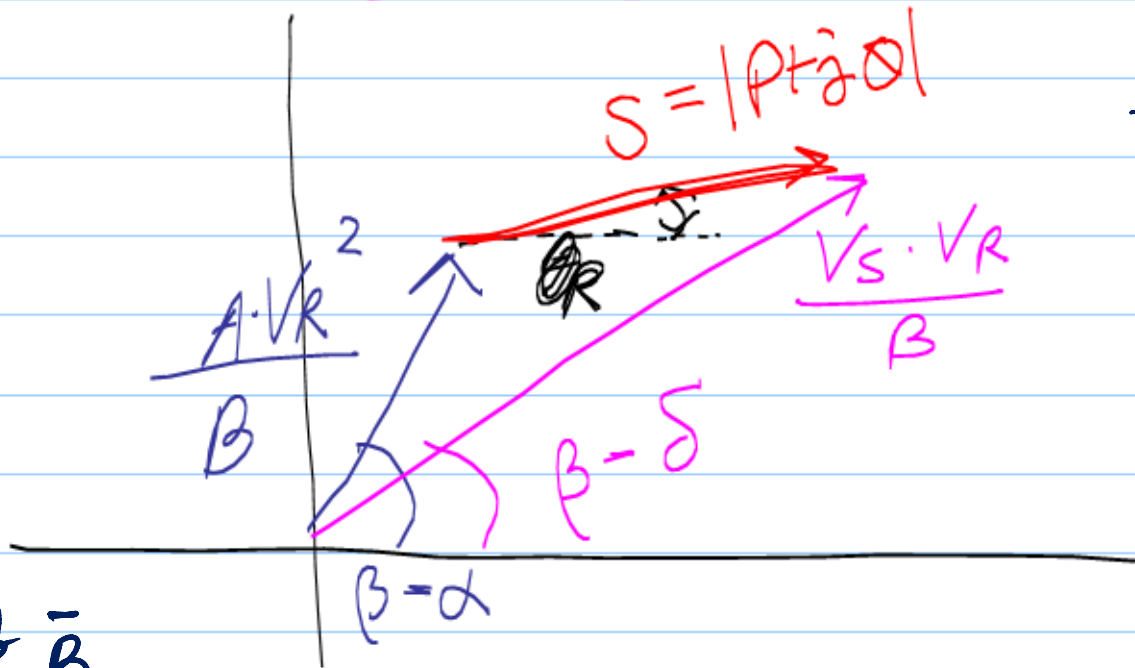


$$A = \frac{ZY}{2} + 1$$


$$B = Z$$

nominal π -ckt

Power Flow: Origin Shift

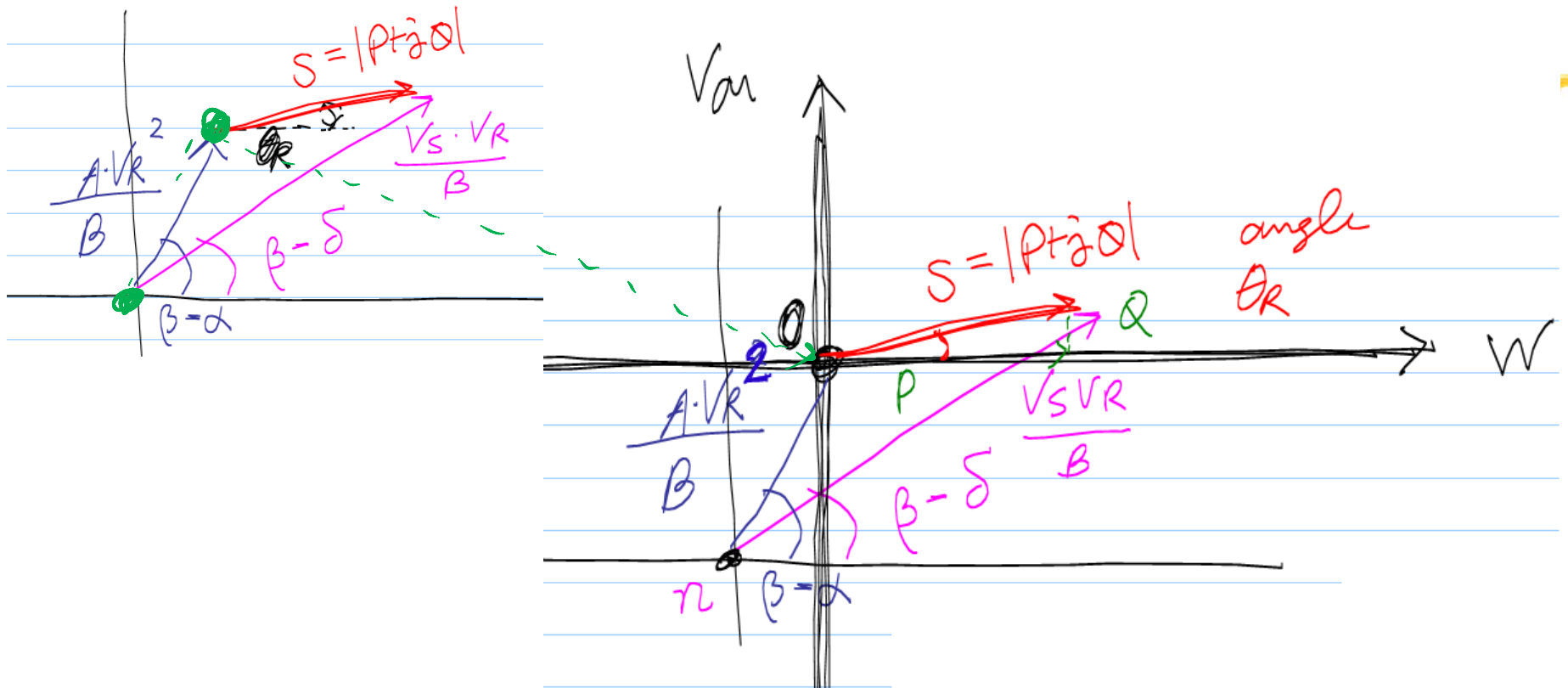

Power Flow: Origin Shift

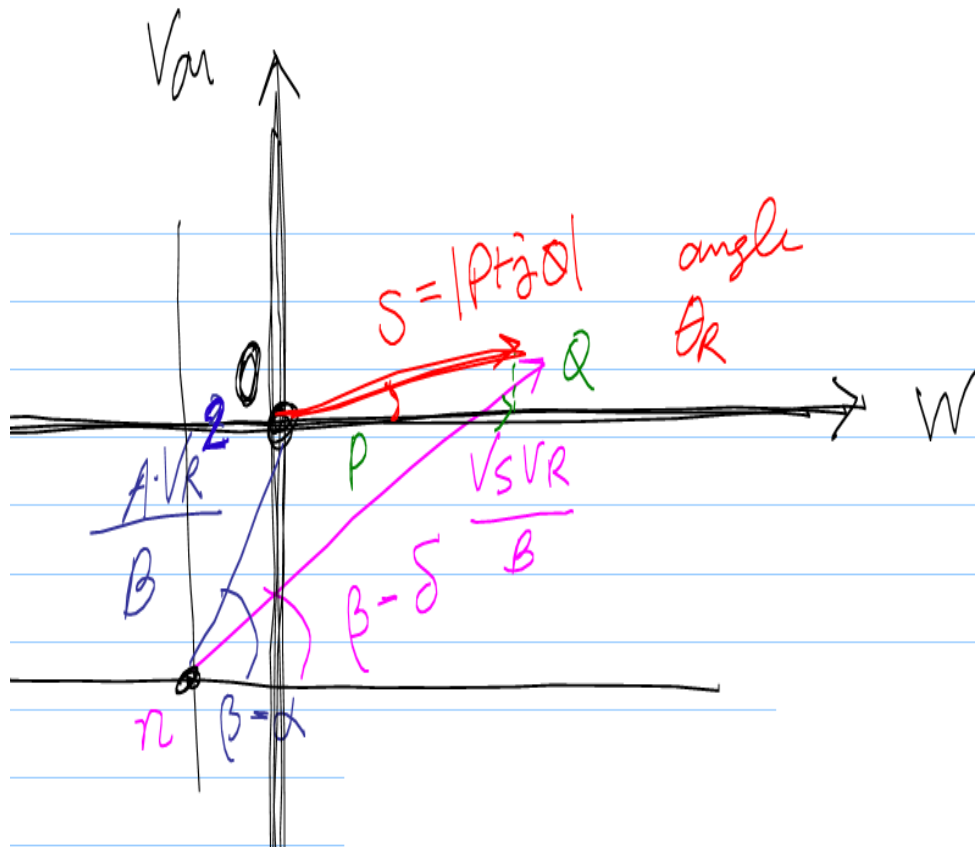


$$P_R = \frac{V_S \cdot V_R}{B} \cos(\beta - \delta) - \frac{A V_R^2}{B} \cos(\beta - \alpha)$$

$$\rightarrow P_R = V_R \cdot I_R \cdot \cos \theta_R$$

$$Q_R = \frac{V_S \cdot V_R}{B} \sin(\beta - \delta) - \frac{A V_R^2}{B} \sin(\beta - \alpha)$$

$$\rightarrow Q_R = V_R \cdot I_R \cdot \sin \theta_R$$

Power Flow

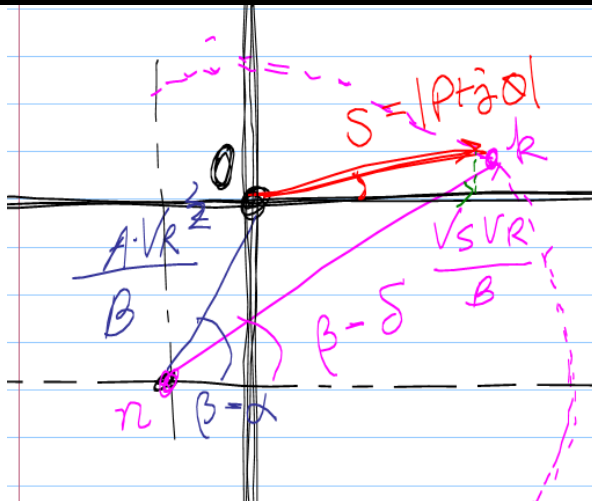

$$P_R = \frac{V_S \cdot V_R}{B} \cos(\beta - \delta) - \frac{A V_R^2}{B} \cos(\beta - \alpha)$$

$$\rightarrow P_R = V_R \cdot I_R \cdot \cos \theta_R$$


$$Q_R = \frac{V_S \cdot V_R}{B} \sin(\beta - \delta) - \frac{A V_R^2}{B} \sin(\beta - \alpha)$$

$$\rightarrow Q_R = V_R \cdot I_R \cdot \sin \theta_R$$

Observations

- ⊞ Point n is not dependent on I_R
- ⊞ Point n will not change if V_R is constant: $(A \cdot V_R^2) / B$
- ⊞ Distance between n and k is constant for fixed value of V_S and V_R : $(V_S \cdot V_R) / B$
- ⊞ Distance between o and k changes with changing load (I_R) $\bar{S} = \bar{V}_R \cdot \bar{I}_R^*$

Power Flow

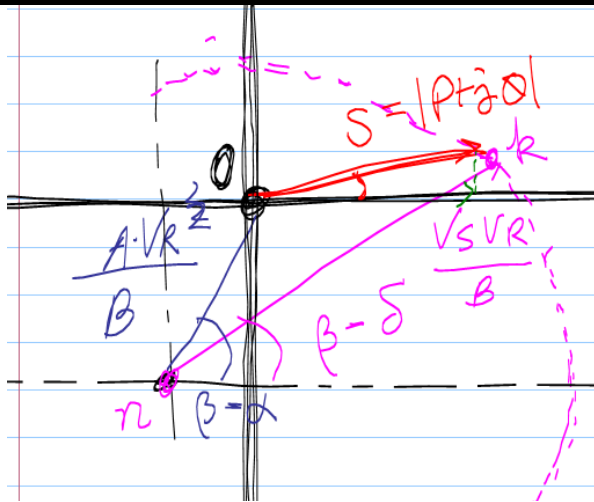

$$P_R = \frac{V_s \cdot V_R}{B} \cos(\beta - \delta) - \frac{A V_R^2}{B} \cos(\beta - \alpha)$$

$$\rightarrow P_R = V_R \cdot I_R \cdot \cos \theta_R$$

$$Q_R = \frac{V_s \cdot V_R}{B} \sin(\beta - \delta) - \frac{A V_R^2}{B} \sin(\beta - \alpha)$$

$$\rightarrow Q_R = V_R \cdot I_R \cdot \sin \theta_R$$


Observations

- ▣ Because the distance between n and k is constant, the distance between o and k is constrained to move in a circle whose center is at n .


for fixed V_R
 with varying I_R
- ▣ If V_R is held constant, a different circle can be drawn for different values of V_s 's

Power Flow for Max Power

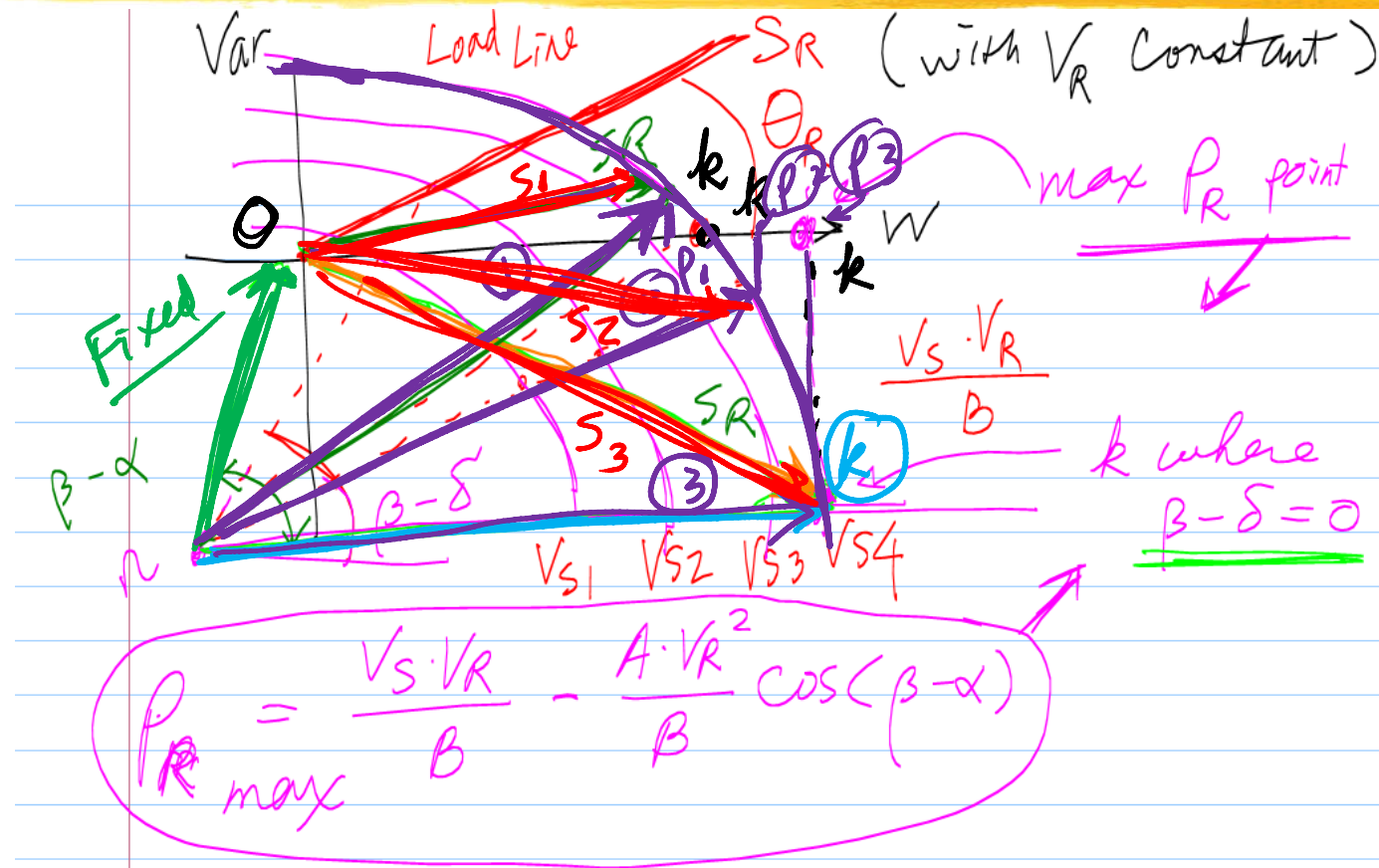⊞ If V_R is held constant, a different circle can be drawn for different values of V_S 's




Power Flow for Max Power

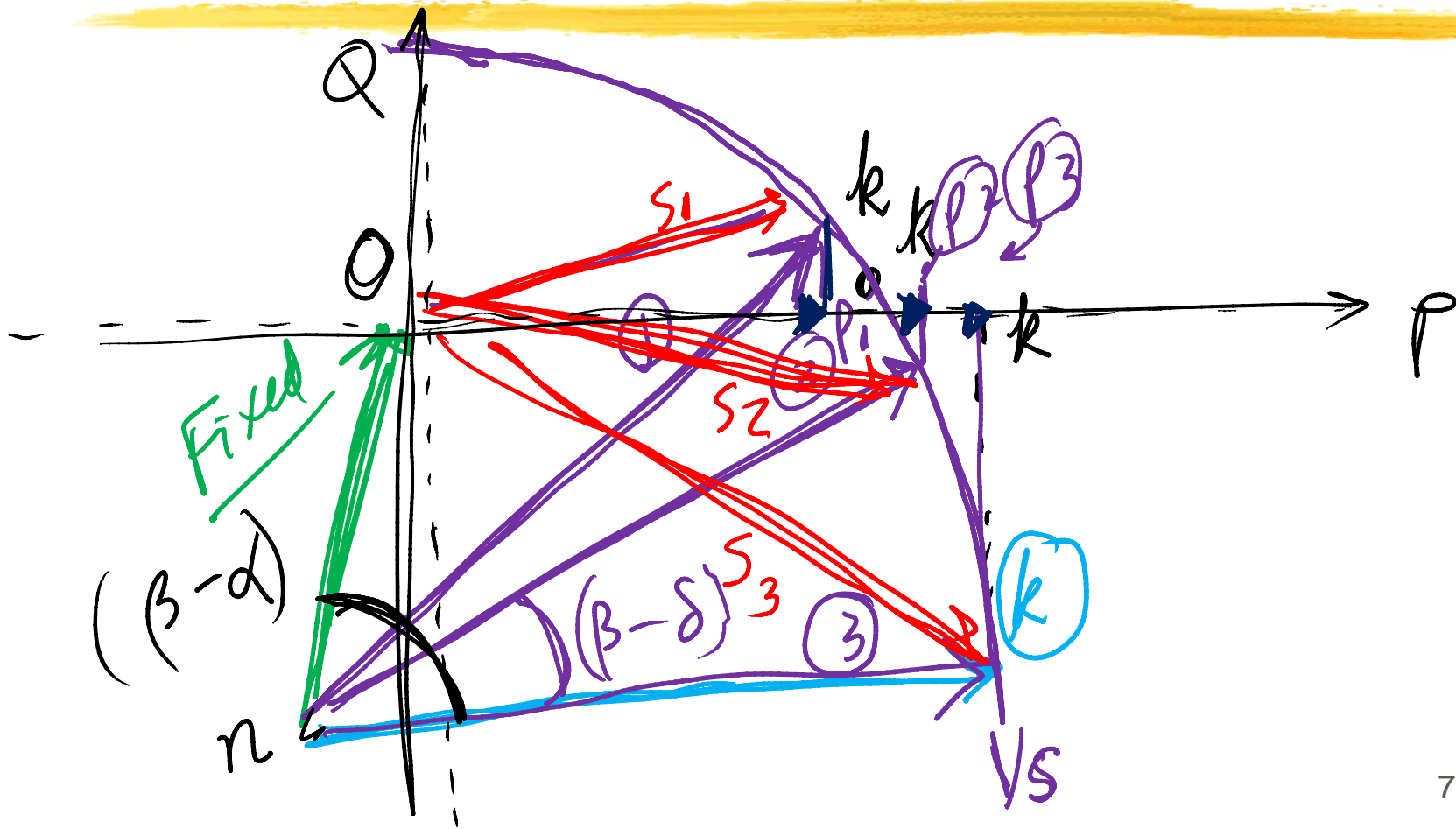

Power Flow: Impact of V_s and Var


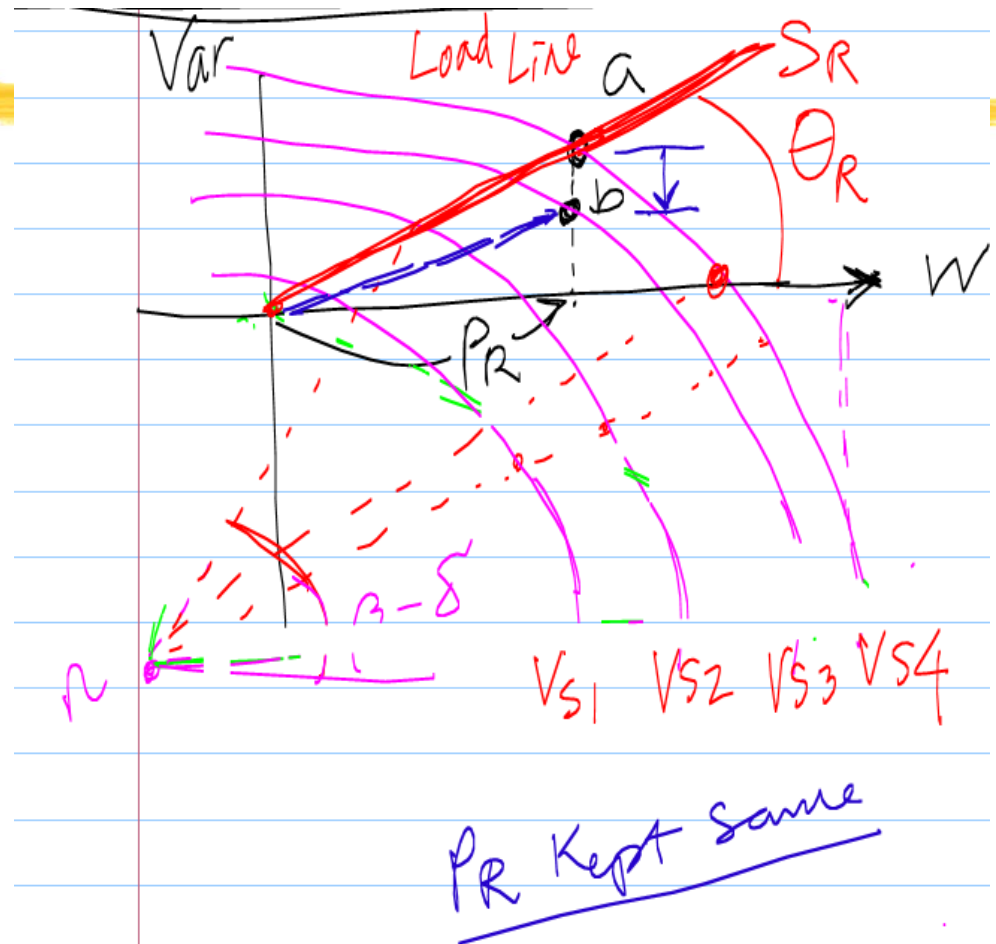
- ⌘ When PR has to be maintained, moving from a to b involves:
 - ☑ Sending end voltage reduces from V_{S4} to V_{S3}
 - ☑ (To keep the VR intact), due to the V_S decrease, the Var has to be decreased, which means negative reactive power must be supplied by parallel capacitors



Reactive Compensation of Transmission Line

⌘ Reactive Compensation by:

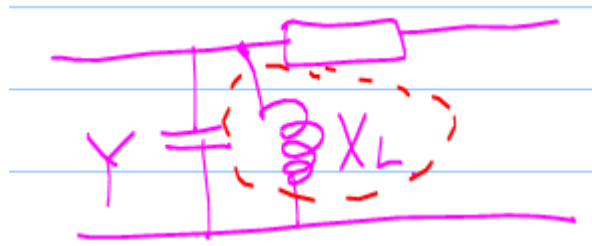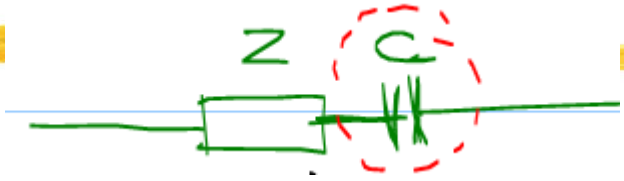- ⌘ Series Compensation: Capacitor placed in each conductor reduces the series impedance
- ⌘ Shunt Compensation: Placement of inductors between conductor and neutral reduces the susceptance (admittance)



⌘ Pi-Circuit Case

$$V_S = \left(\frac{ZY}{2} + 1\right) V_R + \overset{B}{Z} \cdot I_R$$

$$I_S = \underbrace{Y \left(\frac{ZY}{4} + 1\right)}_C V_R + \underbrace{\left(\frac{ZY}{2} + 1\right)}_D \cdot I_R$$

Nominal- π (medium)

OR $Z \leftarrow Z'$, $Y \leftarrow Y'$

$$V_S = V_R \cdot \frac{\cosh \alpha l}{A} + I_R \cdot \frac{Z_c \cdot \sinh \alpha l}{B}$$

$$I_S = \frac{V_R \cdot \sinh \alpha l}{Z_c} + I_R \cdot \frac{\cosh \alpha l}{D}$$

Equivalent- π (long)

Reactive Compensation of Transmission Line

⌘ Pi-Circuit Case

⌘ Maximum Power Equation

$$P_{R_{max}} = \frac{V_s \cdot V_R}{B} - \frac{A \cdot V_R^2}{B} \cos(\beta - \alpha)$$

dominant factor

$$B = \begin{cases} Z \\ Z_c \cdot \sinh \alpha l = \sqrt{\frac{Z}{y}} \cdot \sqrt{\frac{z}{Z}} \cdot \frac{l}{l} \cdot \sinh \alpha l \\ = \frac{z l}{\sqrt{y z} \cdot l} \sinh \alpha l = Z \cdot \frac{\sinh \alpha l}{\alpha l} \end{cases}$$

"Compensation Factor" = $\frac{X_c}{X_L}$

Total inductive reactance the line

capacitive reactance of series capacitance

$$\begin{aligned} V_s &= \left(\frac{ZY}{2} + 1 \right) V_R + Z \cdot I_R \\ I_s &= Y \left(\frac{ZY}{4} + 1 \right) V_R + \left(\frac{ZY}{2} + 1 \right) \cdot I_R \end{aligned}$$


Nominal- π (medium)

$$\begin{aligned} V_s &= V_R \cdot \frac{\cosh \alpha l}{A} + I_R \cdot \frac{Z_c \cdot \sinh \alpha l}{B} \\ I_s &= \frac{V_R}{Z_c} \cdot \frac{\sinh \alpha l}{C} + I_R \cdot \frac{\cosh \alpha l}{D} \end{aligned}$$

Equivalent- π (long)


Reactive Compensation of Transmission Line

In the southwestern part of the United States series compensation is especially important because large generating plants are located hundreds of miles from load centers and large amounts of power must be transmitted over long distances. The lower voltage drop in the line with series compensation is an additional advantage. Series capacitors are also useful in balancing the voltage drop of two parallel lines.

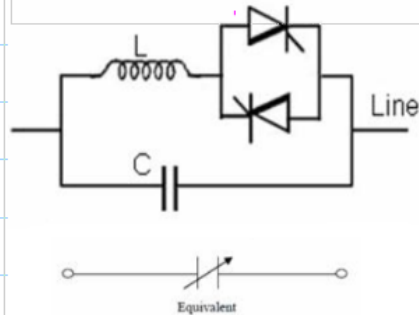

Thyristor Controlled Series Capacitor

Components of a Series Capacitor Bank

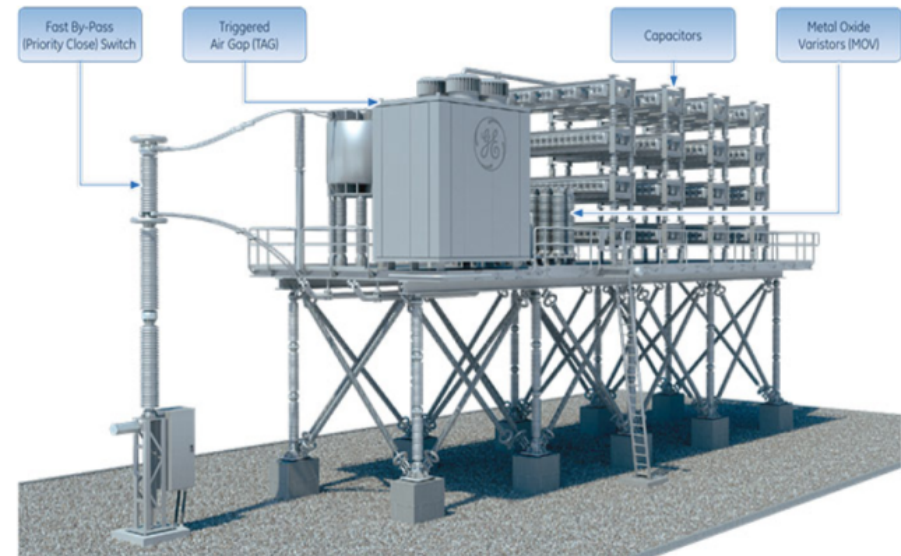

EXAMPLE 5.4: Reactive Compensation of Transmission Line

- ⌘ In order to show the relative changes in the B constant with respect to the change of the A, C, and D constants of a line when series compensation is applied, find the constants for the line of Example 5.1 uncompensated and for a series compensation factor of 70%

EXAMPLE 5.4: Reactive Compensation of Transmission Line

- ⌘ In order to show the relative changes in the B constant with respect to the change of the A, C, and D constants of a line when series compensation is applied, find the constants for the line of Example 5.1 uncompensated and for a series compensation factor of 70%

From 5.1

$$\text{len}=230$$

$$z=0.1603+0.831263 \cdot i \quad y=5.108943 \cdot 10^{-6} \cdot i$$

$$Z_c=405.223629-38.714864 \cdot i \quad \gamma l=0.045492+0.476161 \cdot i$$

For the Uncompensated Line:

$$A=\cosh(\gamma l)=0.889681+0.020859 \cdot i \quad D=A$$

$$B=Z_c \cdot \sinh(\gamma l)=34.153635+184.36891 \cdot i \quad |B|=187.505642$$

$$C=\frac{\sinh(\gamma l)}{Z_c}=-8.295422 \cdot 10^{-6}+0.001132 \cdot i$$

EXAMPLE 5.4: Reactive Compensation of Transmission Line

- ⌘ In order to show the relative changes in the B constant with respect to the change of the A, C, and D constants of a line when series compensation is applied, find the constants for the line of Example 5.1 uncompensated and for a series compensation factor of 70%

Now the compensation with Compensation Factor of 70%: $X_c/X_L = 0.7$

$$\text{Comp} = 0.7$$

$$X_c = \text{Comp} \cdot (-i) \cdot X_L \cdot \text{len} = -133.833265 \cdot i \quad X_L = 0.831263$$

Now new B constant:

$$B_{\text{new}} = B + X_c = 34.153635 + 50.535646 \cdot i \quad |B_{\text{new}}| = 60.994445$$

$$\frac{|B_{\text{new}}|}{|B|} = 0.325294$$

EXAMPLE 5.4: Reactive Compensation of Transmission Line

⌘ In o
C, a
line

Other Constants

change of the A,
constants for the
%

$$z = 0.1603 + 0.831263 \cdot i$$

$$Z = z \cdot \text{len} = 36.869 + 191.190378 \cdot i$$

$$Z_{\text{new}} = \text{Re}(z \cdot \text{len}) + i \cdot \text{Im}(z \cdot \text{len}) \cdot (1 - \text{Comp}) = 36.869 + 57.357113 \cdot i$$

$$z_{\text{new}} = \frac{Z_{\text{new}}}{\text{len}} = 0.1603 + 0.249379 \cdot i$$

$$\gamma l_{\text{new}} = \sqrt{z_{\text{new}} \cdot y} \cdot \text{len} = 0.079759 + 0.271587 \cdot i$$

$$A_{\text{new}} = \cosh(\gamma l_{\text{new}}) = 0.966412 + 0.021419 \cdot i \quad |A_{\text{new}}| = 0.96665$$

$$Z_{\text{cnew}} = \sqrt{\frac{z_{\text{new}}}{y}} = 231.126571 - 67.876998 \cdot i \quad |A| = 0.889926$$

$$\arg(A_{\text{new}}) \cdot \frac{180}{\pi} = 1.269661$$

$$C_{\text{new}} = \frac{\sinh(\gamma l_{\text{new}})}{Z_{\text{cnew}}} = -8.427465 \cdot 10^{-6} + 0.001162 \cdot i \quad |C_{\text{new}}| = 0.001162$$

$$B_{\text{new2}} = Z_{\text{cnew}} \cdot \sinh(\gamma l_{\text{new}}) = 36.044308 + 56.97852 \cdot i \quad |C| = 0.001132$$

EXAMPLE 5.4: Reactive Compensation of Transmission Line

- ⌘ In order to show the relative changes in the B constant with respect to the change of the A, C, and D constants of a line when series compensation is applied, find the constants for the line of Example 5.1 uncompensated and for a series compensation factor of 70%

$$|B_{\text{new}}| = 60.994445$$

$$|B_{\text{new2}}| = 67.422132$$

$$|B| = 187.505642$$

Consider The maximum Power Equation:

$$P_{R_{\text{max}}} = \frac{V_s \cdot V_r}{B} - \frac{A \cdot V_r^2}{B} \cos(\beta - \alpha)$$

Shunt Compensation

⌘ Charging Current Reduction with Shunt Compensation

Charging current reduction with Shunt Compensation (p112)

Remember : $I_{chg} = j\omega C_n V_{an} = \frac{V_{an}}{jX_c}$ ← "capacitive susceptance"

$$\rightarrow I_{chg} = \frac{V_{an}}{|X_c|} = B_c \cdot V_{an}$$

Connection of Inductors from line to Neutral
with amount of B_L ← "inductive susceptance"
 $= \frac{1}{|jX_L|}$

After Shunt Compensation:

$$\begin{aligned} \rightarrow I_{chg} &= (B_c - B_L) \cdot V_{an} \\ &= (B_c - B_L) \frac{B_c}{B_c} \cdot V_{an} = B_c \cdot V_{an} \left(1 - \frac{B_L}{B_c} \right) \end{aligned}$$

"Shunt Compensation Factor"