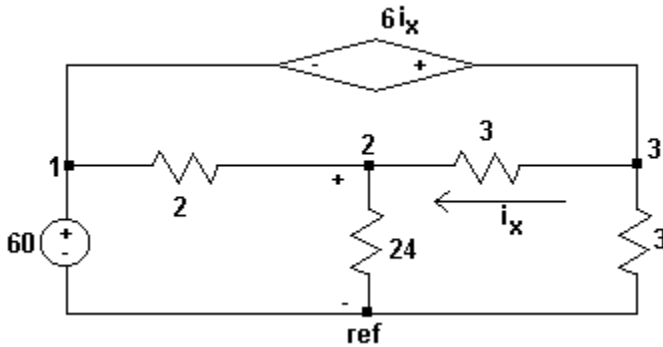


EECE499 – Homework #2
Due (F) Feb 18

SOLUTION

1. Find the voltage at node2, V_2 .



As you see above, we already have all the marks for nodes and the reference.

Solution

1. KCL at node 1: Since we already know the node voltage $V_1=60$, we do not need equation at node 1.

2. KCL at node 2: $\left\{ \frac{V_2 - 60}{2} + \frac{V_2}{24} + \frac{V_2 - V_3}{3} = 0 \right\},$

Simplification yields: $\{ 21V_2 - 8V_3 = 720 \}$ -----(1)

3. KCL at node 3: Since we have two variables in one equation (1), we'd better find one relationship that connects the V_2 and V_3 . In other words, in this example, we do not have to define a current through the dependent source.


First we relate the current i_x in terms of V_2 and V_3 : $\left\{ \frac{V_3 - V_2}{3} = i_x \right\}$

Second, we get the V_3 directly from the circuit: (hint apply KVL around the outer loop): $\{ V_3 = 6i_x + 60 \}$

If we combined these two, we finally have: $\left\{ V_3 = 6 \frac{V_3 - V_2}{3} + 60 \right\} \rightarrow V_3 = 2V_2 - 60$ --(2)

4. By equation (1) and (2), we have: $V_2 = (48)$

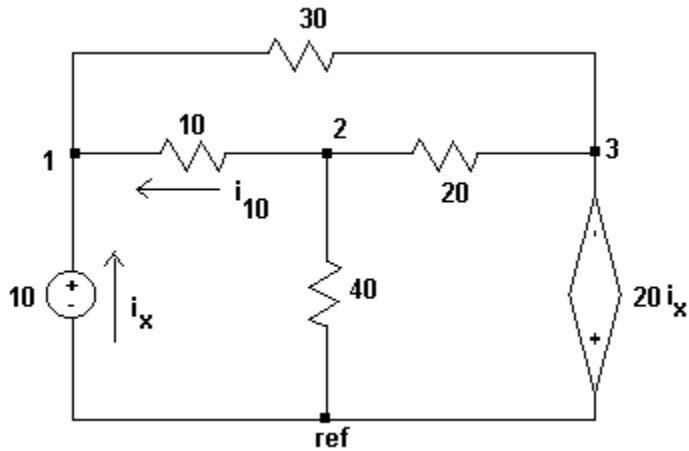2. Using node-voltage method, find the current i_{10} .



SOLUTION

Step 1: Essential nodes

Step 2: Reference

Step 3: Node voltage equations.

$$\text{@node 2: } \frac{V_2 - 10}{10} + \frac{V_2}{40} + \frac{V_2 - V_3}{20} = 0 \text{ -----} > 7V_2 - 2V_3 = 40 \text{ -----(1)}$$

$$\text{@node 1: } -i_x + \frac{10 - V_2}{10} + \frac{10 - V_3}{30} = 0$$

Since $V_3 = -20i_x$ or $i_x = -\frac{V_3}{20}$, the equation @node 1 becomes:

$$\frac{V_3}{20} + \frac{10 - V_2}{10} + \frac{10 - V_3}{30} = 0 \text{ -----} > 6V_2 - V_3 = 80 \text{ -----(2)}$$

From (1) and (2): $V_2 = 24$ and $V_3 = 64$

Your answer: $i_{10} = \underline{\underline{\frac{24 - 10}{10} = 1.4}}$