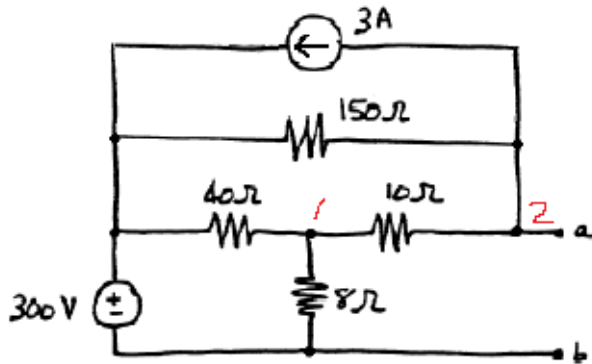


499 HW3 Solution SP22

1



$$V_{th} = V_2$$

At node 1:

$$(V_1 - 300)/40 + V_1/8 + (V_1 - V_2)/10 = 0 \quad \text{---- (1)}$$

At node 2:

$$(V_2 - V_1)/10 + 3 + (V_2 - 300)/150 = 0 \quad \text{---- (2)}$$

From (1) and (2):

$$X := \begin{bmatrix} \frac{1}{40} + \frac{1}{8} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{150} \end{bmatrix}$$

$$Y := \begin{bmatrix} \frac{300}{40} \\ \frac{300}{150} - 3 \end{bmatrix}$$


$$V := \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

From $X \cdot V = Y \implies V = X^{-1} \cdot Y$

$$V := X^{-1} \cdot Y = \begin{bmatrix} 42 \\ 30 \end{bmatrix}$$

$$V_{th} := V_2 = 30$$

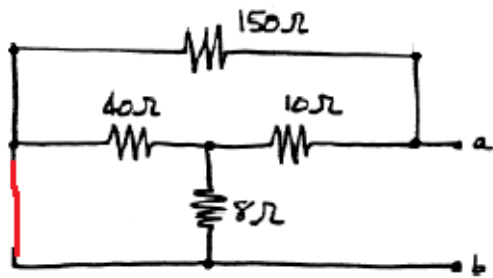
For R_{th} , we apply input resistance method: (deactivation of all independent source first)




$$R_{th} = 150 \parallel (10 + (40 \parallel 8))$$

$$R_1 := 10 + \frac{40 \cdot 8}{40 + 8} = 16.6666667$$
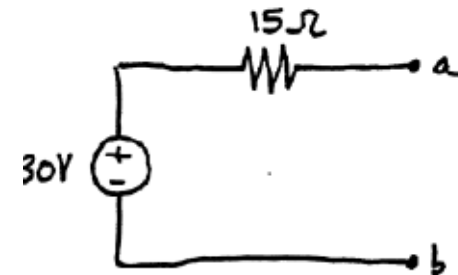
$$R_{th} := \frac{150 \cdot R_1}{150 + R_1} = 15$$



2

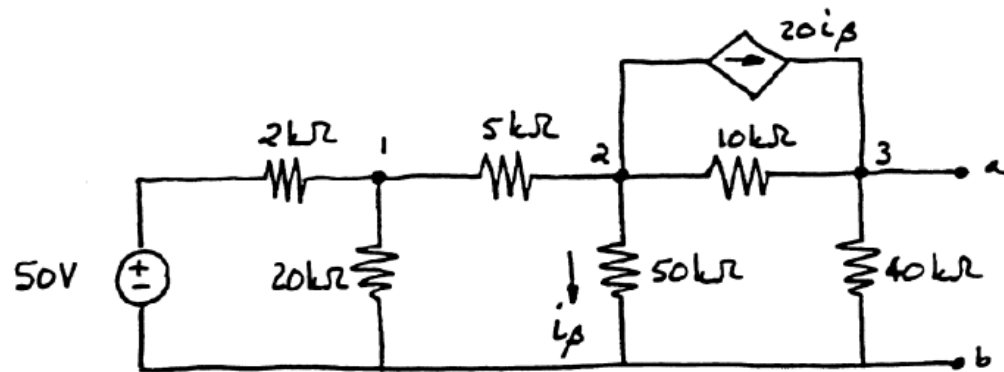

$$V_{th} = V_3$$

At node 1:

$$(V_1 - 50)/2 + V_1/20 + (V_1 - V_2)/5 = 0 \quad \text{-- (1)}$$

At node 2:

$$(V_2 - V_1)/5 + V_2/50 + (V_2 - V_3)/10 + 20 \cdot i_\beta = 0$$

$$\text{Since } i_\beta = V_2/50$$

$$(V_2 - V_1)/5 + V_2/50 + (V_2 - V_3)/10 + (20 \cdot V_2)/50 = 0 \quad \text{-- (2)}$$

$$\text{At node 3: } V_3/40 + (V_3 - V_2)/10 - 20 \cdot (V_2/50) = 0 \quad \text{-- (3)}$$


From (1), (2), and (3):

$$X := \begin{bmatrix} \frac{1}{2} + \frac{1}{20} + \frac{1}{5} & -\frac{1}{5} & 0 \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{50} + \frac{1}{10} + \frac{20}{50} & -\frac{1}{10} \\ 0 & -\frac{1}{10} - \frac{20}{50} & \frac{1}{40} + \frac{1}{10} \end{bmatrix} \quad Y := \begin{bmatrix} \frac{50}{2} \\ 0 \\ 0 \end{bmatrix}$$

$$V := X^{-1} \cdot Y = \begin{bmatrix} 40 \\ 25 \\ 100 \end{bmatrix}$$

$$V_{th} := V_3 = 100$$

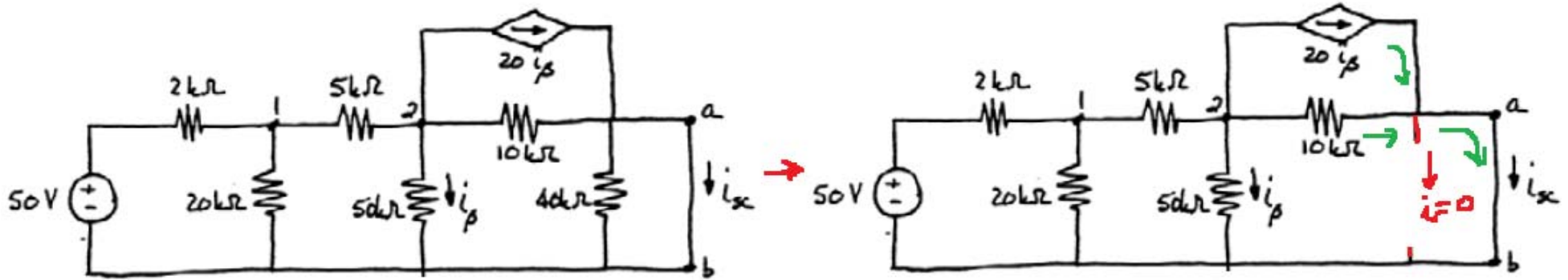For R_{th} , we apply short circuit current approach:



$$i_{sc} = V_2/10 + 20 \cdot i_\beta = V_2/10 + 20 \cdot (V_2/50) \quad [\text{mA}]$$

At node 1:

$$(V_1 - 50)/2 + V_1/20 + (V_1 - V_2)/5 = 0 \quad \text{-- (1)}$$

At node 2:

$$(V_2 - V_1)/5 + V_2/50 + V_2/10 + (20 \cdot V_2)/50 = 0 \quad \text{-- (2)}$$


$$X := \begin{bmatrix} \frac{1}{2} + \frac{1}{20} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{50} + \frac{1}{10} + \frac{20}{50} \end{bmatrix} \quad Y := \begin{bmatrix} \frac{50}{2} \\ 0 \end{bmatrix}$$

$$V := X^{-1} \cdot Y = \begin{bmatrix} 36 \\ 10 \end{bmatrix}$$


$$V_2 := V_2 = 10$$

$$I_{sc} := \frac{V_2}{10} + 20 \cdot \left(\frac{V_2}{50} \right) = 5 \quad \text{mA}$$
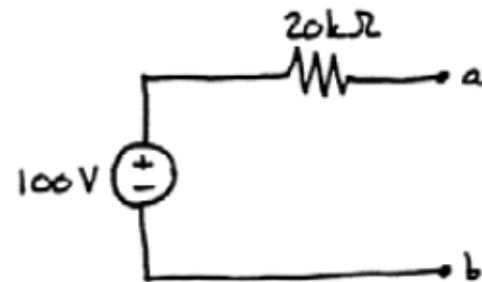
$$R_{th} := \frac{V_{th}}{I_{sc}} = 20 \quad \text{k}\Omega$$



3

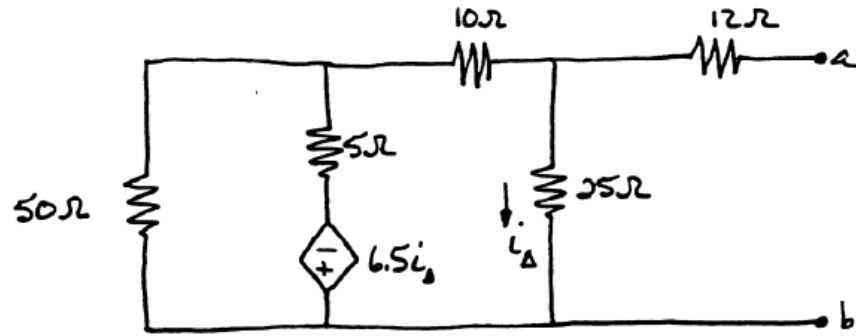

At node 1:

$$V_1 / 50 + (V_1 + 6.5 \cdot i_\Delta) / 5 + (V_1 - V_2) / 10 = 0$$

But since $i_\Delta = V_2 / 25$

$$V_1 / 50 + (V_1 + 6.5 \cdot (V_2 / 25)) / 5 + (V_1 - V_2) / 10 = 0 \quad \text{---- (1)}$$

At node 2:

$$(V_2 - V_1) / 10 + V_2 / 25 + (V_2 - V_T) / 12 = 0$$

For calculation purpose (Especially with Smath), let us assume $V_T = 1$,

$$\text{Then } I_T = (1 - V_2) / 12 \text{ and } R_{th} = V_T / I_T = 1 / I_T$$

$$(V_2 - V_1) / 10 + V_2 / 25 + (V_2 - 1) / 12 = 0 \quad \text{----- (2)}$$


From (1) and (2):

$$X := \begin{bmatrix} \frac{1}{50} + \frac{1}{5} + \frac{1}{10} & \frac{6.5}{25 \cdot 5} - \frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{25} + \frac{1}{12} \end{bmatrix} \quad Y := \begin{bmatrix} 0 \\ \frac{1}{12} \end{bmatrix}$$

$V_{th} = 0$ since there is no independent source

And the only approach to get R_{th} is the test source (voltage) method and

$$R_{th} = V_T / I_T$$

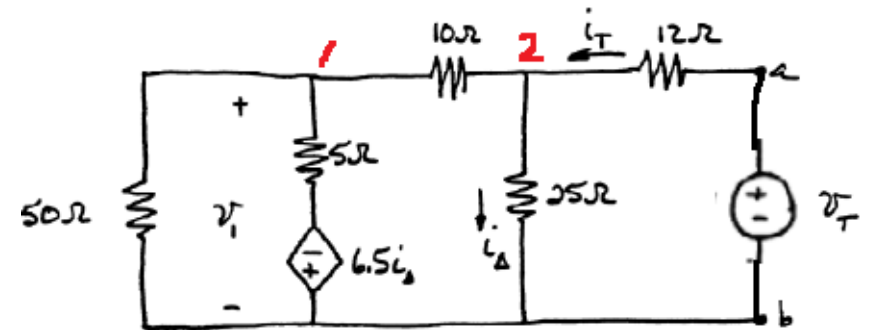

$$\text{And } I_T = (V_T - V_2) / 12$$

$$V := X^{-1} \cdot Y = \begin{bmatrix} 0.06 \\ 0.4 \end{bmatrix}$$


$$V_2 := V_2 = 0.4$$

$$I_T := \frac{(1 - V_2)}{12} = 0.05$$

$$R_{th} := \frac{1}{I_T} = 20$$



4

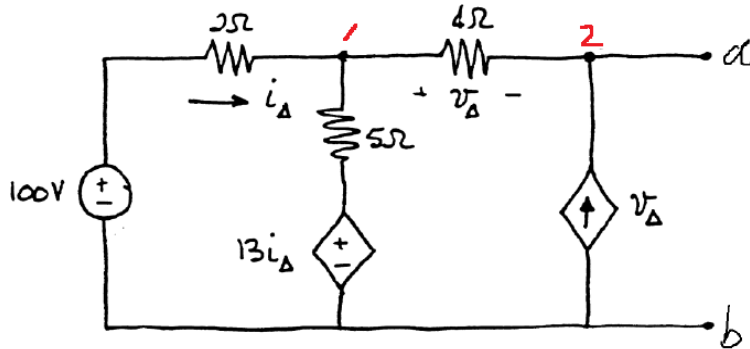

$$V_{th} = V_2$$

At node 1:

$$(V_1 - 100)/2 + (V_1 - 13 \cdot i_\Delta)/5 + (V_1 - V_2)/4 = 0$$

$$\text{Since } i_\Delta = (100 - V_1)/2$$

$$(V_1 - 100)/2 + (V_1 - 13 \cdot ((100 - V_1)/2))/5 + (V_1 - V_2)/4 = 0 \quad (1)$$

At node 2:

$$(V_2 - V_1)/4 - v_\Delta = 0$$

$$\text{But } v_\Delta = (V_1 - V_2)$$

$$(V_2 - V_1)/4 - (V_1 - V_2) = 0 \quad (2)$$

From (1) and (2):


$$X := \begin{bmatrix} \frac{1}{2} + \frac{1}{5} + \frac{13}{5} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} - 1 & \frac{1}{4} + 1 \end{bmatrix}$$

$$Y := \begin{bmatrix} \frac{100}{2} + \frac{13 \cdot 100}{5} \\ 0 \end{bmatrix}$$

$$V := X^{-1} \cdot Y = \begin{bmatrix} 90 \\ 90 \end{bmatrix}$$

$$V_{th} := V_2 = 90$$

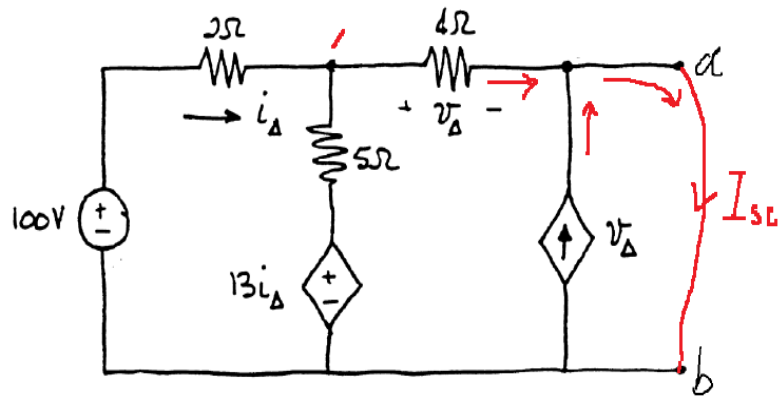For Rth, let us apply short circuit approach:



$$I_{sc} = v_{\Delta} + V1/4 \quad \text{but } v_{\Delta}=V1$$

$$I_{sc} = V1 + V1/4 = (5/4)V1$$

At node 1:

$$(V1 - 100)/2 + (V1 - 13 \cdot (100 - V1)/2)/5 + V1/4 = 0 \quad \text{--- (1)}$$

$$V1 \left(\frac{1}{2} + \frac{1}{5} + \frac{13}{5} + \frac{1}{4} \right) = \frac{100}{2} + \frac{13 \cdot 100}{2 \cdot 5}$$

$$V1 := \frac{\frac{100}{2} + \frac{13 \cdot 100}{2 \cdot 5}}{\frac{1}{2} + \frac{1}{5} + \frac{13}{5} + \frac{1}{4}} = 80$$

$$I_{sc} := \frac{5}{4} \cdot V1 = 100$$

$$R_{th} := \frac{V_{th}}{I_{sc}} = 0.9$$

