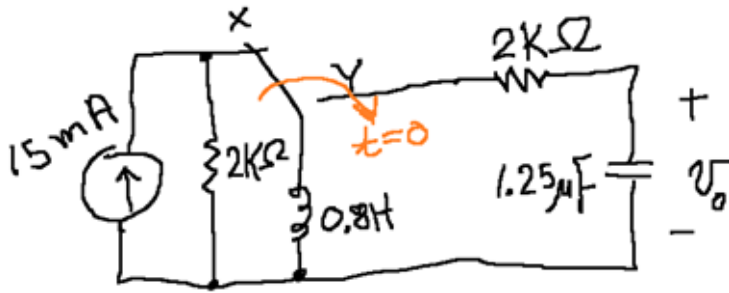


499 HW4 SP22

1

$L := 0.8$      $C := 1.25 \cdot 10^{-6}$      $R := 2000$




Before  $t=0$ :

$v_0 := 0$      $i_0 := 15 \cdot 10^{-3}$   
 L becomes short circuit

$L \cdot i_0 = 0.012$

After  $t=0$ : s - domain circuit

Voltage across the C by voltage division

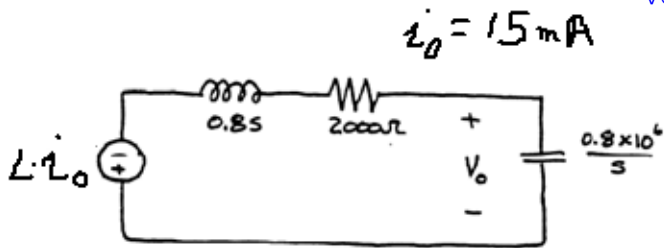

$$V := - \frac{L \cdot i_0 \cdot \left( \frac{1}{sC} \right)}{R + s \cdot L + \frac{1}{s \cdot C}}$$

$$V := - \frac{\frac{L \cdot i_0}{L \cdot C}}{s^2 + \frac{R}{L} \cdot s + \frac{1}{L \cdot C}}$$

$$V := - \frac{L \cdot i_0}{R \cdot s \cdot C + s^2 \cdot L \cdot C + 1}$$

$\frac{R}{L} = 2500$

$\frac{1}{L \cdot C} = 1 \cdot 10^6$

$\frac{i_0}{C} = 12000$

$$V := - \frac{\frac{i_0}{C}}{s^2 + \frac{R \cdot s}{L} + \frac{1}{L \cdot C}}$$

$$V := - \frac{12000}{s^2 + 2500 \cdot s + 1 \cdot 10^6}$$

$\frac{30}{2000} = 0.015$

$$V := \frac{-12000}{(s + 500) \cdot (s + 2000)}$$


$$V := \frac{K1}{s + 500} + \frac{K2}{s + 2000}$$

$K1 := -8$


$K2 := 8$

$v(t) = (-8 \cdot \exp(-500t) + 8 \cdot \exp(-2000t)) \cdot u(t)$

2

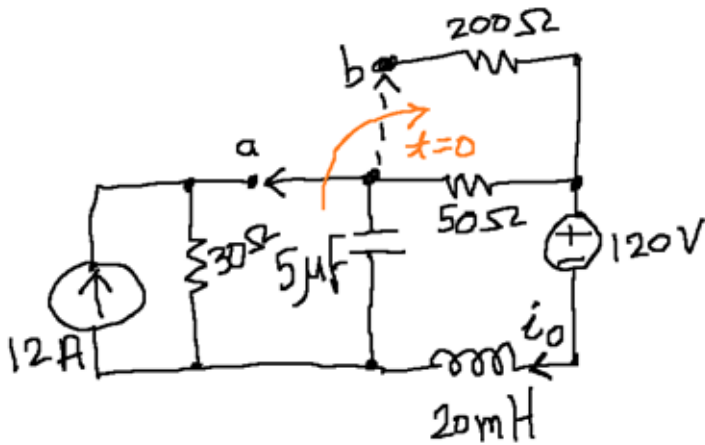

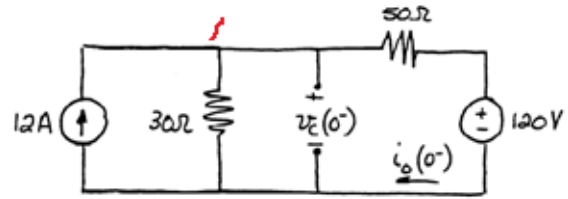Before  $t < 0$ , C becomes open and L becomes short



$v_1 = v_0$  and  $i_0 =$  current through 50 ohm resistor

$$V_1 := \frac{12 + \frac{12}{5}}{\frac{1}{30} + \frac{1}{50}} = 270$$


$$-12 + V_1/30 + (V_1-120)/50 = 0$$

$$V_1(1/30 + 1/50) = 12 + 120/50$$

$$v_0 := V_1 = 270$$

$$i_0 := \frac{V_1 - 120}{50} = 3$$

After  $t > 0$ :

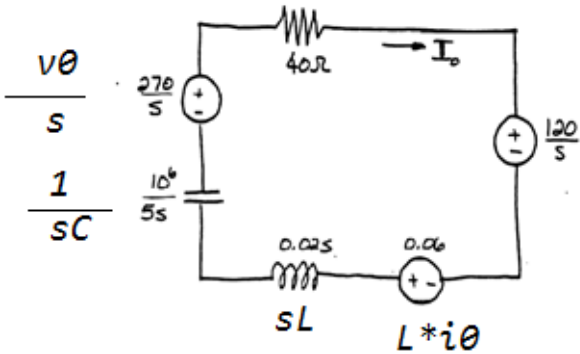

$$I := \frac{\frac{270}{s} + L \cdot i_0 - \frac{120}{s}}{s \cdot L + 40 + \frac{1}{s \cdot C}}$$

$$I := \frac{270 \cdot C + L \cdot i_0 \cdot C \cdot s - 120 \cdot C}{s^2 \cdot L \cdot C + 40 \cdot s \cdot C + 1}$$

$$L := 0.02 \quad C := 5 \cdot 10^{-6}$$

$$I := \frac{\frac{270}{L} + s \cdot i_0 - \frac{120}{L}}{s^2 + \frac{40}{L} \cdot s + \frac{1}{L \cdot C}}$$

$$\frac{270}{L} - \frac{120}{L} = 7500 \quad \frac{40}{L} = 2000 \quad \frac{1}{L \cdot C} = 1 \cdot 10^7$$


$$I := \frac{3 \cdot s + 7500}{s^2 + 2000 \cdot s + 10^7}$$

$$I := \frac{3 \cdot s + 7500}{(s + 1000)^2 + 3000}$$

$$I := \frac{3 \cdot (s + 1000)}{(s + 1000)^2 + 3000} + \frac{\frac{4500}{3000} \cdot 3000}{(s + 1000)^2 + 3000}$$

$$i(t) = \exp(-1000t) \cdot (3 \cdot \cos(3000t) + 1.5 \cdot \sin(3000t)) \cdot u(t)$$

3

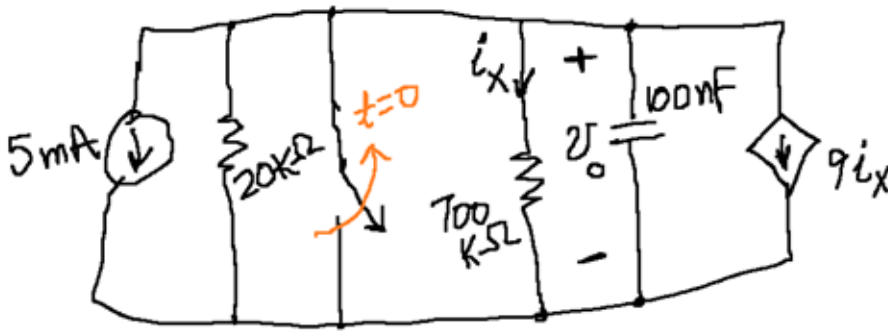

Before  $t < 0$ , all current flows through the shorted line, voltage is zero. So the initial voltage in the capacitor is zero.

After  $t > 0$ , s-domain circuit

Apply node voltage method, the node voltage is voltage across the capacitor,  $v$

$$\frac{I}{s} + \frac{V(s)}{200000} + \frac{V(s)}{700000} + 9 \cdot \frac{V(s)}{700000} + sCV(s) = 0 \quad \text{because } ix = V/700K$$

$$I := 5 \cdot 10^{-3}$$

$$C := 100 \cdot 10^{-9}$$

$$V := \frac{-\frac{I}{s}}{s \cdot C + \frac{1}{20000} + \frac{10}{700000}}$$

$$\frac{I}{C} = 50000$$

$$V := \frac{-I}{\left( s^2 \cdot C + \left( \frac{1}{20000} + \frac{10}{700000} \right) \cdot s \right)}$$

$$\frac{\frac{1}{20000} + \frac{10}{700000}}{C} = 642.8571429$$

$$V := \frac{-\frac{I}{C}}{\left( s^2 + \left( \frac{\frac{1}{20000} + \frac{10}{700000}}{C} \right) \cdot s \right)}$$

$$K2 := -\frac{50000}{642.86} = -77.7774321$$

$$V := \frac{-50000}{s \cdot (s + 642.86)}$$

$$K1 := -K2 = 77.7774321$$


$$V := \frac{K1}{s} + \frac{K2}{s + 642.86}$$

$$v(t) = 77.78 \cdot (1 - \exp(-642.86t)) \quad u(t)$$

4



For  $t < 0$ :

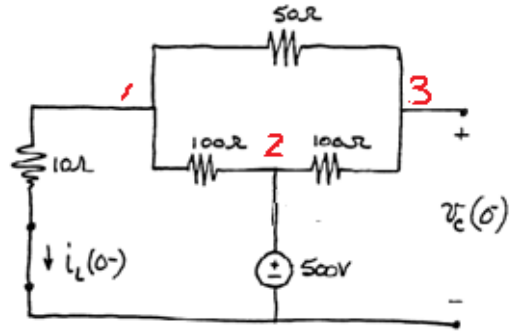

$V_2 = 500$  and  $V_3 = v_0$ ,  $i_0 = V_1/10$

Node 1:  $V_1/10 + (V_1-500)/100 + (V_1-V_3)/50 = 0$

Node 3:  $(V_3-500)/100 + (V_3-V_1)/50 = 0$

$V_2 := 500$

$$X := \begin{bmatrix} \frac{1}{10} + \frac{1}{100} + \frac{1}{50} & -\frac{1}{50} \\ -\frac{1}{50} & \frac{1}{100} + \frac{1}{50} \end{bmatrix} \quad Y := \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

$$V := X^{-1} \cdot Y = \begin{bmatrix} 71.4285714 \\ 214.2857143 \end{bmatrix}$$

$V_1 := V_1 = 71.4285714$

$V_3 := V_2 = 214.2857143$

Therefore

$$i_0 := \frac{V_1}{10} = 7.1428571$$


$$v_0 := V_3 = 214.2857143$$

After  $t > 0$  s-domain circuit

$L := 0.002$

$C := 5 \cdot 10^{-6}$

$L \cdot i_0 = 0.0142857$

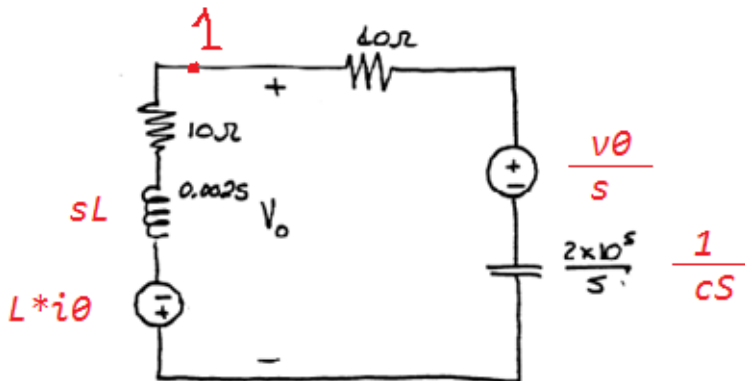

By node voltage method

$$V(s) = V_1$$

$$\frac{V_1 + L \cdot i_0}{10 + s \cdot L} + \frac{V_1 - \frac{v_0}{s}}{40 + \frac{1}{s \cdot C}} = 0$$

$$V_1 \cdot \left( \frac{1}{10 + s \cdot L} + \frac{1}{40 + \frac{1}{s \cdot C}} \right) + \left( \frac{L \cdot i_0}{10 + s \cdot L} + \frac{-\frac{v_0}{s}}{40 + \frac{1}{s \cdot C}} \right) = 0$$

$$V1 \cdot \left( \frac{1}{10 + s \cdot L} + \frac{1 \cdot C \cdot s}{40 \cdot C \cdot s + 1} \right) + \left( \frac{L \cdot i0}{10 + s \cdot L} + \frac{-v0 \cdot C}{40 \cdot C \cdot s + 1} \right) = 0$$

$$V1 \cdot \left( \frac{1 + 40 \cdot C \cdot s + C \cdot s \cdot (10 + s \cdot L)}{(10 + s \cdot L) \cdot (40 \cdot C \cdot s + 1)} \right) + \frac{L \cdot i0 \cdot (40 \cdot C \cdot s + 1) - v0 \cdot C \cdot (10 + s \cdot L)}{(10 + s \cdot L) \cdot (40 \cdot C \cdot s + 1)} = 0$$

$$V1 := \frac{L \cdot i0 \cdot (40 \cdot C \cdot s + 1) - v0 \cdot C \cdot (10 + s \cdot L)}{C \cdot L \cdot s^2 + 50 \cdot C \cdot s + 1}$$

$$V1 := \frac{\frac{i0}{C} \cdot (40 \cdot C \cdot s + 1) - \frac{v0}{L} \cdot (10 + s \cdot L)}{s^2 + \frac{50}{L} \cdot s + \frac{1}{L \cdot C}}$$

$$V1 := \frac{(40 \cdot i0 - v0) \cdot s + \frac{i0}{C} - \frac{10 \cdot v0}{L}}{s^2 + \frac{50}{L} \cdot s + \frac{1}{L \cdot C}}$$

$$\frac{50}{L} = 25000 \quad \frac{1}{L \cdot C} = 1 \cdot 10^8$$

$$40 \cdot i0 - v0 = 71.4285714$$

$$\frac{i0}{C} - \frac{10 \cdot v0}{L} = 3.5714286 \cdot 10^5$$

$$V1 := \frac{71.43 \cdot s + 357143}{s^2 + 25000 \cdot s + 10^8}$$

$$V1 := \frac{71.43 \cdot s + 357143}{(s + 5000) \cdot (s + 20000)}$$

$$V1 := \frac{K1}{s + 5000} + \frac{K2}{s + 20000}$$

$$(K1 + K2) \cdot s + K1 \cdot 20000 + K2 \cdot 5000 = 71.43s + 357143$$

$$K1 + K2 = 71.43 \quad \rightarrow \quad K1 = 71.43 - K2$$

$$K2 := \frac{71.43 \cdot 20000 - 357143}{15000} = 71.4304667$$

$$K1 := 71.43 - K2 = -0.0004667$$

$$K1 + K2 = 71.43$$

$$K1 \cdot 20000 + K2 \cdot 5000 = 3.57143 \cdot 10^5$$

$$v(t) = (-0.00047 \cdot \exp(-5000t) + 71.4 \cdot \exp(20000t)) u(t)$$